

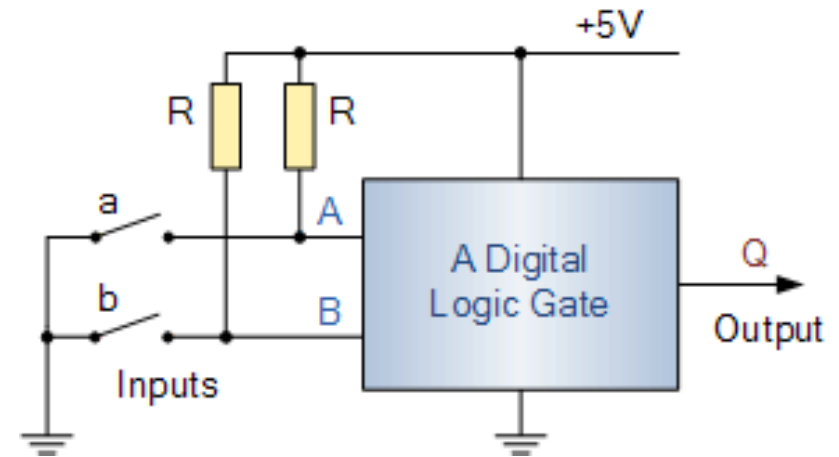


Pull Up and Pull Down Resistor

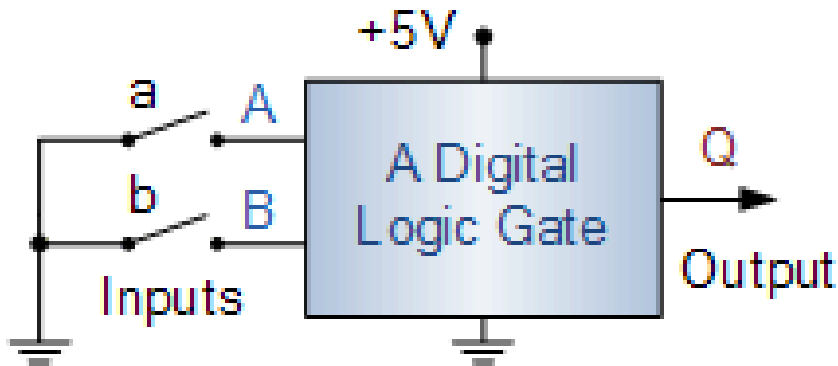- Pull-up and Pull-down resistors are used to correctly bias the inputs of digital gates to **prevent them from floating** about randomly when there is no input condition



Calculating Pull-Up Resistor Value

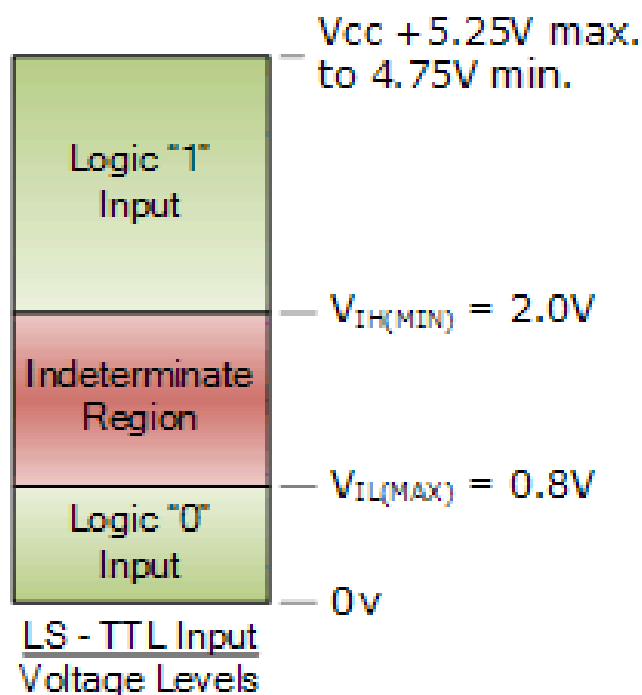

- TTL 74LSxxx series:

- Input high: $V_{IH(min)} = 2.0V$, $I_{IH(max)} = 20\mu A$
- Input low: $V_{IL(max)} = 0.8V$, $I_{IL(max)} = 0.4mA$

Single Gate Pull-up Resistor Value

$$R_{MAX} = \frac{V_{CC} - V_{IH(MIN)}}{I_{IH}} = \frac{5 - 2}{20 \times 10^{-6}} = 150K\Omega$$

Multiple Gate Pull-up Resistor Value (10 inputs)

$$R_{MAX} = \frac{V_{CC} - V_{IH(MIN)}}{10 \times I_{IH}} = \frac{5 - 2}{10 \times 20 \times 10^{-6}} = 15K\Omega$$

Calculating Pull-Up Resistor Value

- A *Pull-down resistor* works in the same way as the previous pull-up resistor, except this time the logic gates input is tied to ground, logic level “0” (LOW)


$$R_{MAX} = \frac{V_{IL(MAX)} - 0}{I_{IL}} = \frac{0.8 - 0}{400 \times 10^{-6}} = 2K\Omega$$

Example

- TTL 74LS00 NAND Gates along with a single-pole double-throw switch are to be used to make a simple set-reset bistable circuit signal. Calculate:
 - 1). The maximum pull-up resistor values if the voltage representing a logic HIGH input is to be held at 4.5 volts when the switch is open, and
 - 2). The current flowing through the resistor when the switch is closed (assume zero contact resistance). Also draw the circuit.
- Data given: $V_{cc} = 5V$, $V_{IH} = 4.5V$, and $I_{IH(max)} = 20\mu A$

Answer

Set-Reset Bistable Circuit


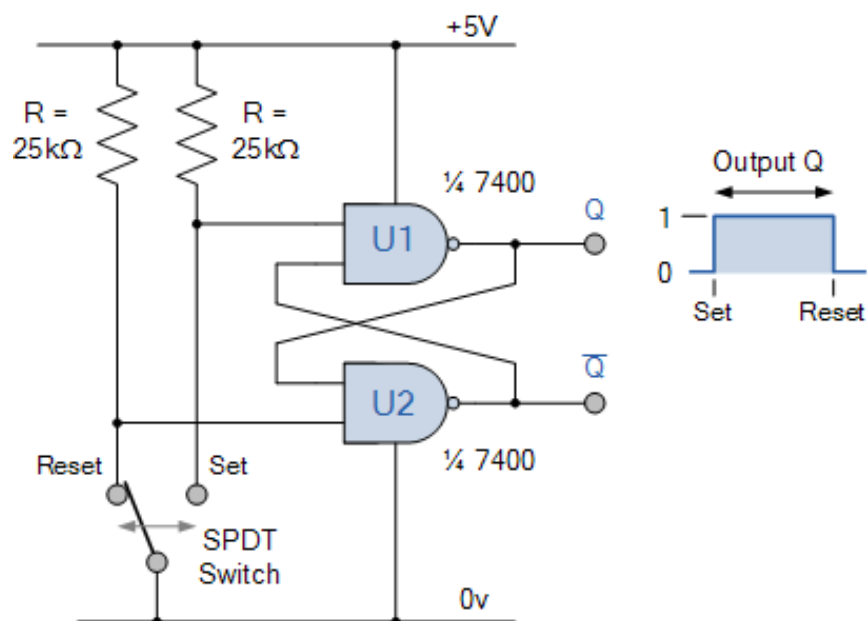


$$R_{MAX} = \frac{V_{CC} - V_{IH}}{I_{IH}} = \frac{5 - 4.5}{20 \times 10^{-6}} = 25K\Omega$$

$$I_R = \frac{V_{CC}}{R} = \frac{5V}{25k\Omega} = 200\mu A \text{ or } 0.2mA$$


C02015

Diode & Its Applications

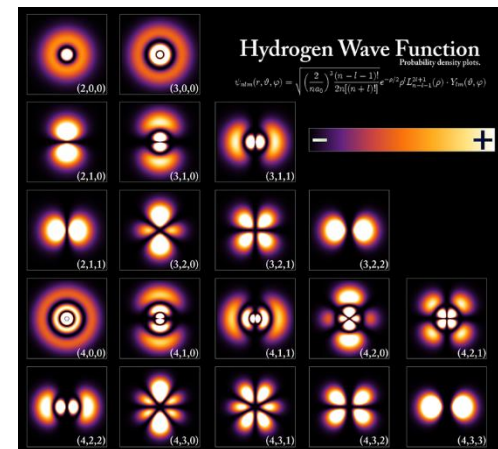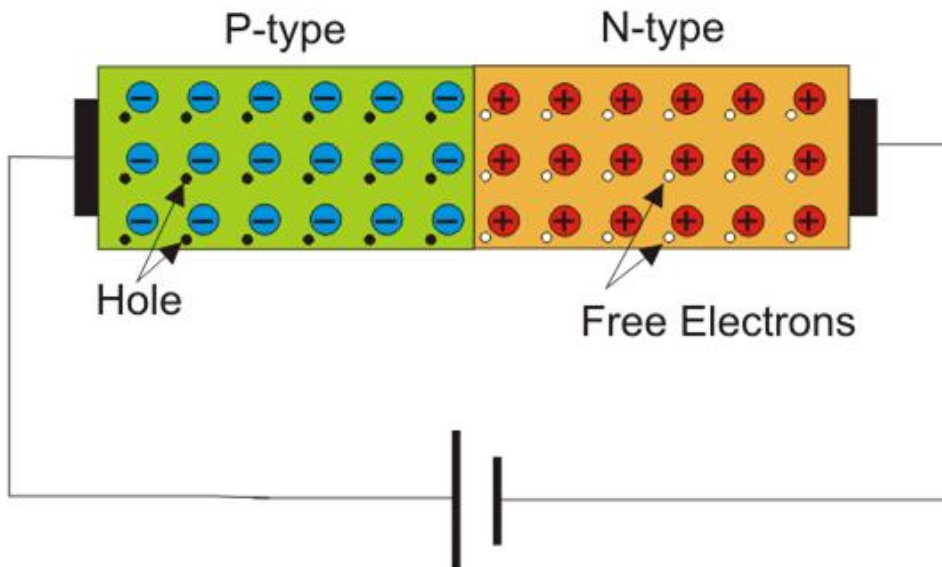


Diode and Its Applications

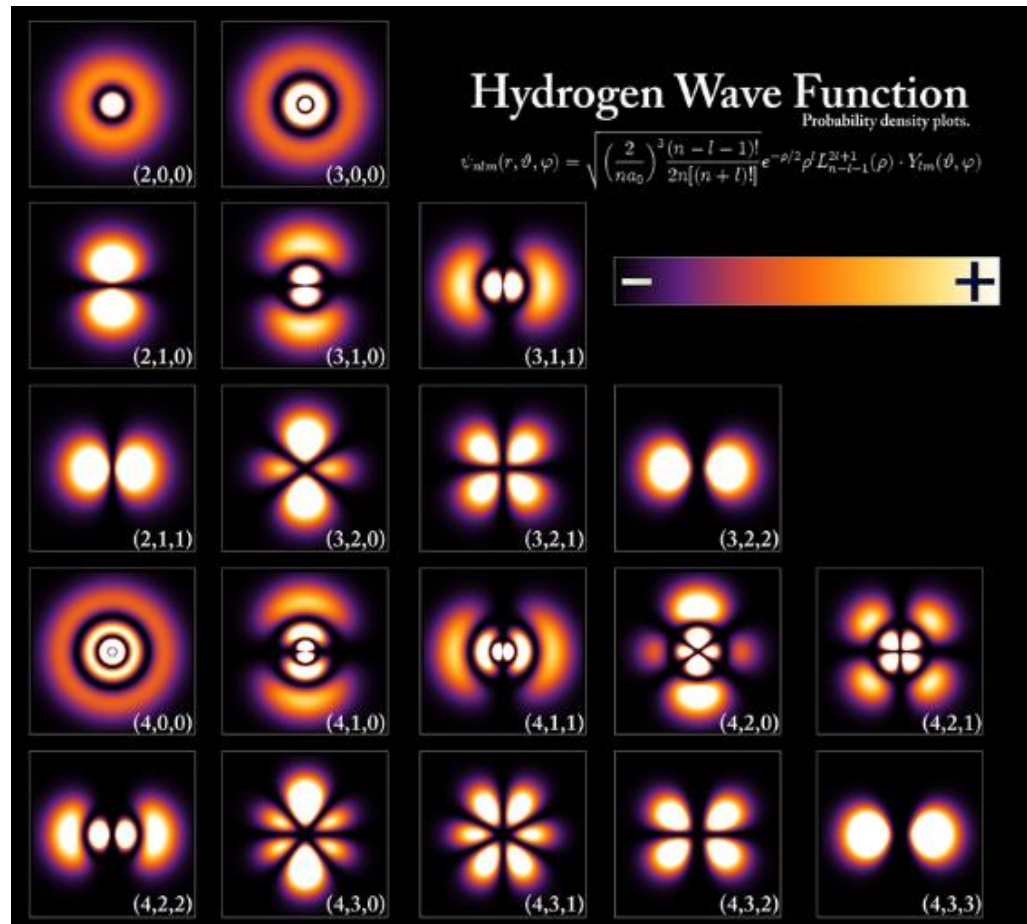- Introduction to semiconductor
- Diode
- Applications




Semiconductor

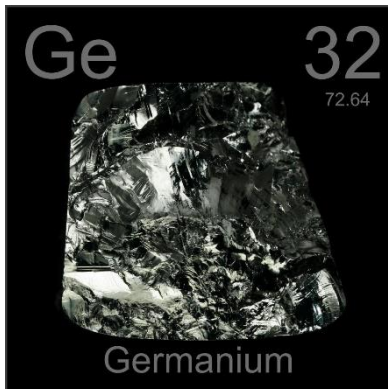- Semiconductors are a special class of elements having a conductivity between that of a good conductor and that of an insulator.
- Two classes: single-crystal and compound
- The three semiconductors used most frequently in the construction of electronic devices are [Ge](#), [Si](#), and [GaAs](#).



Germanium (Ge)

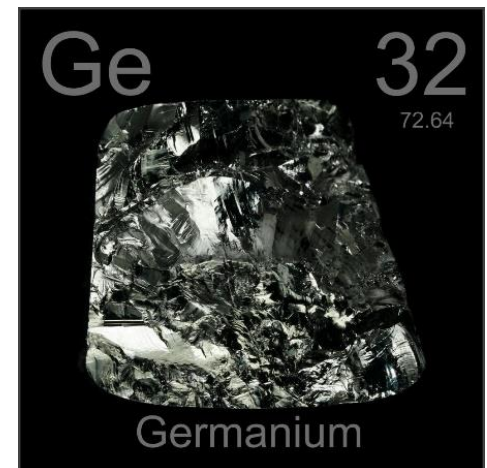- The discovery of the diode in 1939 and the transistor in 1947 germanium was used almost exclusively
- Advantages
 - Easy to find
 - Fairly large quantities
 - Easy to refine to obtain very high levels of purity
- Disadvantage
 - Sensitivity to changes in temperature



Silicon (Si)

- 1954 the first silicon transistor was introduced
- Advantages
 - Less temperature sensitive
 - The most abundant materials on earth
 - High levels of purity
- Disadvantage
 - Sensitive to issues of speed.





Gallium Arsenide (GaAs)

- The first GaAs transistor in the early 1970s.
- New transistor had speeds of operation up to five times that of Si.
- GaAs was more difficult to manufacture at high levels of purity, was more expensive.
- Today, it is often used as the base material for new high-speed, very large scale integrated (VLSI) circuit designs.


Diode

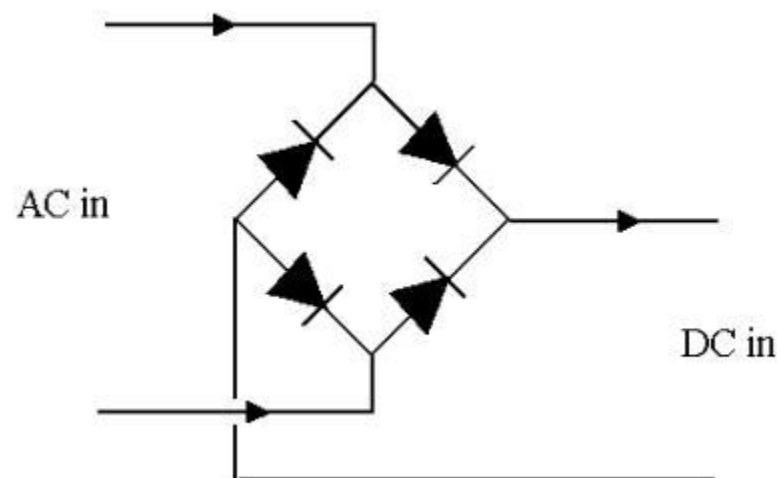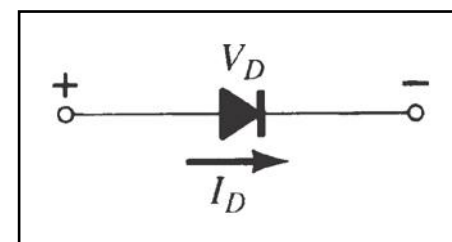- The diode is the simplest and most fundamental non-linear circuit element
- Like a resistor, it has two terminals
- Unlike a resistor, it has a non-linear current-voltage characteristics.
- Its use in rectifiers is the most common application




Diode

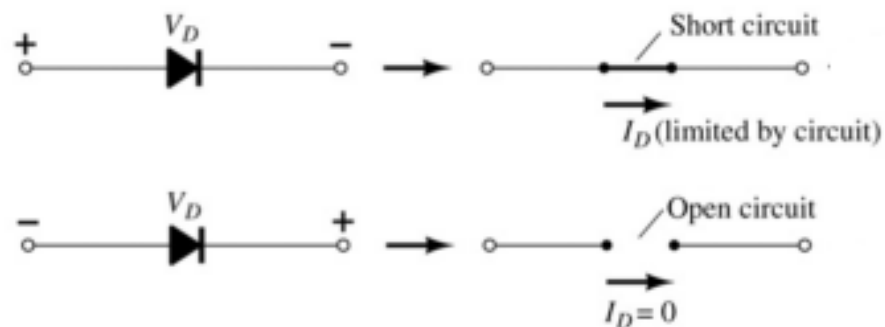
- Diode is an electric device which allows current to flow only in one direction.



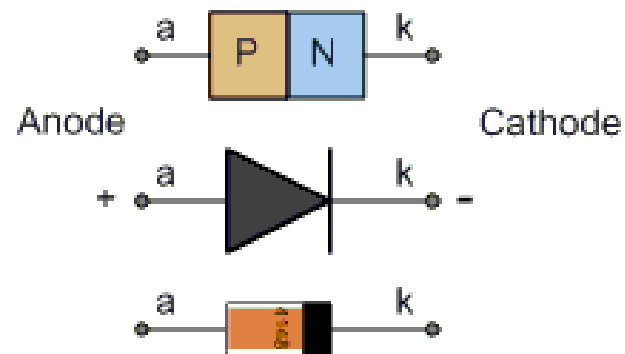- The voltage applied to the semiconductor diode is referred to as bias voltage
- There are two types of bias voltage
 - Forward biased
 - Reversed biased




PN Junction and Diode

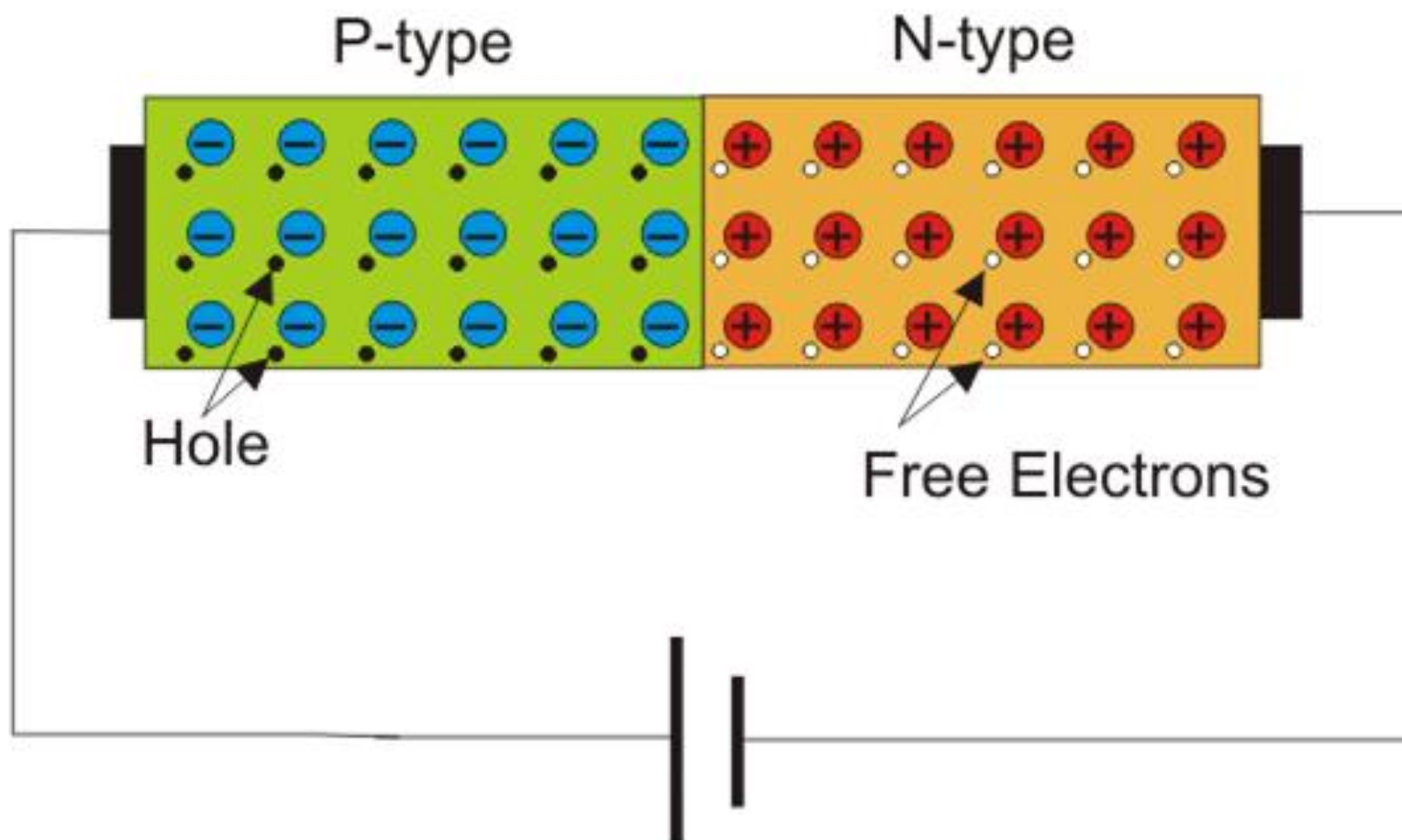


PN Junction and Diode

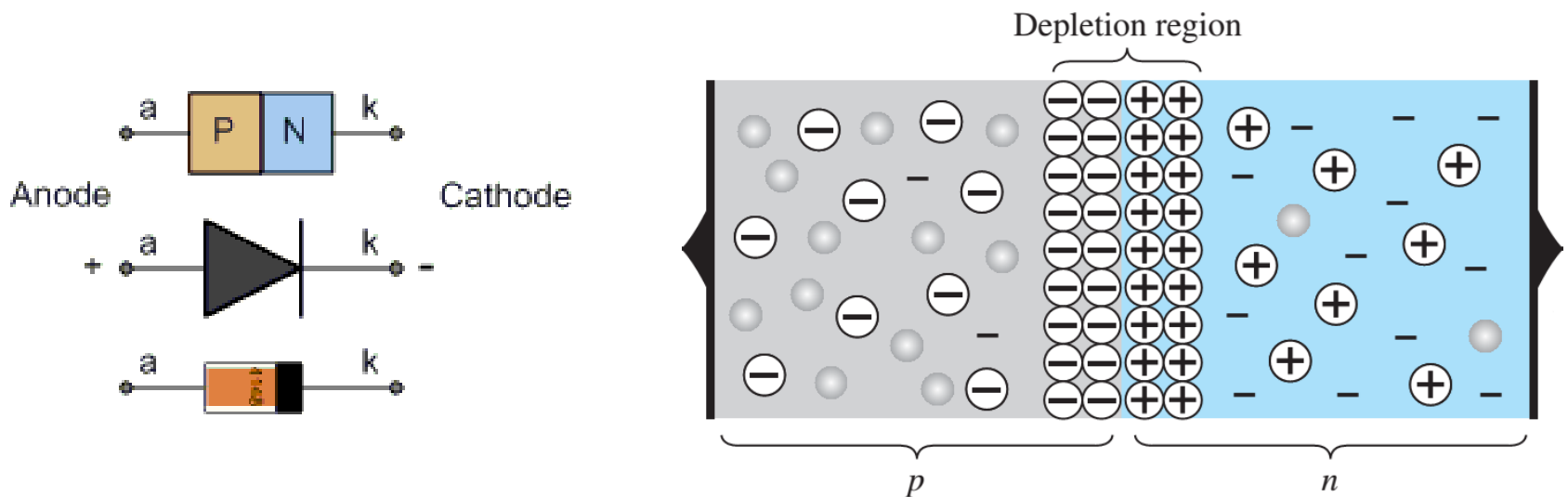- One end of a silicon or germanium crystal can be doped as a p-type material and the other end as an n-type material.
- At the p-n junction, the excess conduction-band electrons on the n-type side are attracted to the valence-band holes on the p-type side.





Diode – No Bias

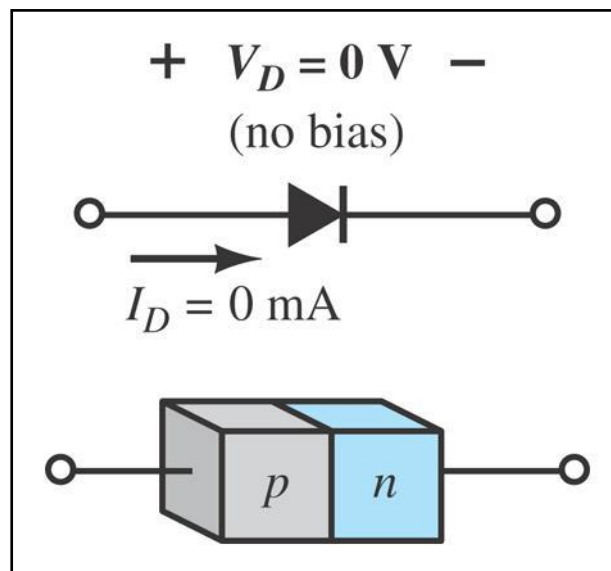- No external voltage is applied: $V_D = 0\text{ V}$
- There is no diode current: $I_D = 0\text{ A}$
- Only a modest depletion region exists





Diode – Forward Bias

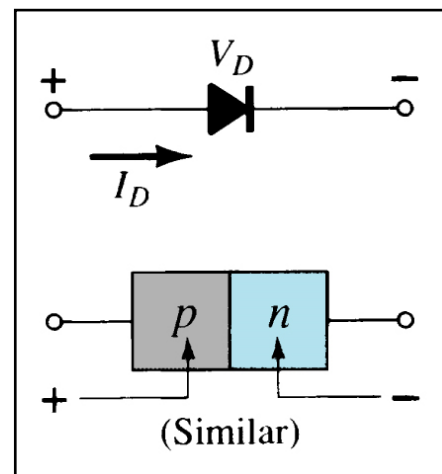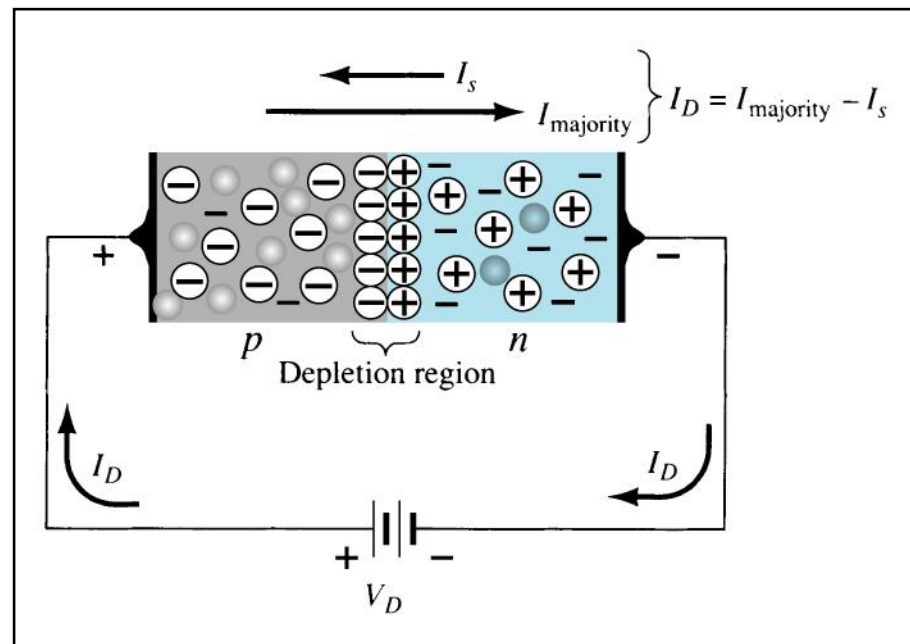- External voltage is applied across the p - n junction in the same polarity as the p - and n -type materials.
- The forward voltage causes the depletion region to narrow.
- The electrons and holes are pushed toward the p - n junction.
- The electrons and holes have sufficient energy to cross the p - n junction



Diode – Reverse Bias

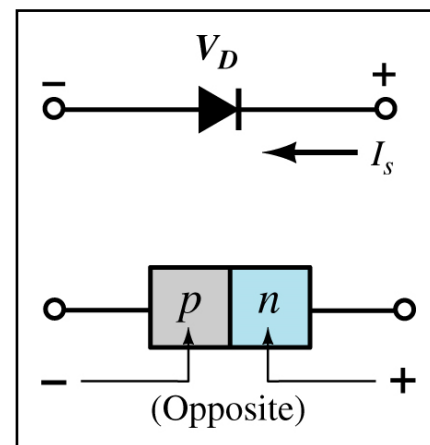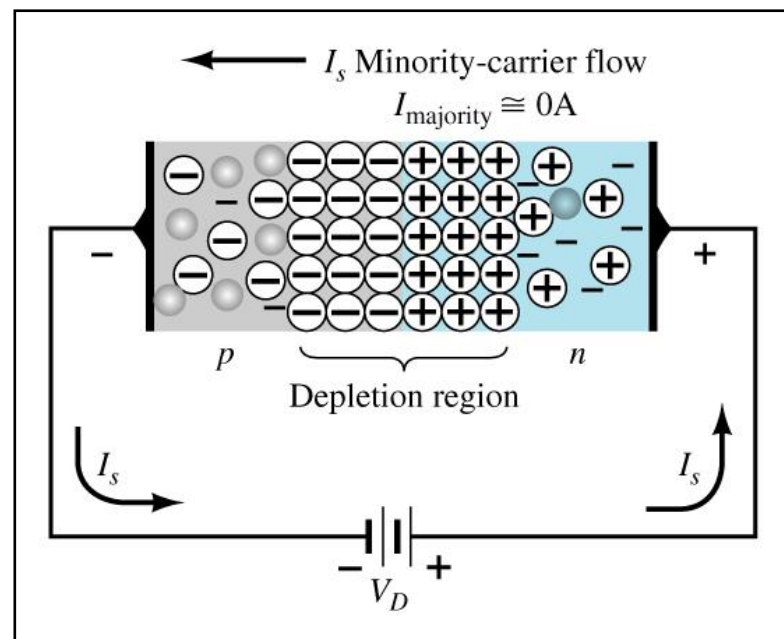- External voltage is applied across the p - n junction in the opposite polarity of the p - and n -type materials.
- The reverse voltage causes the depletion region to widen.
- The electrons in the n -type material are attracted toward the positive terminal of the voltage source.
- The holes in the p -type material are attracted toward the negative terminal of the voltage source.



Diode Equivalent Circuit


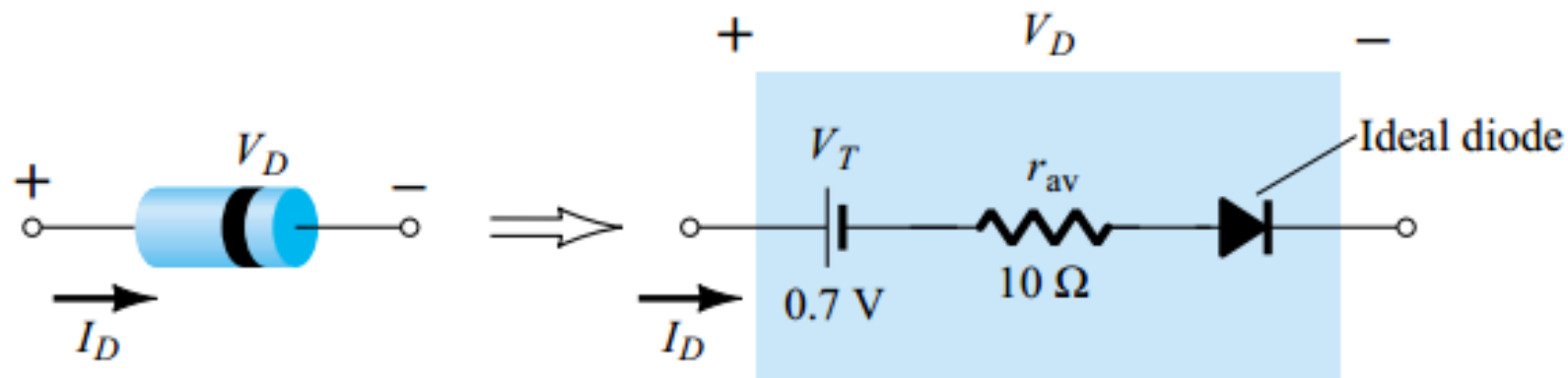
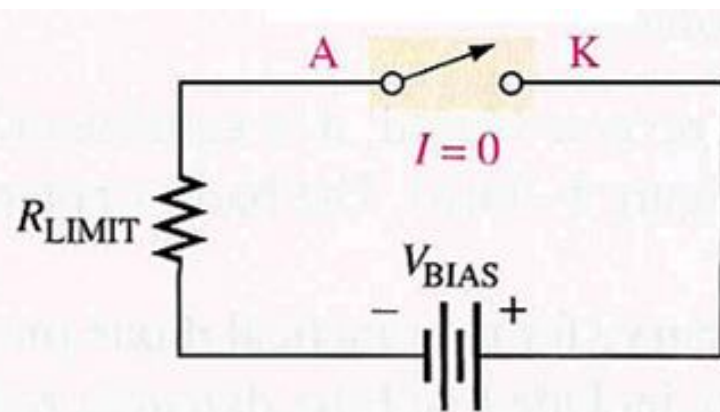


Figure 1.32 Components of the piecewise-linear equivalent circuit.

Ideal Diode Model

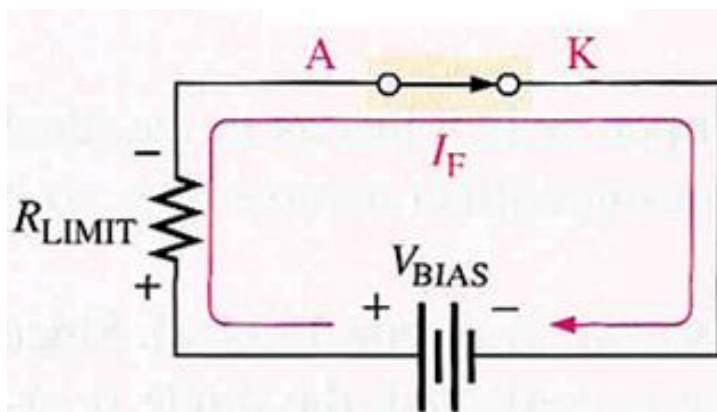- Works as a switch
 - Forward bias (switch is close)
 - Reverse bias (switch is open)
- Threshold battery voltage and internal resistance are ignored.




$$I_F = \frac{V_{BIAS}}{R_{LIMIT}}$$

Forward bias


Reverse bias

Practical Diode Model
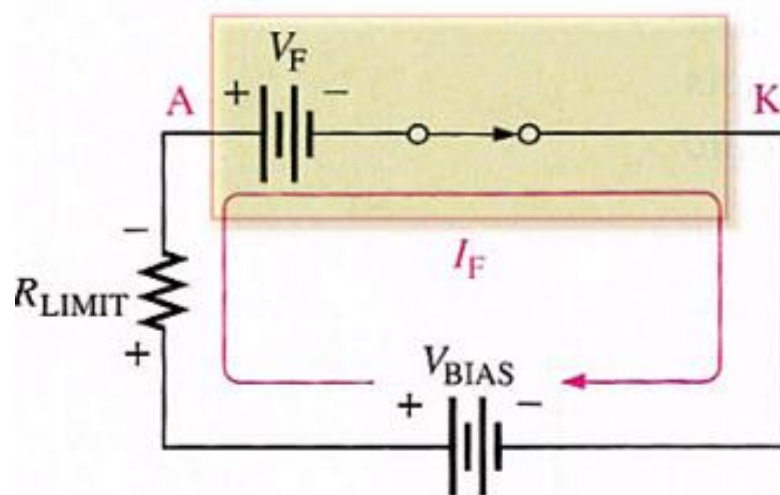
$$I_F = \frac{V_{BIAS} - V_F}{R_{LIMIT}}$$



Forward bias

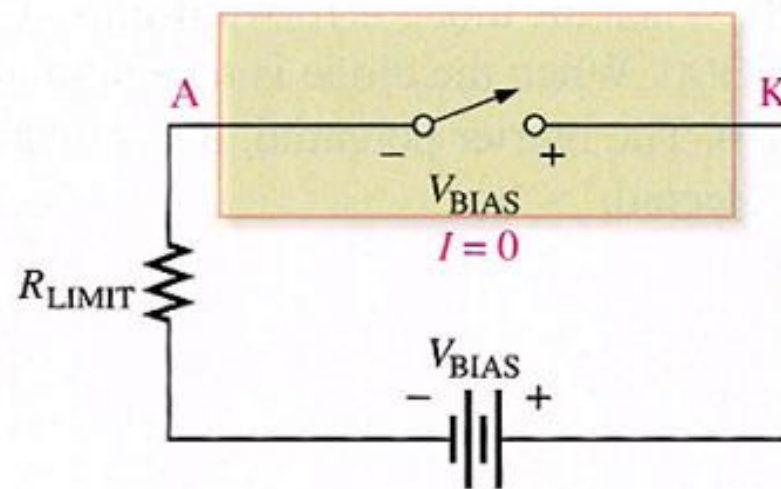


Reverse bias

■ Constants

- Silicon Diode: $V_F = 0.7V$ ($V_F = V_{BIAS}$ if $V_{BIAS} < 0.7V$)
- Germanium Diode: $V_F = 0.3V$ ($V_F = V_{BIAS}$ if $V_{BIAS} < 0.3V$)


Complete Diode Model
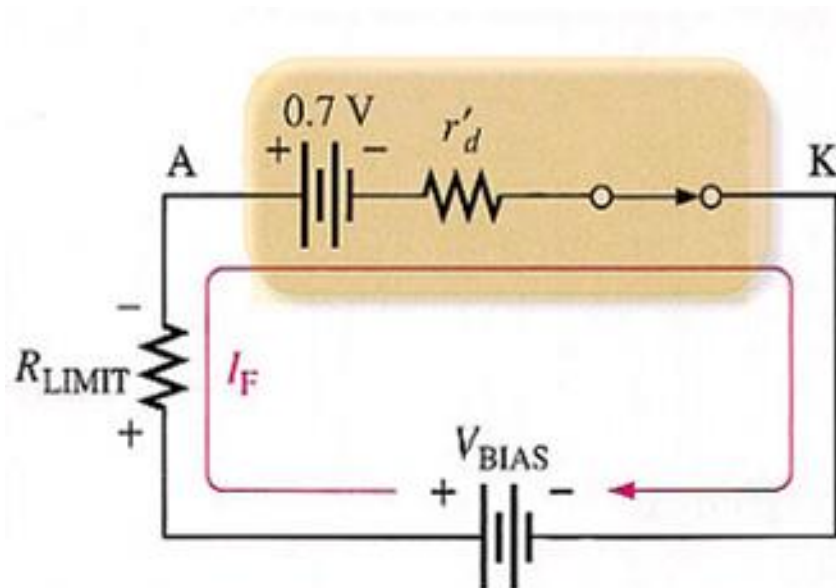
$$I_F = \frac{V_{\text{BIAS}} - 0.7 \text{ V}}{R_{\text{LIMIT}} + r'_d}$$



Forward bias

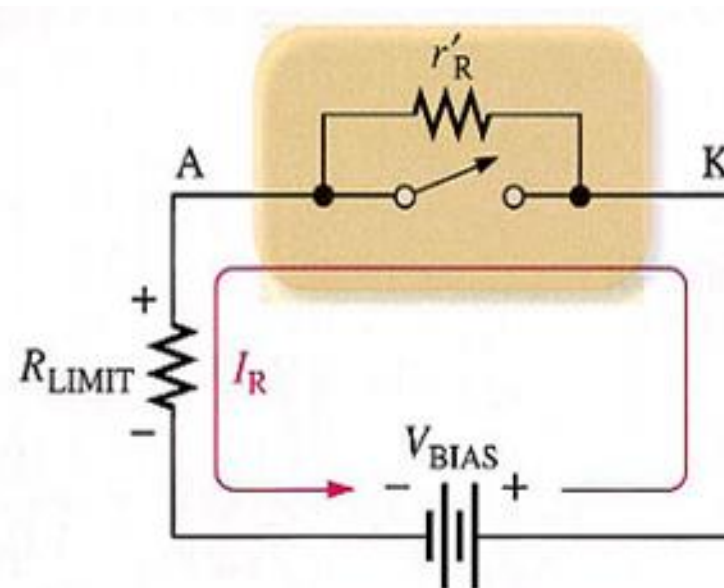
$$I_R = \frac{V_{\text{BIAS}}}{R_{\text{LIMIT}} + r'_R}$$



Reverse bias

Exercise 3

- Given circuit
 - Forward bias voltage $V_F = 0.7V$
 - Internal resistance $r'_d = 10\Omega$
- Determine V_F , I_F and V_{RLIMIT} for three diode models
 - Ideal diode model
 - Practical diode model
 - Complete diode model

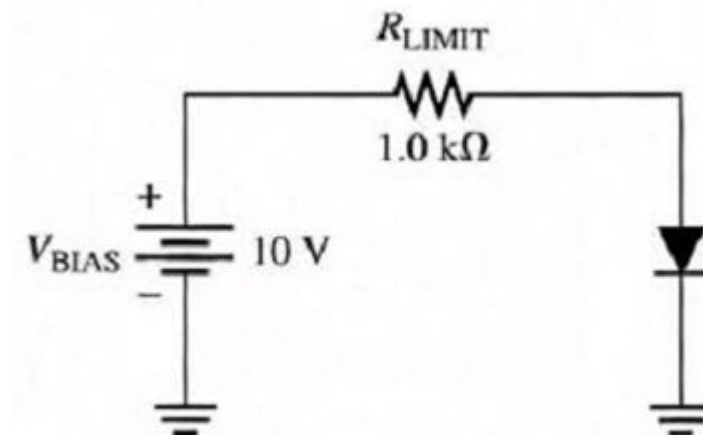

Solution 3

- Ideal diode model

$$V_F = 0V$$

$$I_F = \frac{V_{BIAS}}{R_{LIMIT}} = \frac{10V}{1k\Omega} = 10mA$$

$$V_{R_{LIMIT}} = I_F \cdot R_{LIMIT} = (10mA) \cdot (1k\Omega) = 10V$$

- Practical diode model

$$V_F = 0,7V$$

$$I_F = \frac{V_{BIAS} - V_F}{R_{LIMIT}} = \frac{10V - 0,7V}{1k\Omega} = 9,3mA$$

$$V_{R_{LIMIT}} = I_F \cdot R_{LIMIT} = (9,3mA) \cdot (1k\Omega) = 9,3V$$

- Complete diode model

$$I_F = \frac{V_{BIAS} - 0,7}{R_{LIMIT} + r'_d} = \frac{10V - 0,7V}{1k\Omega + 10\Omega} = \frac{9,3V}{1010\Omega} = 0,00921A = 9,21mA$$



$$V_F = 0,7V + r'_d \cdot I_F = 0,7V + (10\Omega) \cdot (9,21mA) = 792mV$$

$$V_{R_{LIMIT}} = I_F \cdot R_{LIMIT} = (9,21mA) \cdot (1k\Omega) = 9,21V$$

Load-Line Analysis


The load line plots all possible combinations of diode current (I_D) and voltage (V_D) for a given circuit. The maximum I_D equals E/R , and the maximum V_D equals E .

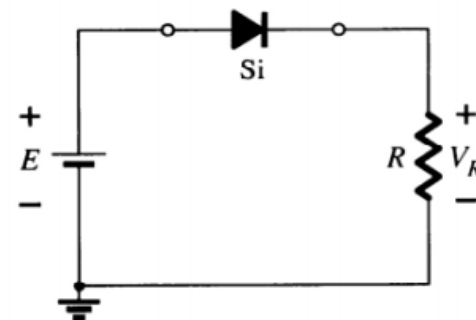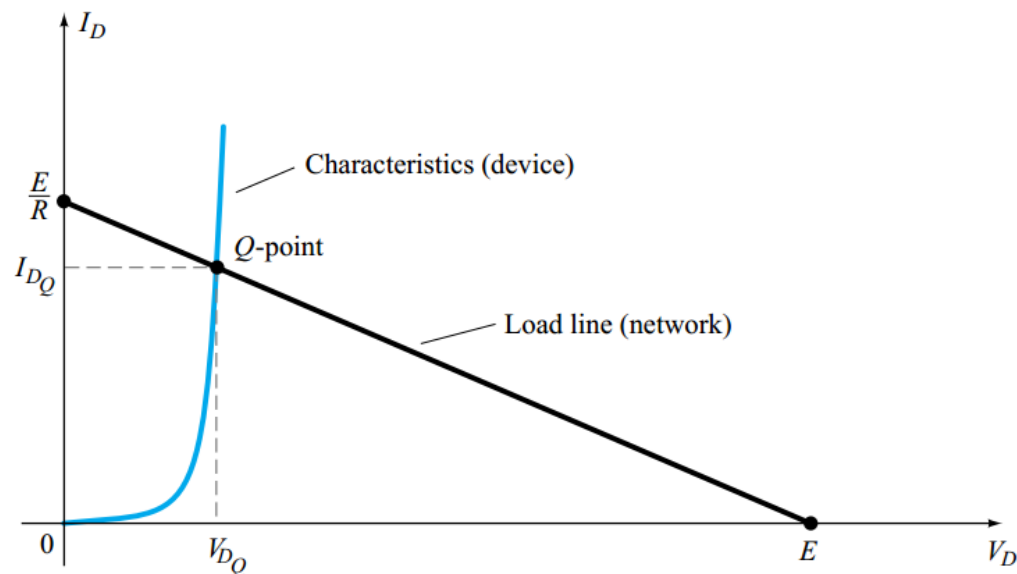The point where the load line and the characteristic curve intersect is the Q-point, which identifies I_D and V_D for a particular diode in a given circuit.




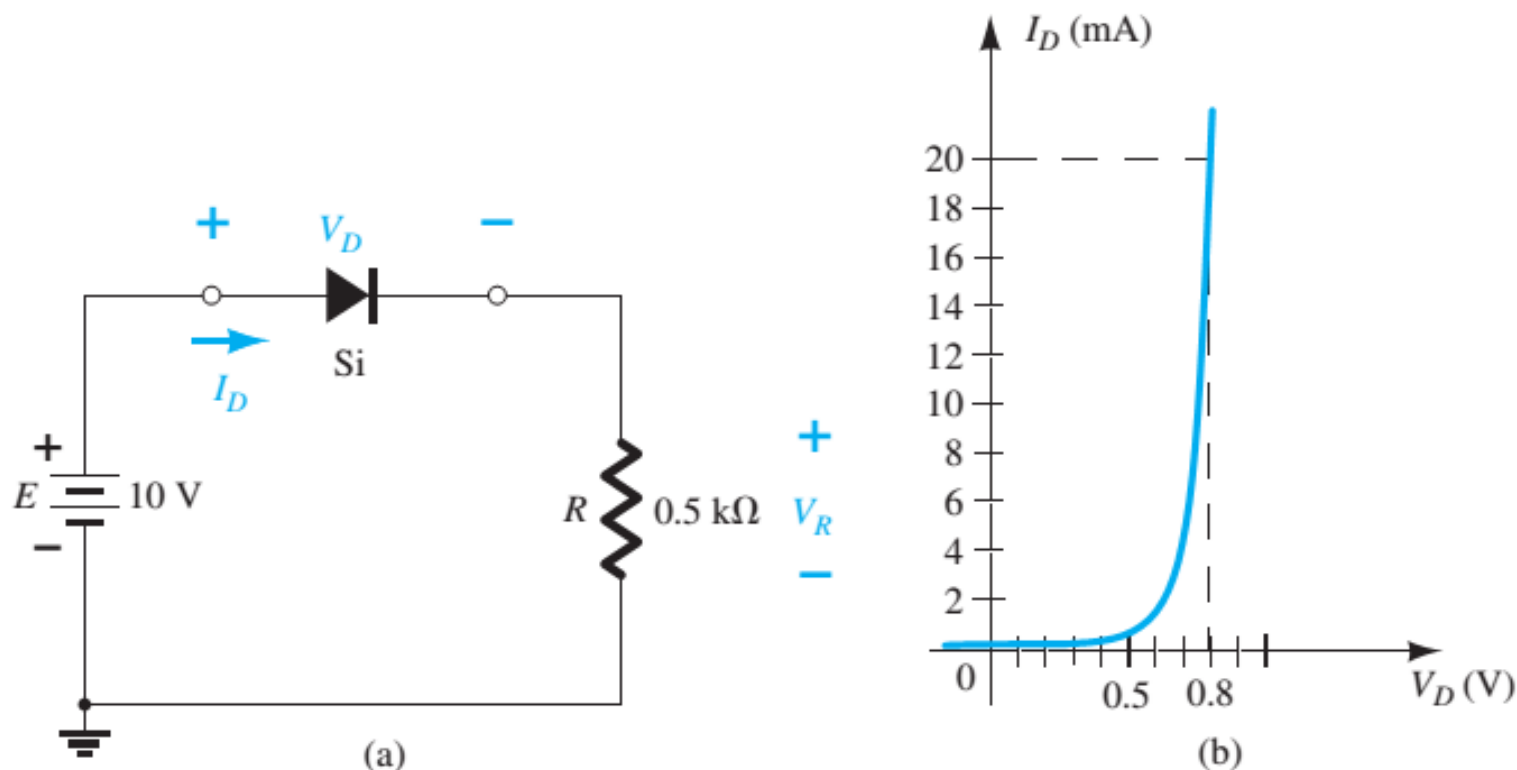Exercise

- Determine V_D , I_D and V_R based on the characteristic of the diode given in the following figure.




Solution

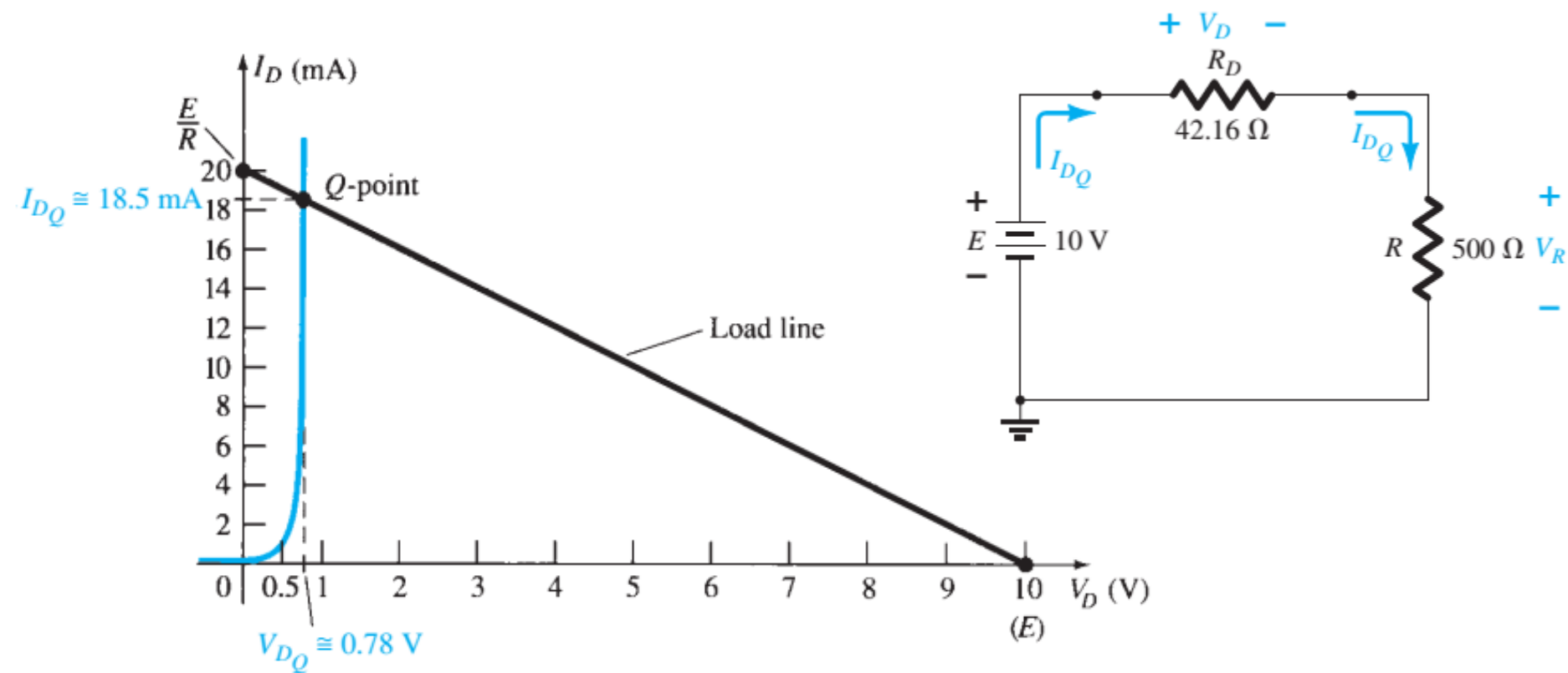

$$V_R = E - V_D = 10 \text{ V} - 0.78 \text{ V} = 9.22 \text{ V}$$




Diode Symbol and Packaging

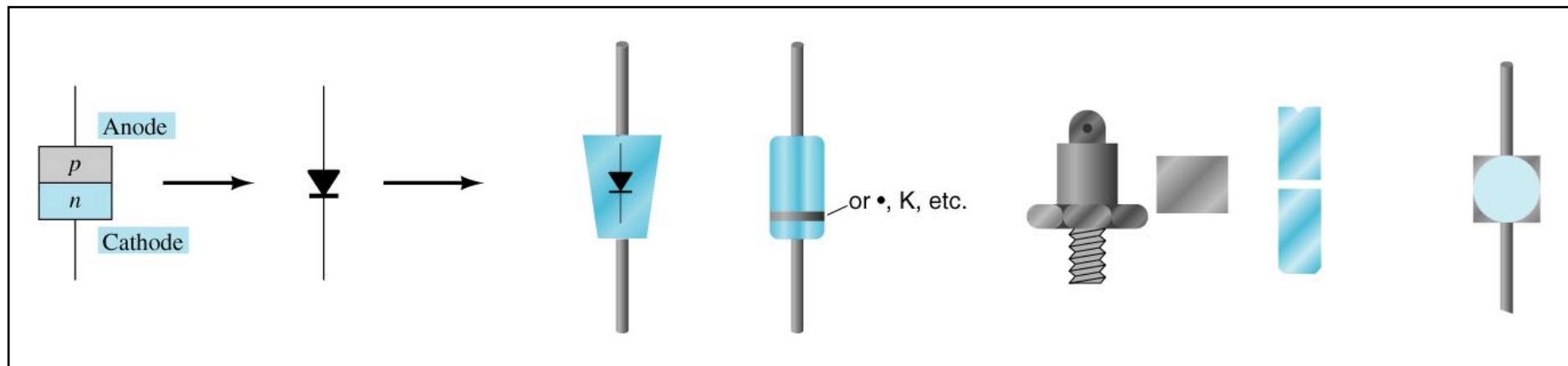- The anode is abbreviated A
- The cathode is abbreviated K




Diode Testing

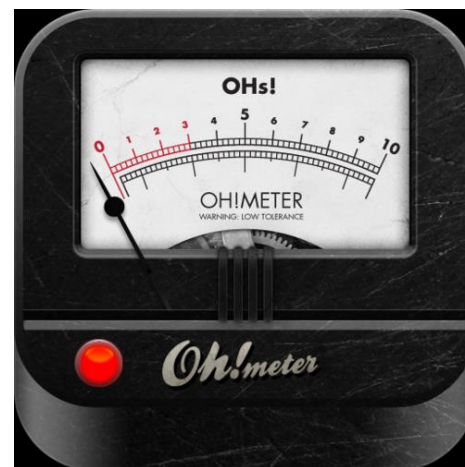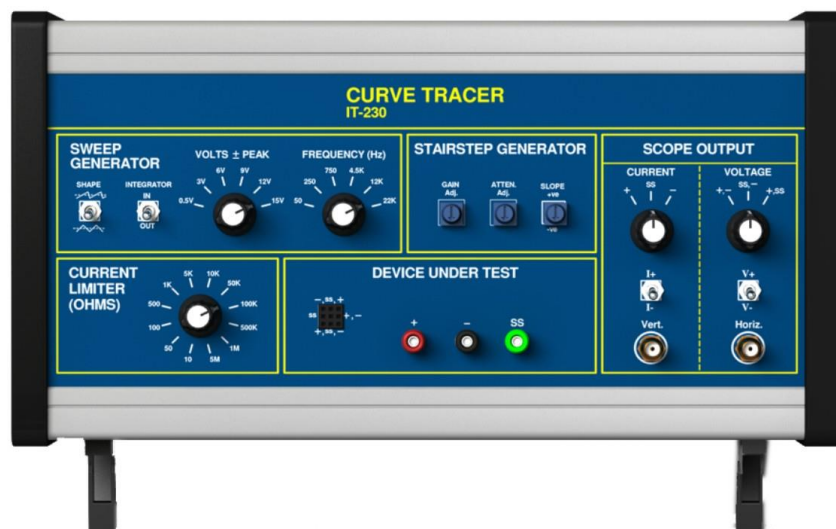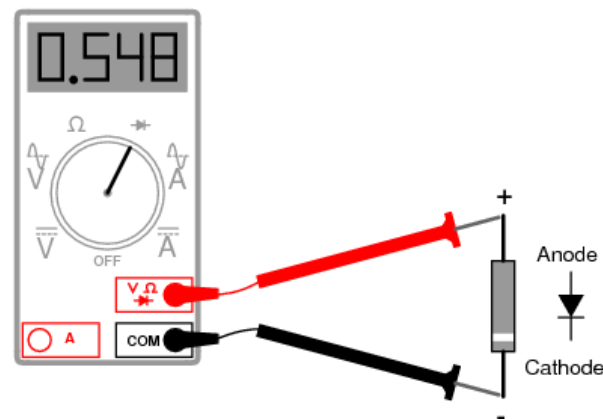- Diodes are commonly tested using one of these types of equipment:
 - Diode checker
 - Ohmmeter
 - Curve tracer




Ohmmeter

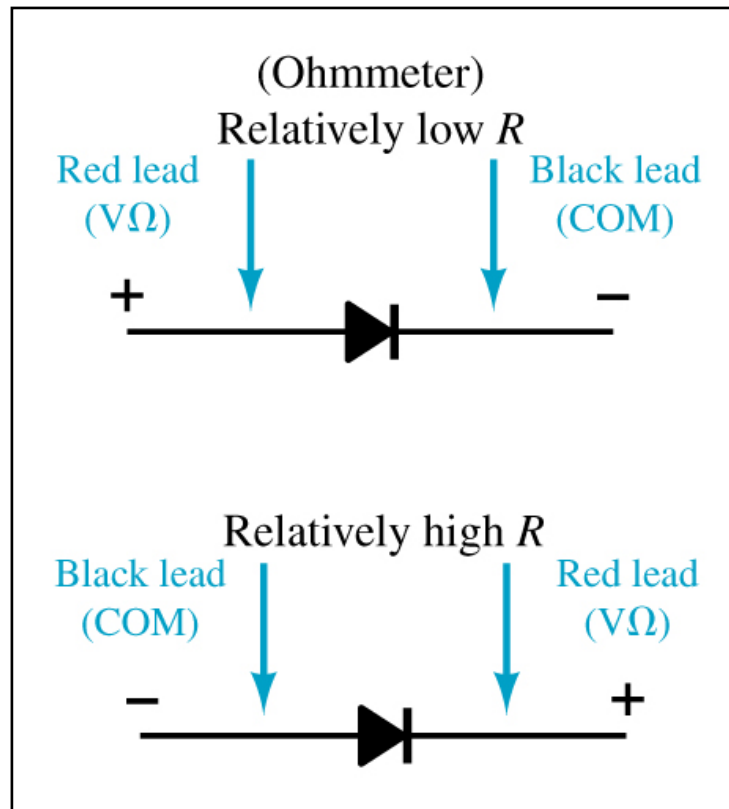- An ohmmeter set on a low Ohms scale can be used to test a diode. The diode should be tested out of circuit.




Diode Checker

- Many digital multimeters have a diode checking function. The diode should be tested out of circuit.
- A normal diode exhibits its forward voltage:
 - Gallium arsenide $\approx 1.2\text{ V}$
 - Silicon diode $\approx 0.7\text{ V}$
 - Germanium diode $\approx 0.3\text{ V}$

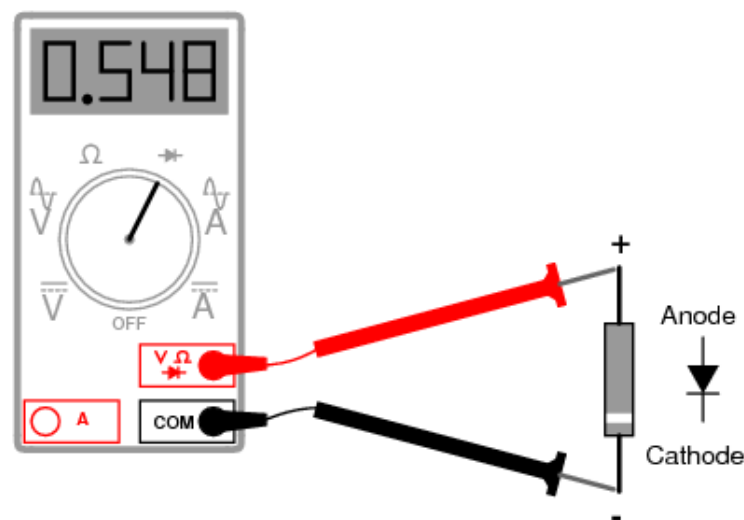


Exercise 2

- Determine
 - I_1 , I_{D1} , I_{D2}

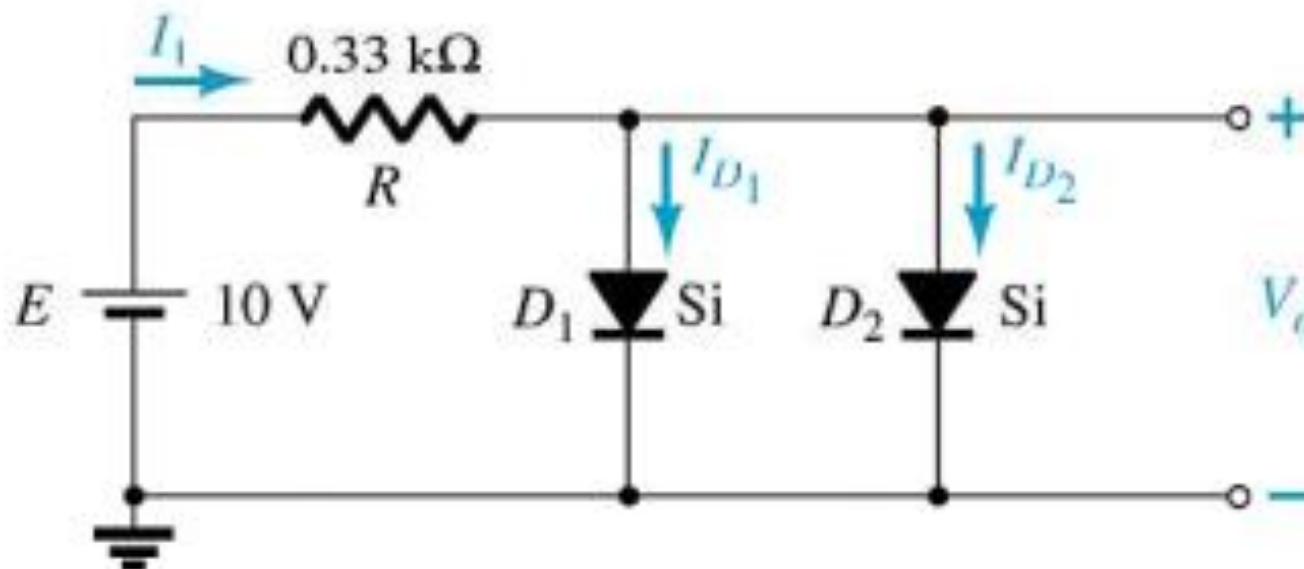



Curve Tracer

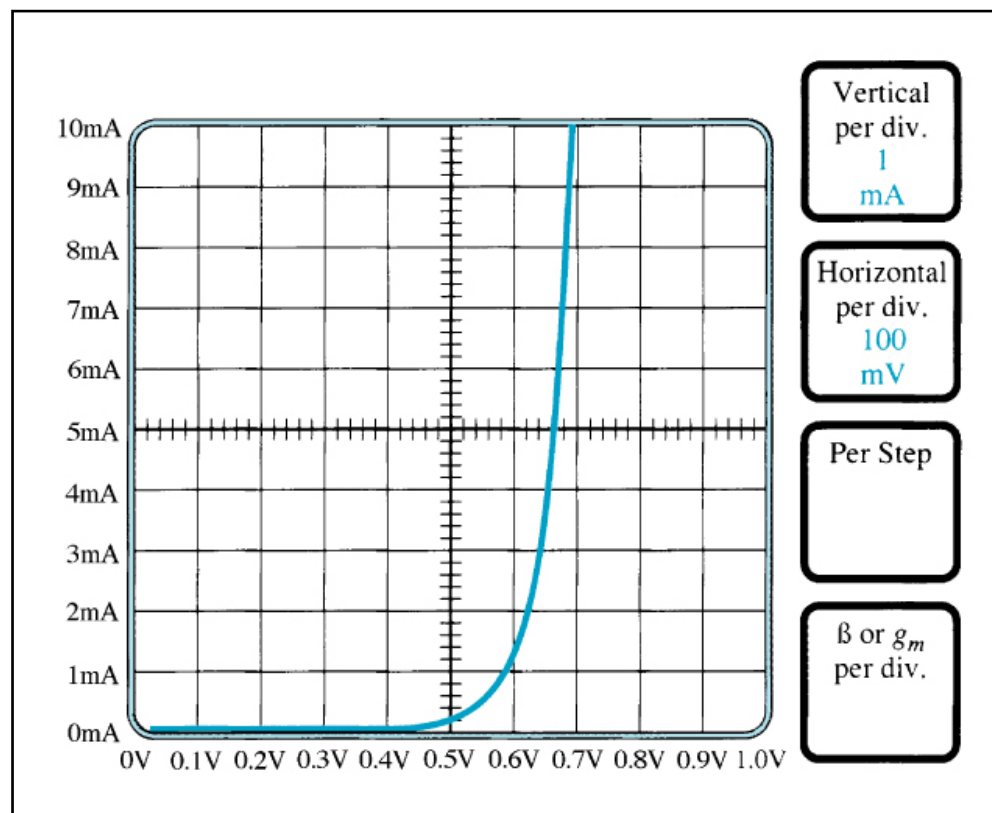- A curve tracer displays the characteristic curve of a diode in the test circuit. This curve can be compared to the specifications of the diode from a data sheet.




Other Types of Diodes

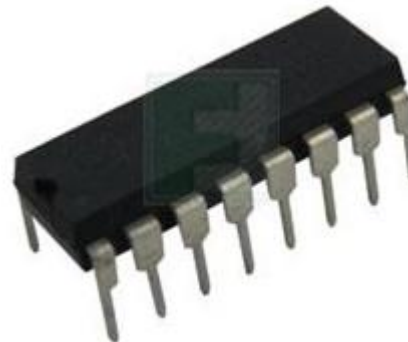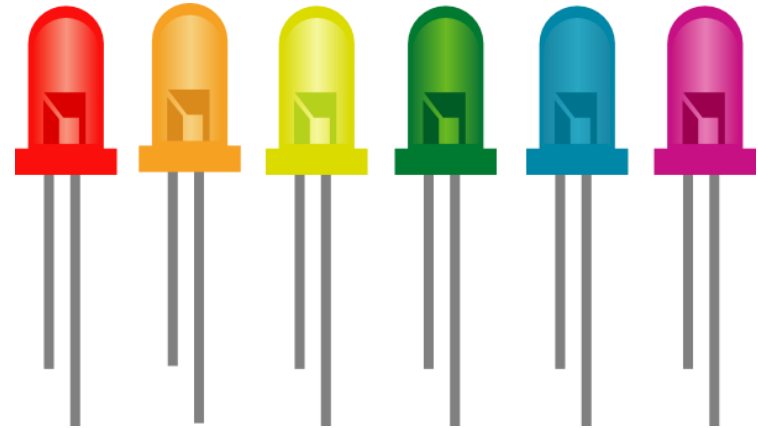- There are several types of diodes besides the standard $p-n$ junction diode. Three of the more common are:
 - Zener diodes
 - Light-emitting diodes
 - Diode arrays





Zener Diode

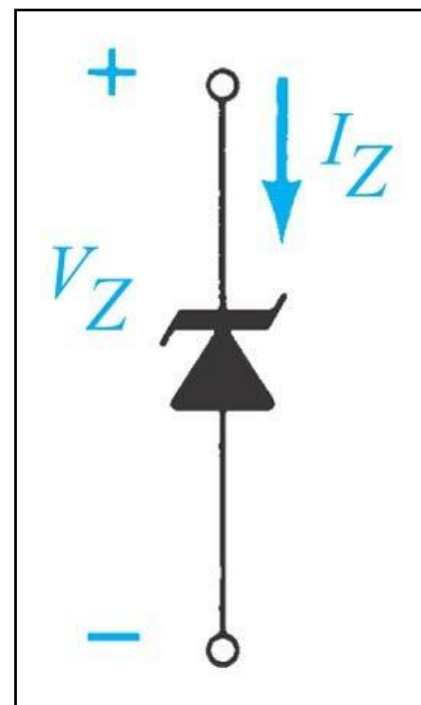- A **Zener diode** is one that is designed to safely operate in its zener region; i.e., biased at the Zener voltage (V_Z).
- Common zener diode voltage ratings are between 1.8 V and 200 V




Light-Emitting Diode (LED)

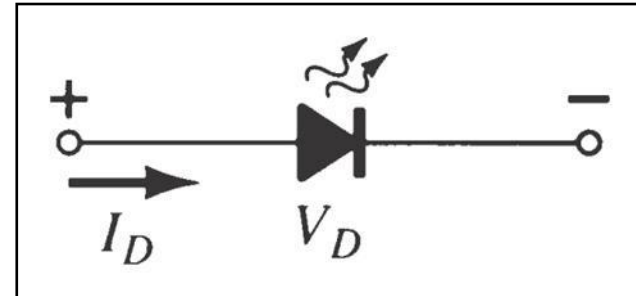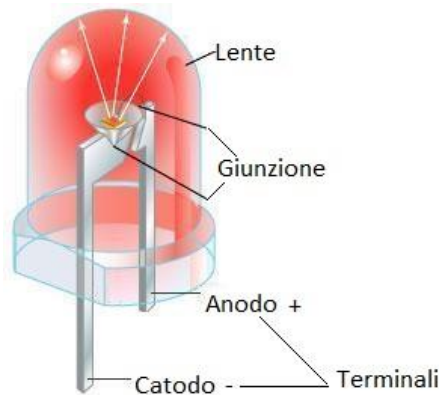- An **LED** emits light when it is forward biased, which can be in the infrared or visible spectrum.
- The forward bias voltage is usually in the range of 2 V to 3 V.




Diode Arrays

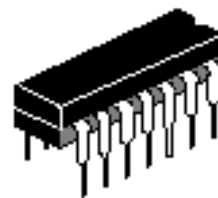- Multiple diodes can be packaged together in an integrated circuit (IC).




- A variety of diode configurations are available.



Common Anode

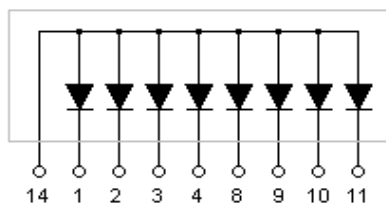


Common Cathode

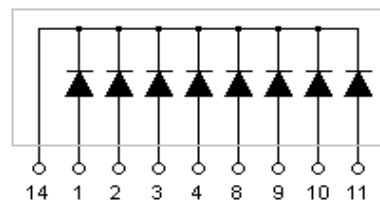

DC Adapter Circuits

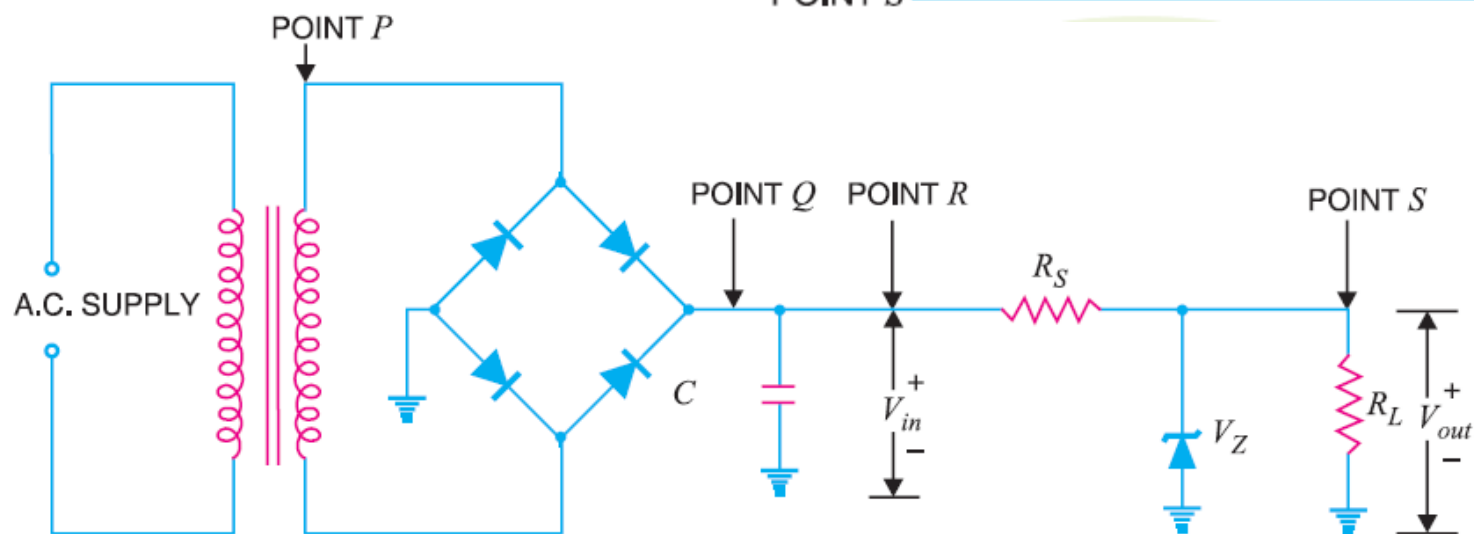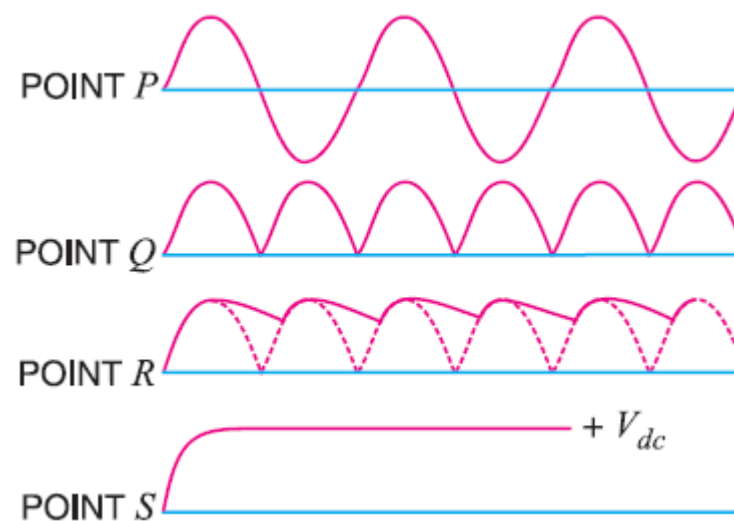

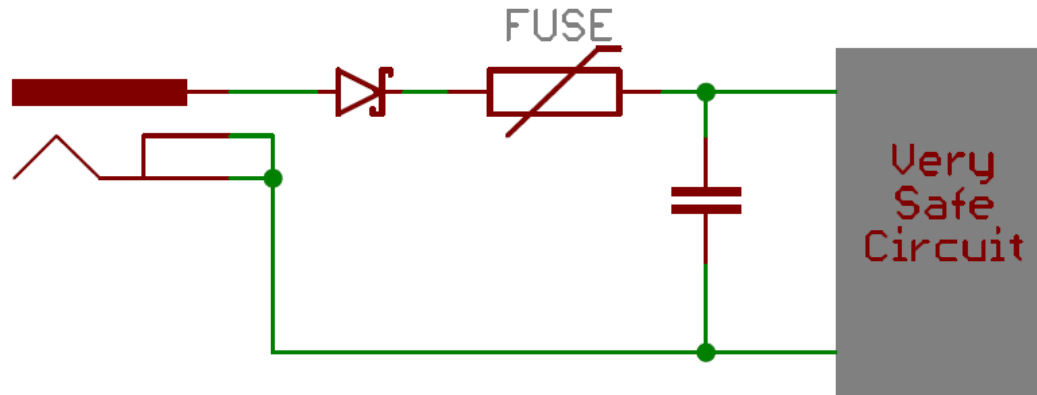
Diode Application - Reverse Current Protection



- **Mandatory design** for any system
 - Drawback: around 0.7V loss because of the forward voltage drop.
- ☐ **Schottky diodes** an excellent choice for reverse protection diodes.


Diode Application – Reverse Current Protection

- SIM800L: 4.3V

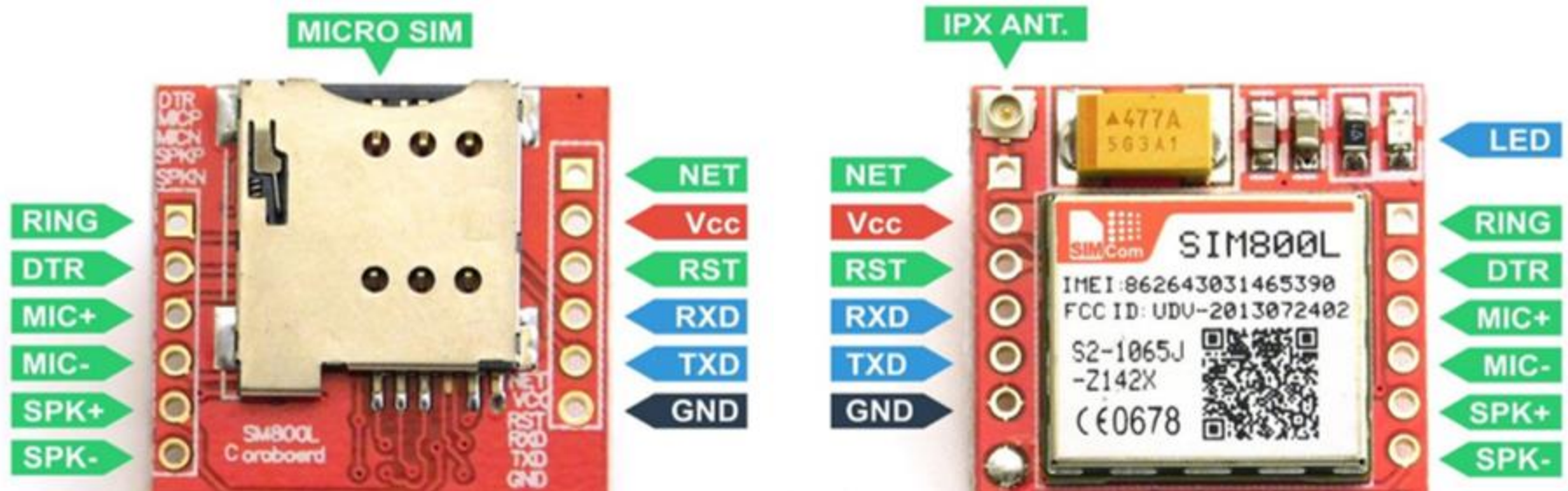


Diode and Its Application

- Half-wave Rectification



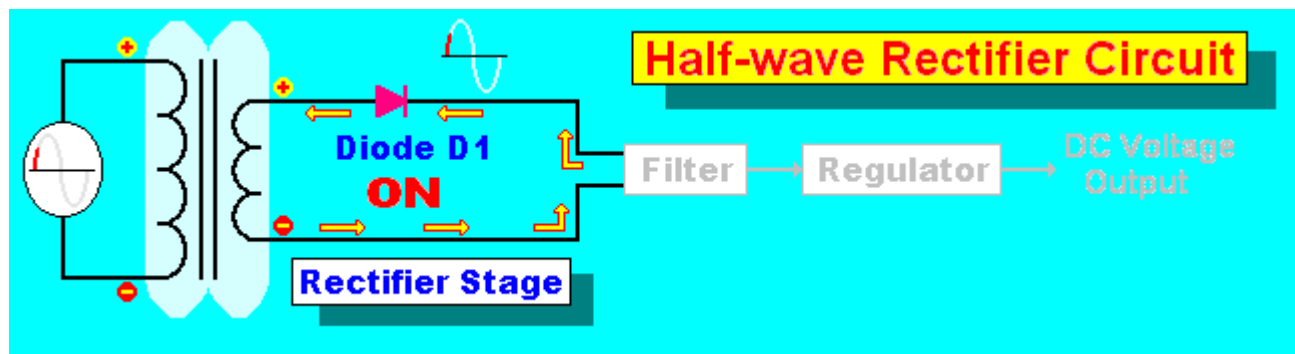


- Full-wave Rectification








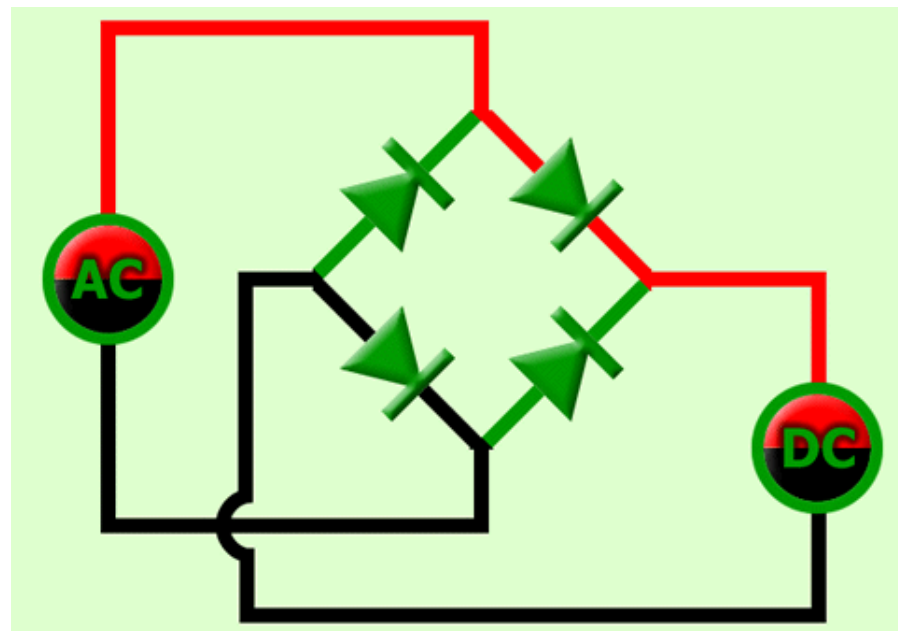


Half-Wave Rectification

- Convert AC to DC using one Diode

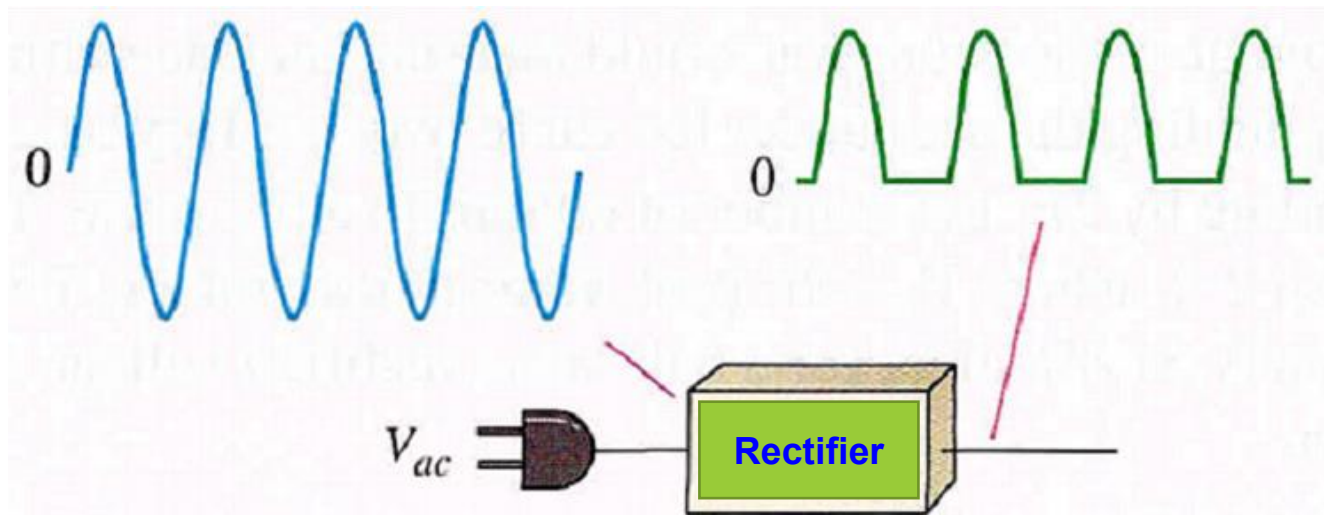
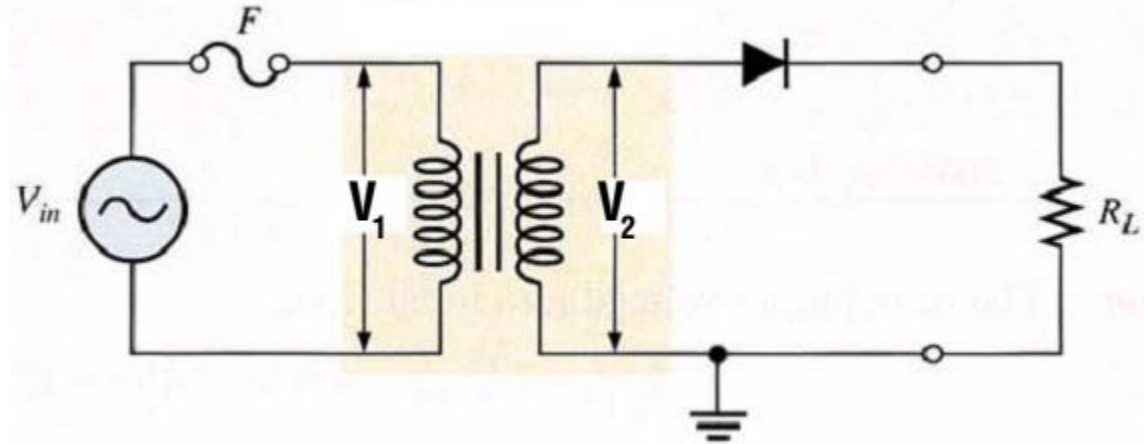
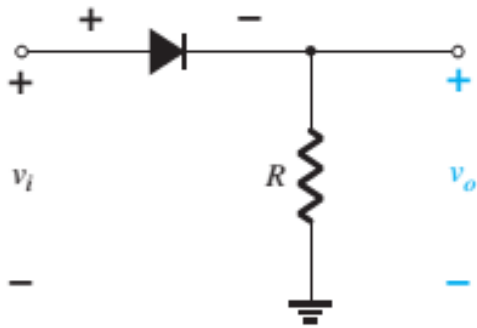


Half-Wave Rectification (cont.)

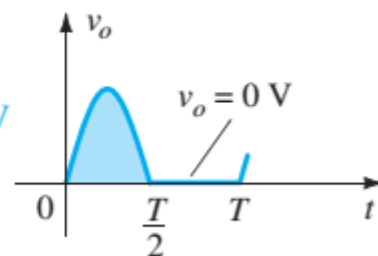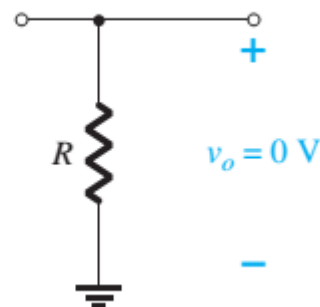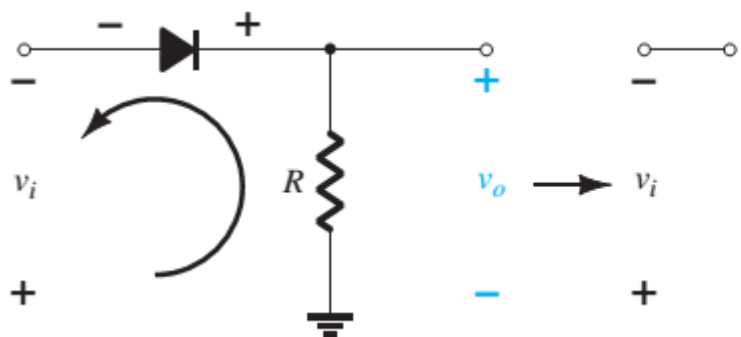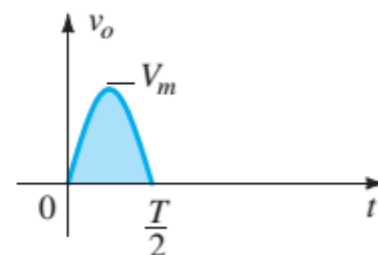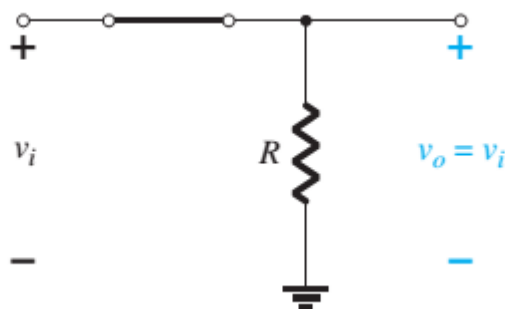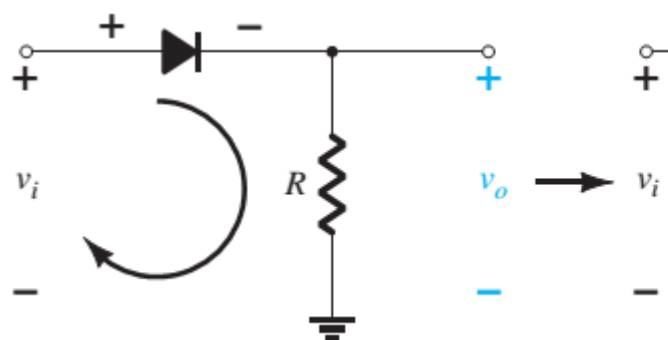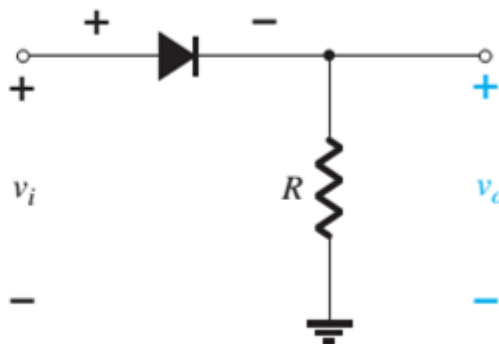
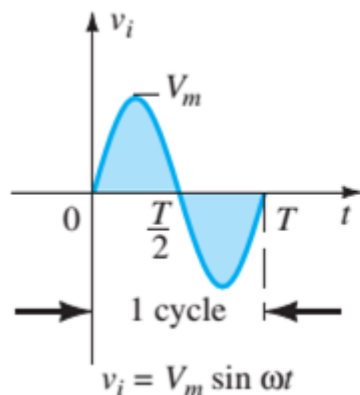


Full-Wave Rectification

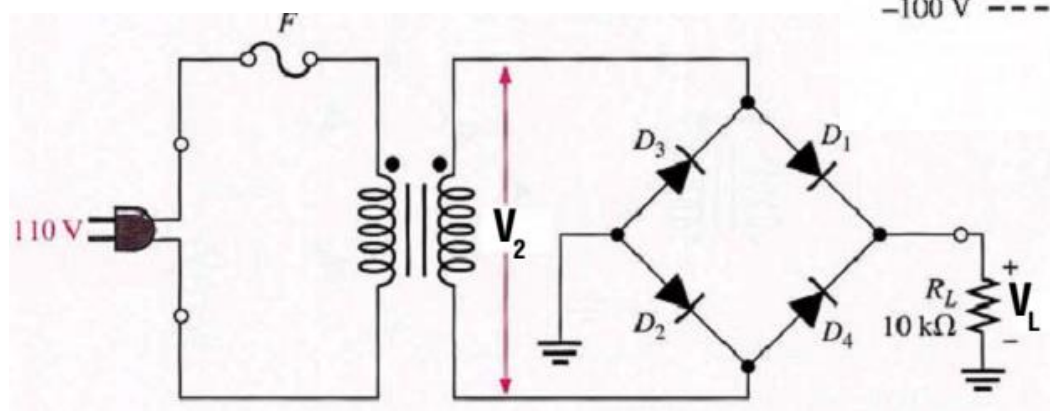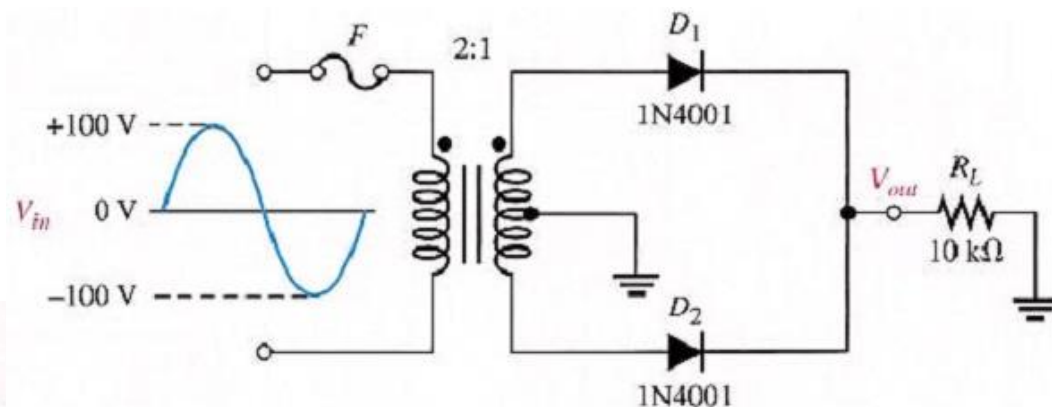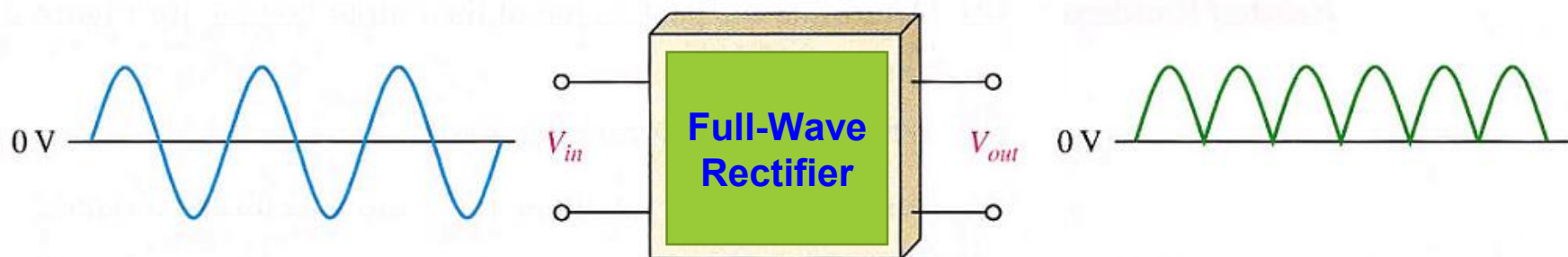
- Convert AC to DC using two or four diodes




Bridge Rectifier

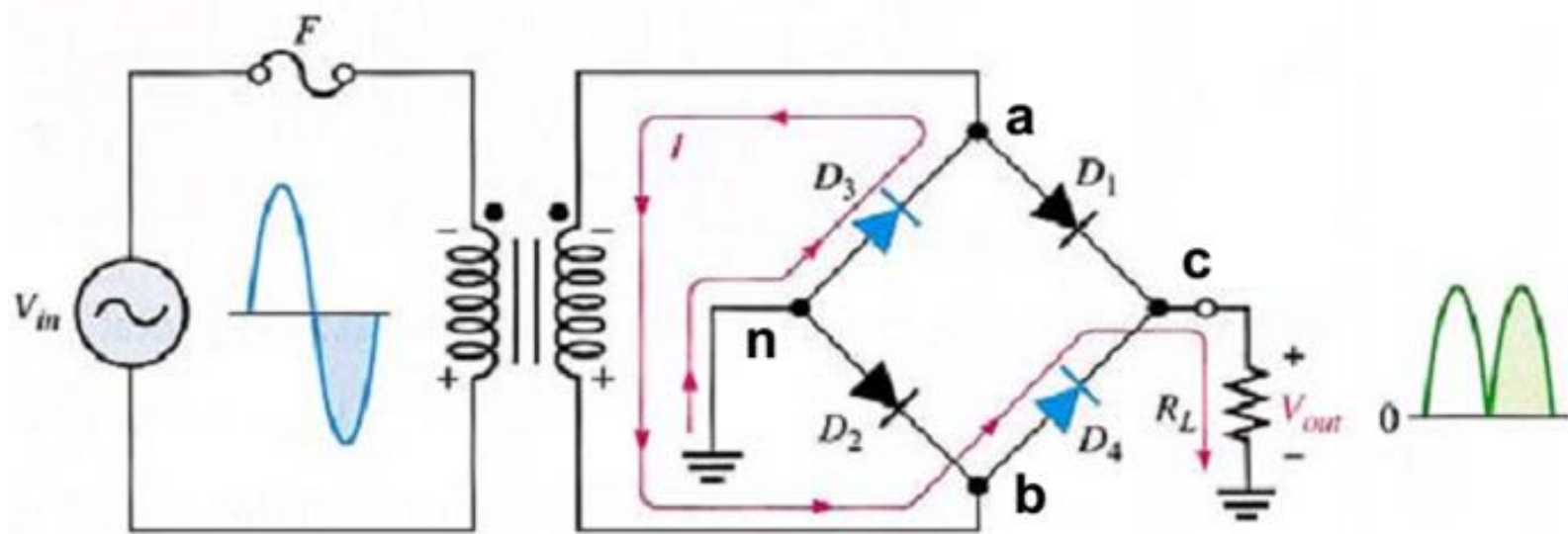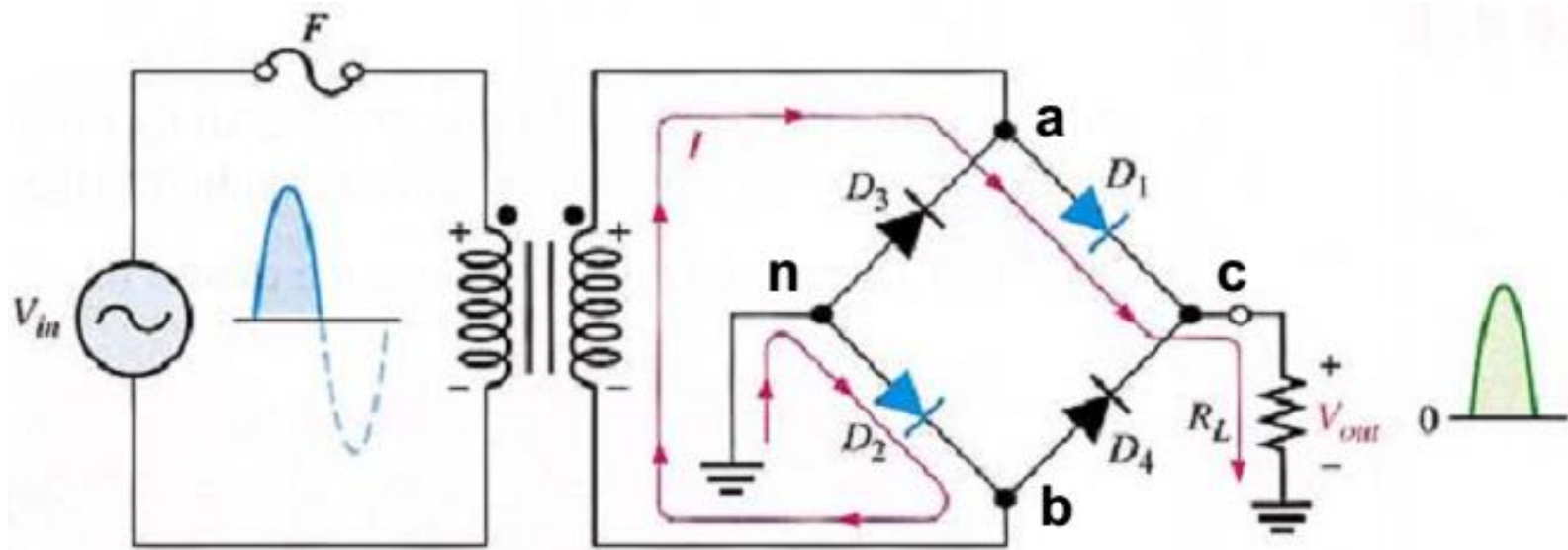

Ripple in Rectification


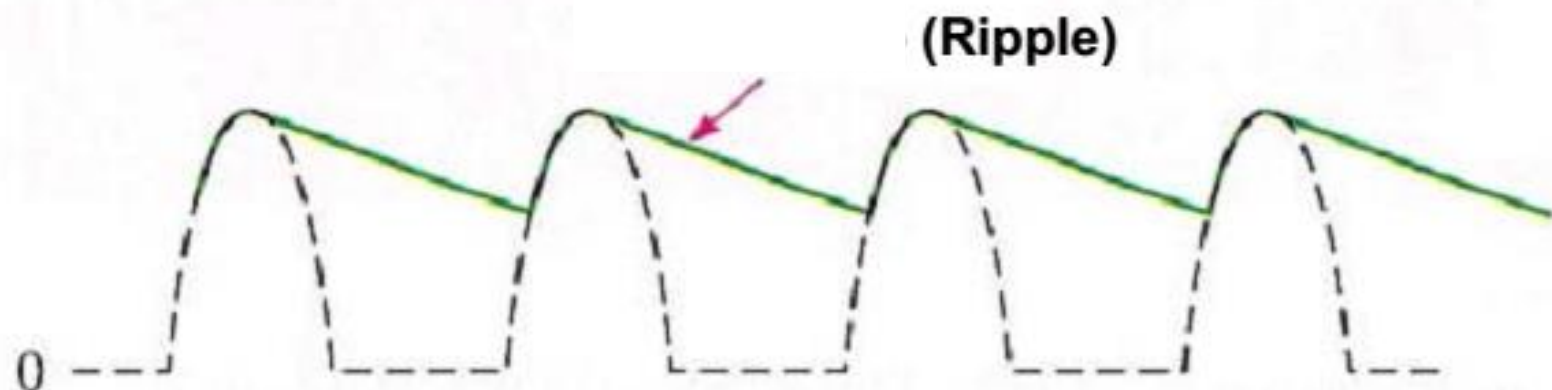


(a) Half-wave

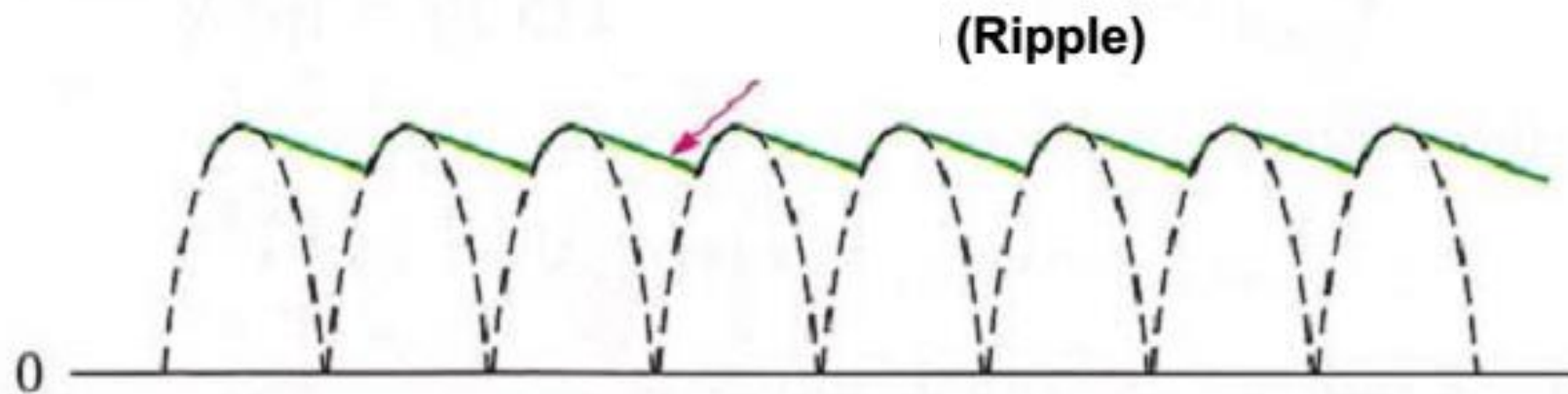


(b) Full-wave


Diode Application - AC to DC Converter

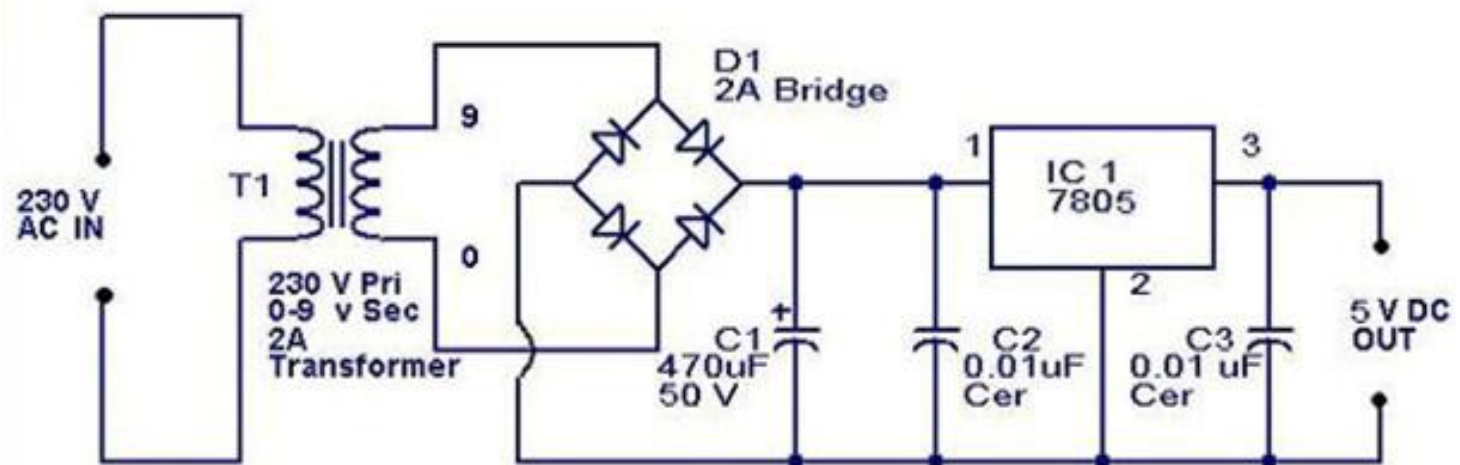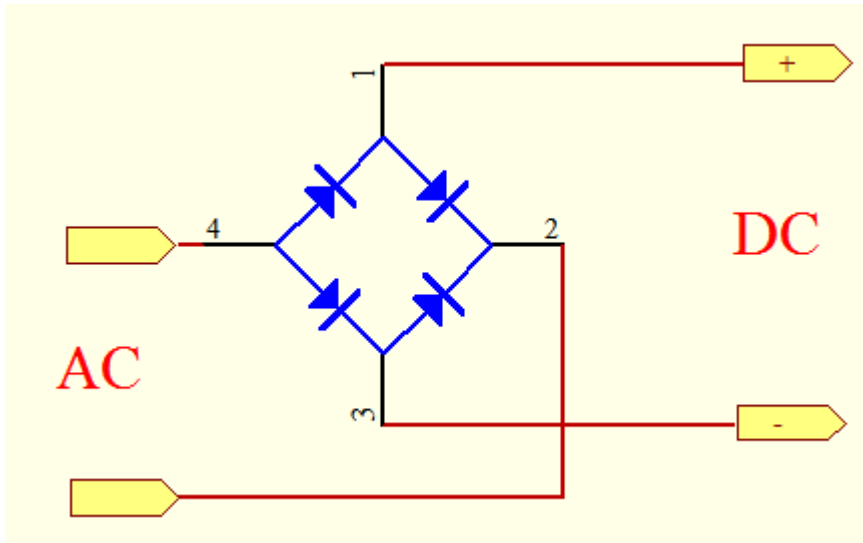


Complete AC/DC Power Circuit

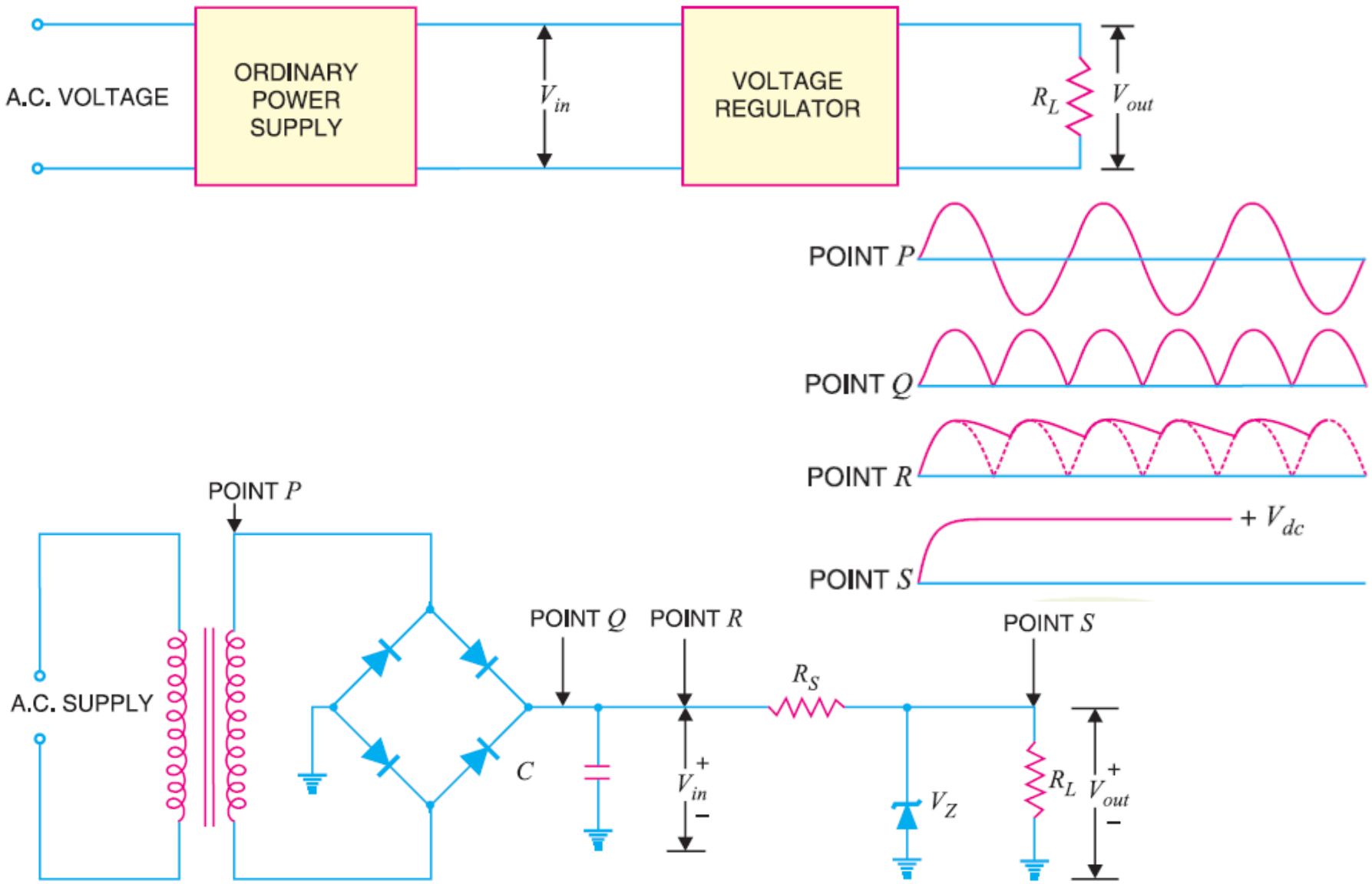

Logic Gates

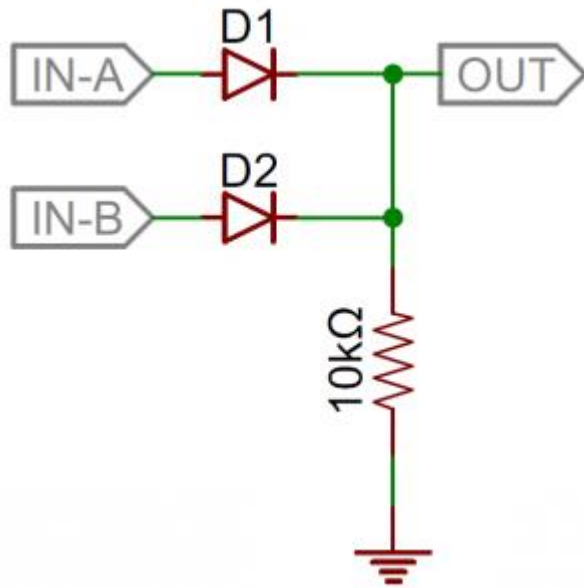


■ OR

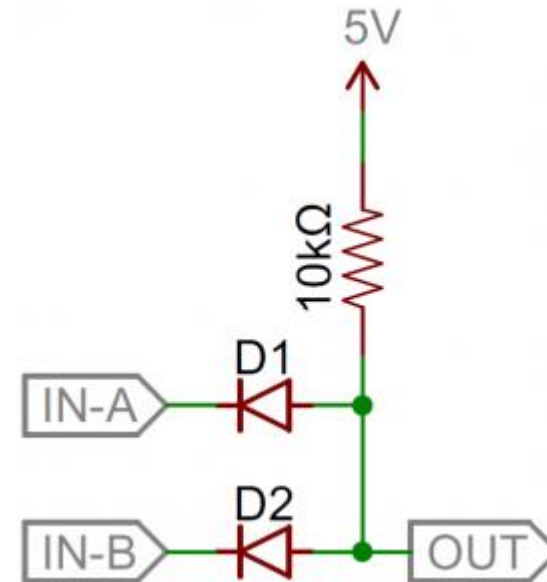


■ AND

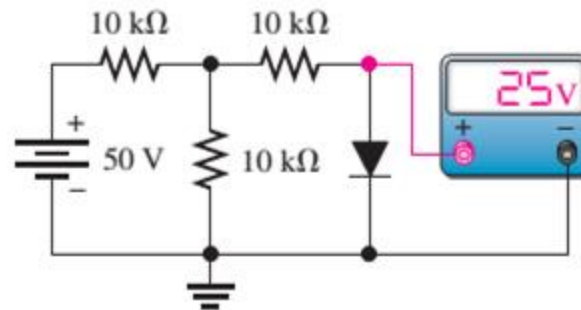Exercise 5


- Analyze and validate the value of the voltmeter in case of using ideal diode model ?




(a)

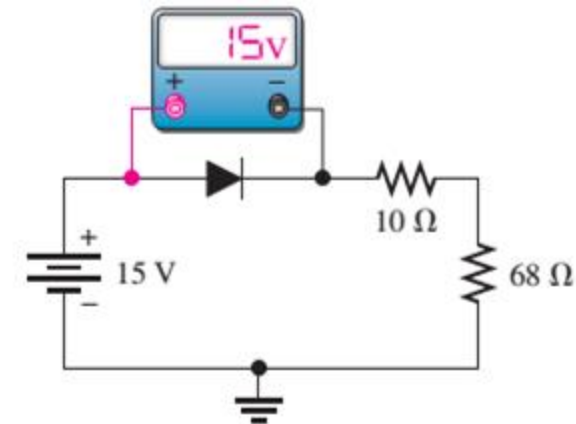

(b)

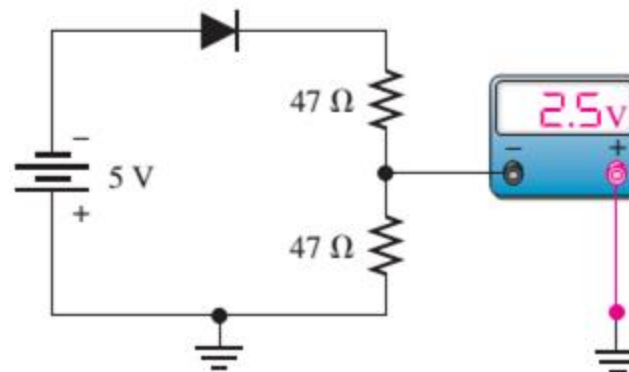

(c)

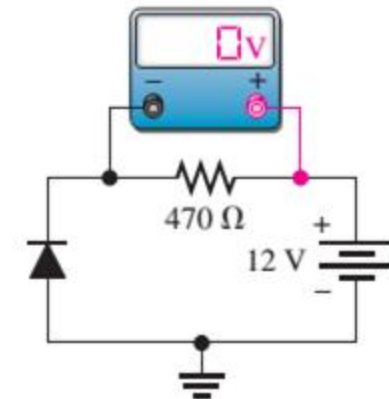

(d)

