

C02015


Exercise – BJT

- When a transistor is used as a switch, it is stable in which two distinct regions?
 - saturation and active
 - active and cutoff
 - saturation and cutoff
 - none of the above


- For a silicon transistor, when a base-emitter junction is forward-biased, it has a nominal voltage drop of
 - 0.7
 - 0.3
 - 0.2
 - V_{CC}

- A certain BJT has $I_B = 167\mu\text{A}$, $I_C = 15\text{mA}$, the amplifier DC factor is:
 - 15
 - 167
 - 90
 - All are not correct

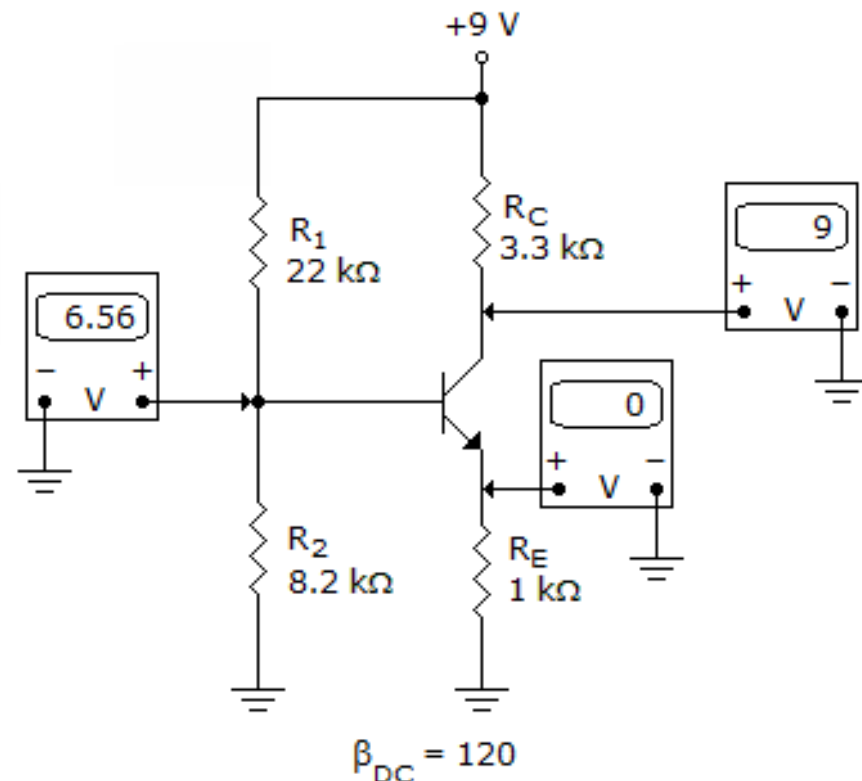
- Refer to the given figure. The most probable cause of trouble, if any, from these voltage measurements is



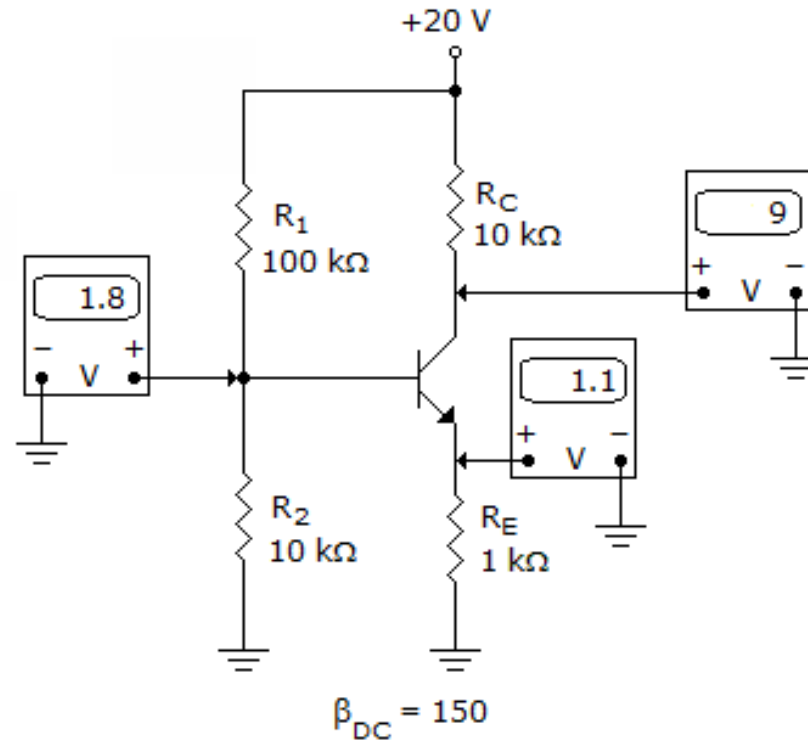
- Refer to the given figure. The most probable cause of trouble, if any, from these voltage measurements is



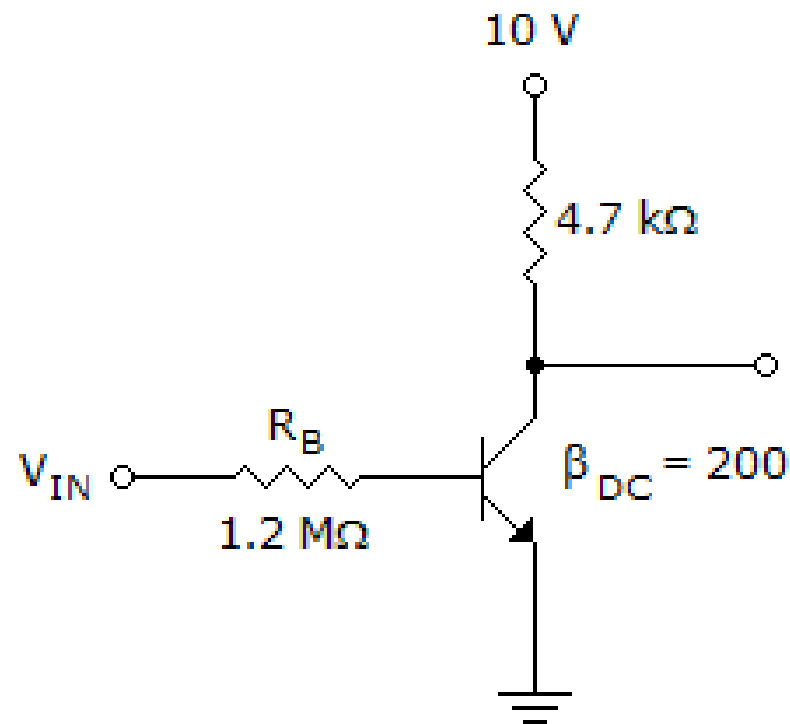
- Refer to this figure. If $V_{CE} = 0.2 \text{ V}$, $I_{C(\text{sat})}$ is



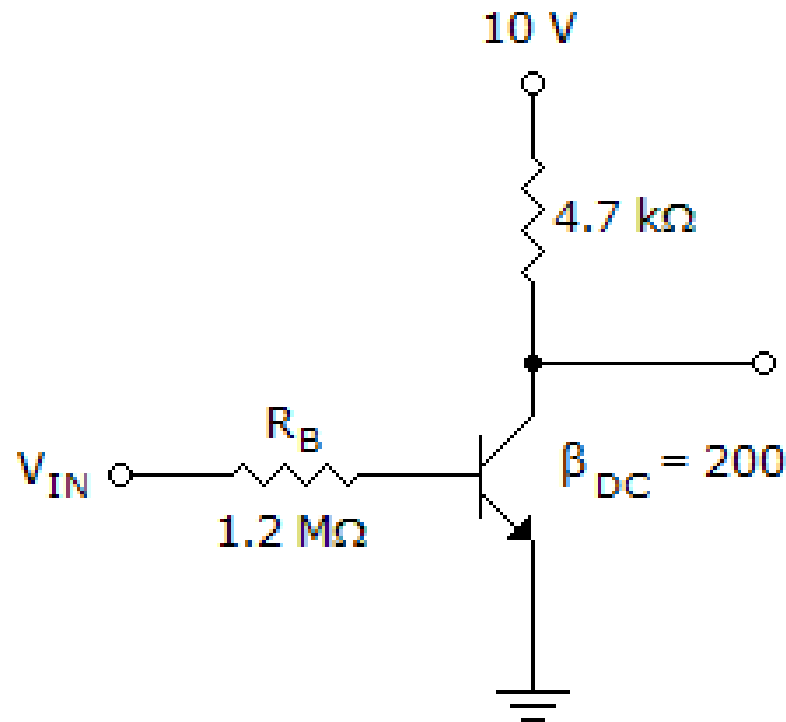- Refer to this figure. Determine the minimum value of I_B that will produce saturation ($V_{CE}(\text{sat}) = 0.2\text{V}$).



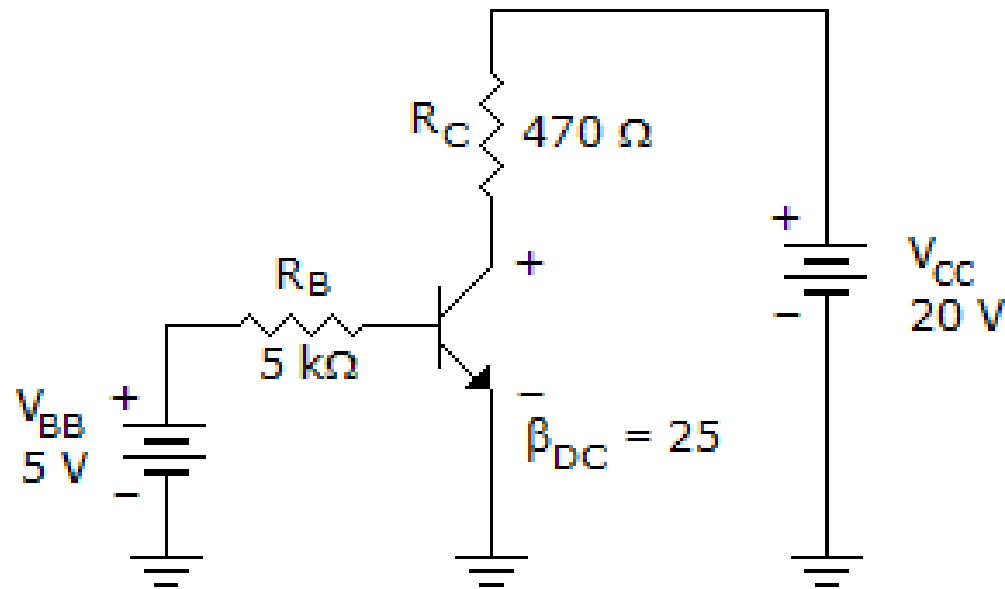
- Refer to this figure. The value of V_{BC} is



C02015

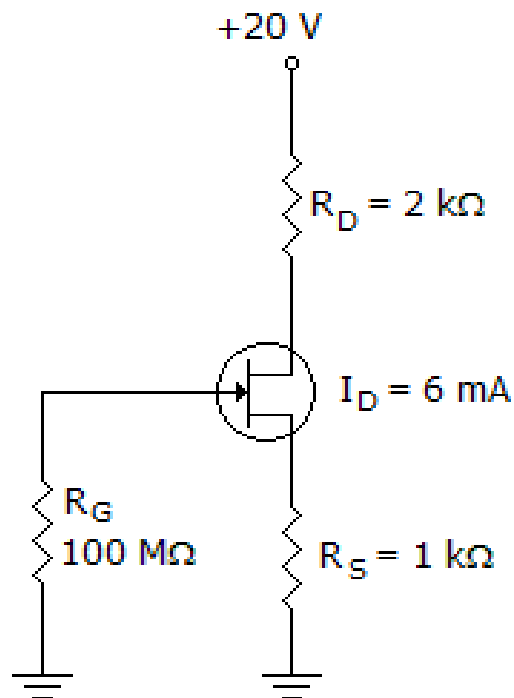Exercise – FET


- Refer to the given figure. Calculate the value of V_{DS}



Answer

- 2V

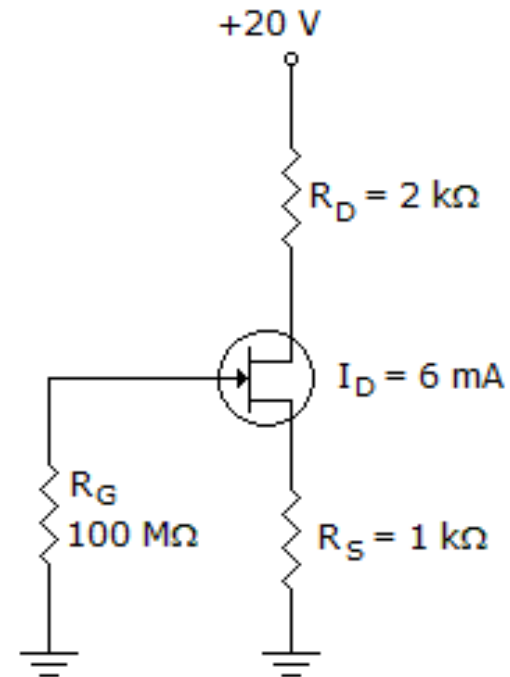
- Refer to figure shown below. Determine the value of V_S .



Answer

- 6V

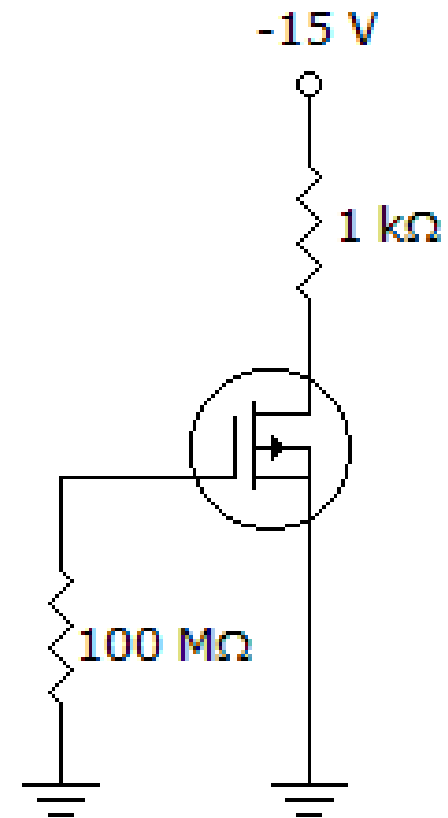
- Refer to the given figure. $I_D = 6 \text{ mA}$.
Calculate the value of V_{DS}



- -9V

- In general $V_{DS} = V_{DD} - (I_D * R_D)$
But in figure direction of FET transistor is out of drain so,
 I_D becomes negative .

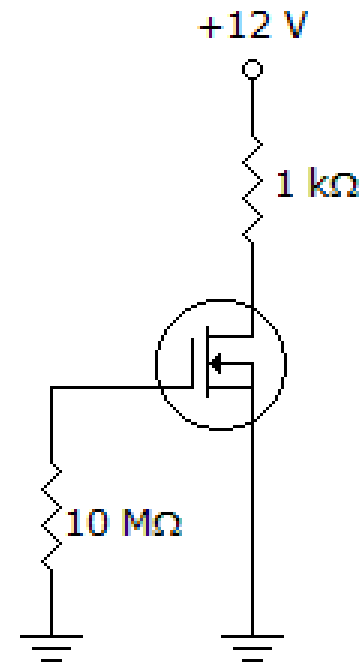
- Refer to the given figure. $I_D = 6 \text{ mA}$. Calculate the value of V_{DS}



Answer

- 6V

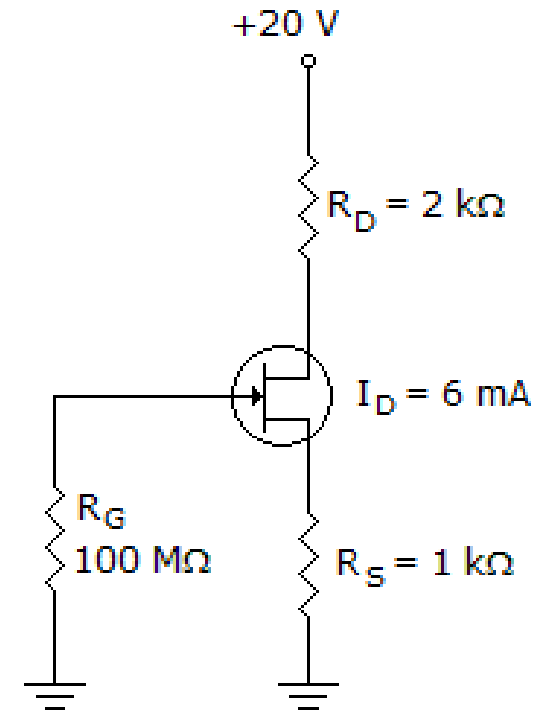
- Refer to figure given below. Determine the value of V_{GS}



Answer

- -6V

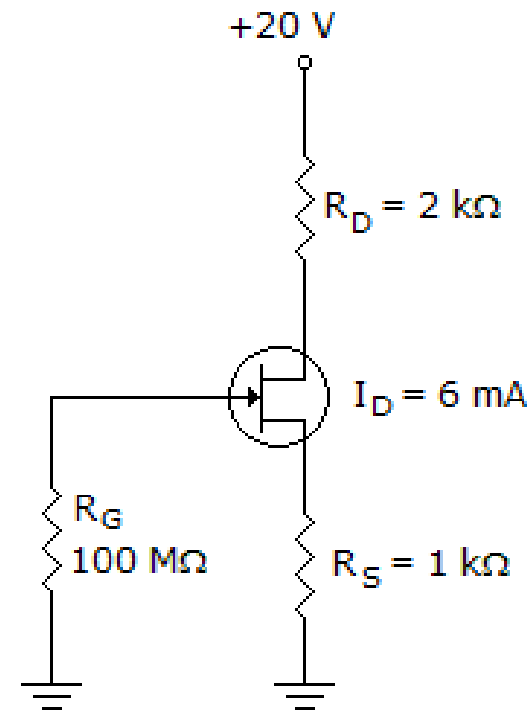- Refer to figure show below. Calculate the value of V_D





Answer

- 8V

- For a JFET, the value of V_{DS} at which I_D becomes essentially constant is the
 - pinch-off voltage.
 - cutoff voltage.
 - breakdown voltage.
 - ohmic voltage.

Answer: A

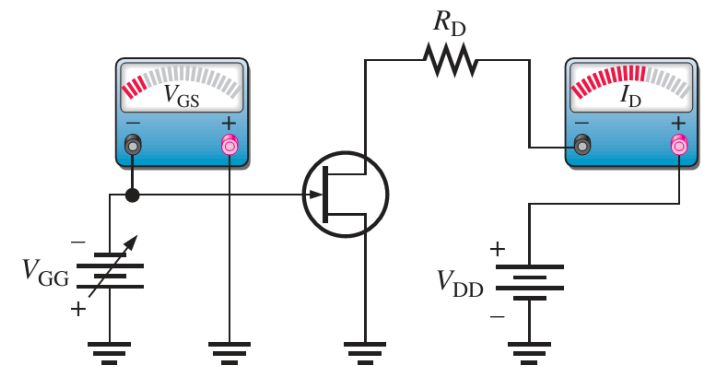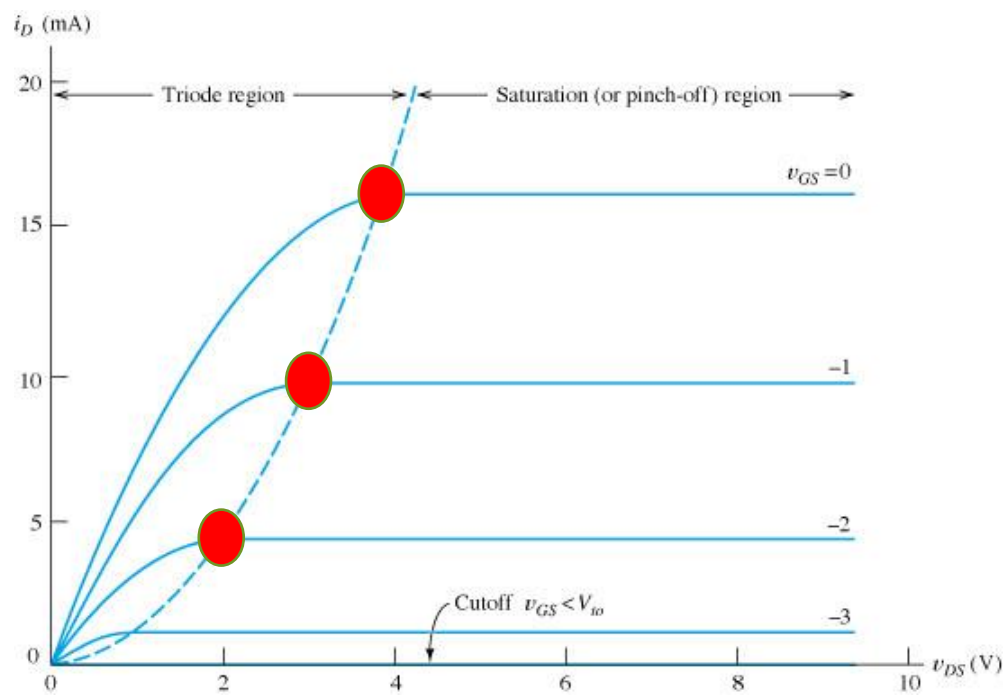



- The value of V_{GS} that makes I_D approximately zero is the
 - Pinch-off voltage
 - Cut-off voltage
 - Breakdown voltage

Answer

- B

- The _____ has a physical channel between the drain and source.
 - DFET
 - EFET
 - VFET


Answer: A

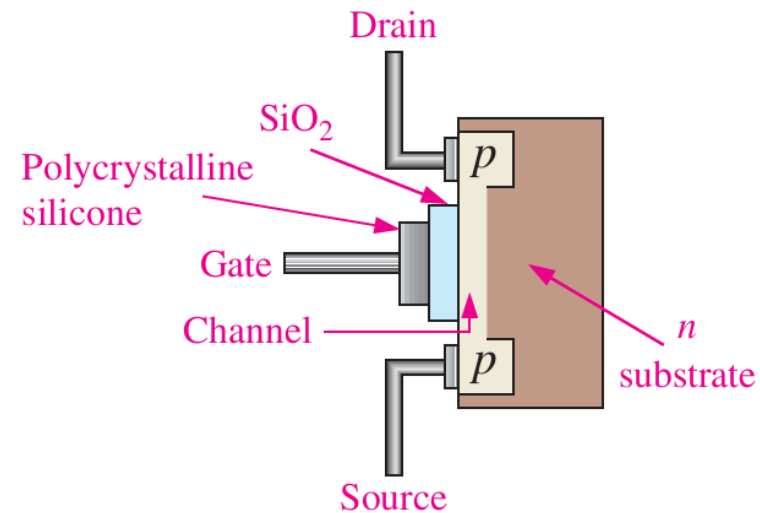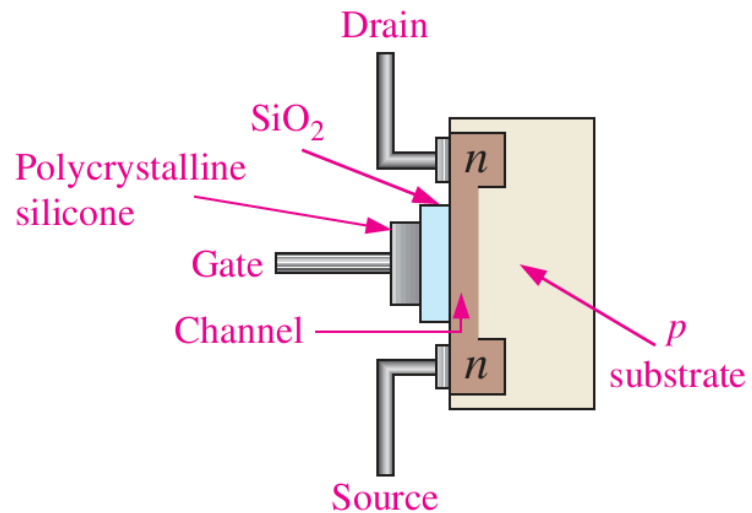

- What type(s) of gate-to-source voltage(s) can a depletion MOSFET (D-MOSFET) operate with?
 - Zero
 - Positive
 - Negative
 - All of them

- Midpoint bias for a D-MOSFET is $I_D = \underline{\hspace{2cm}}$, obtained by setting $V_{GS} = 0$
 - $I_{DSS} / 2$
 - $I_{DSS} / 3.4$
 - I_{DSS}


- Identify D-FET p channel

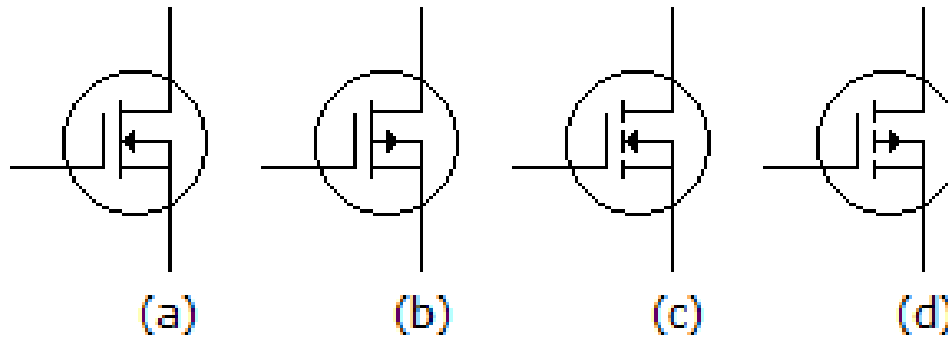

Answer

- B

- Determine V_{GS} and I_D

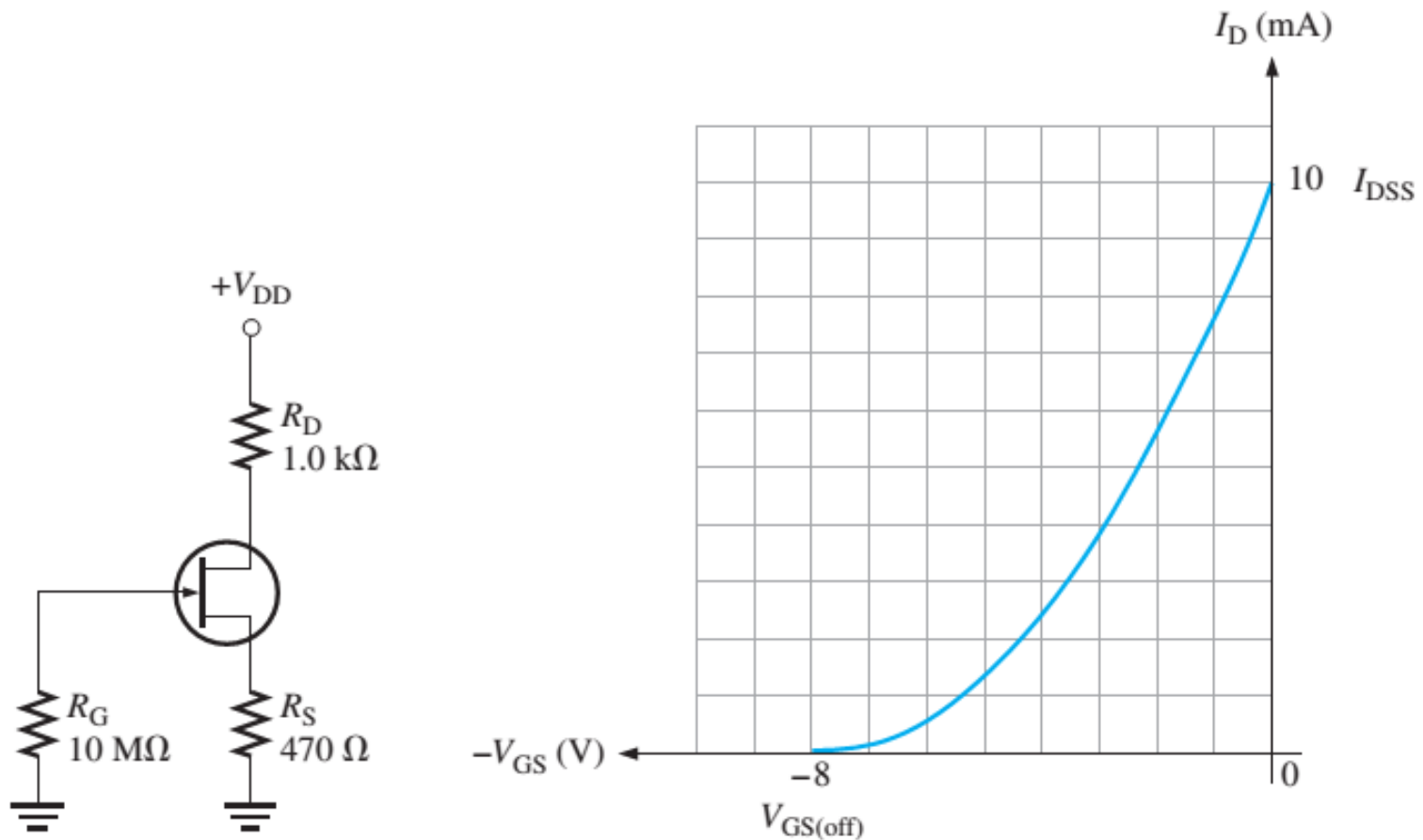

Answer

■ Determine the Load line

■ $I_D = 0$

$$V_{GS} = -I_D R_S = (0)(470 \Omega) = 0 \text{ V}$$



■ $I_D = I_{DSS}$

$$V_{GS} = -I_D R_S = -(10 \text{ mA})(470 \Omega) = -4.7 \text{ V}$$


■ Q is the intersection point of the load line & transfer curve.

• $I_D = 5.07 \text{ mA}$

• $V_{GS} = -2.3 \text{ V}$

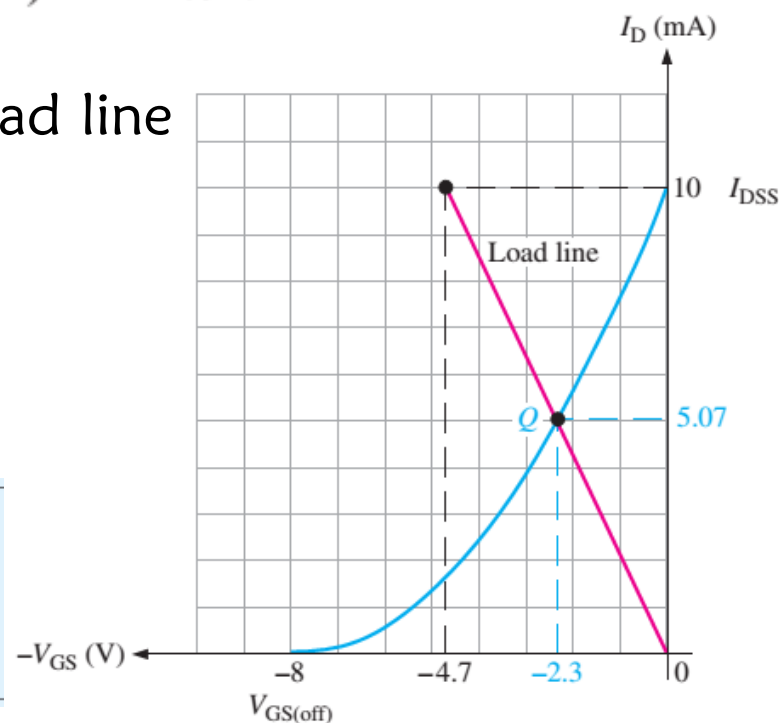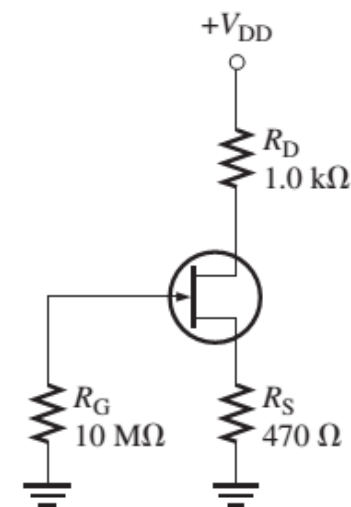



JFET
Self-bias

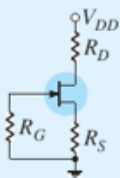

$$V_{GS} = -I_D R_S$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

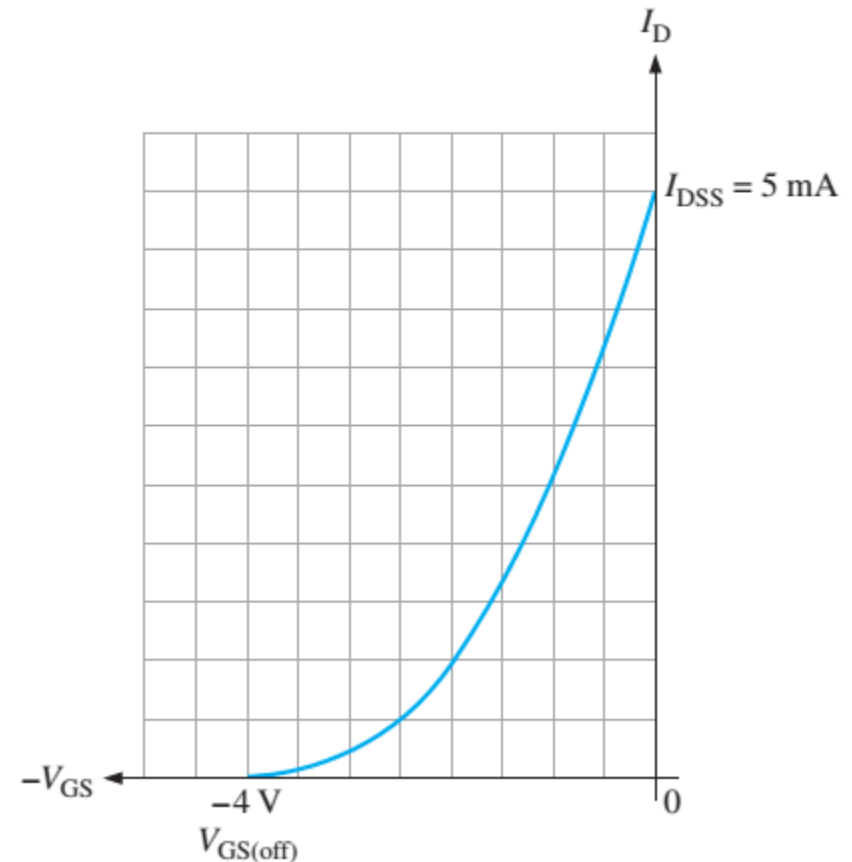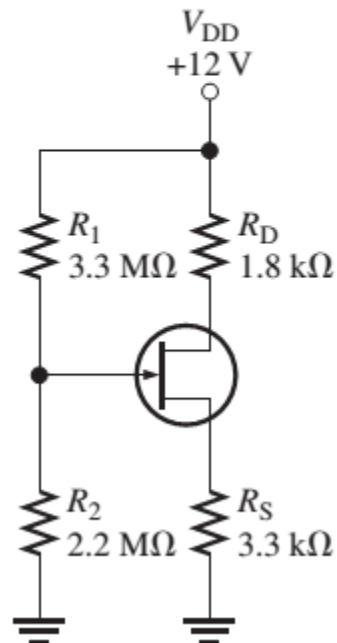
- Determine V_{GS} and I_D for the given JFET, where
 - $I_{DSS} = 5\text{mA}$ and $V_{GS(off)} = -4\text{V}$



C02015

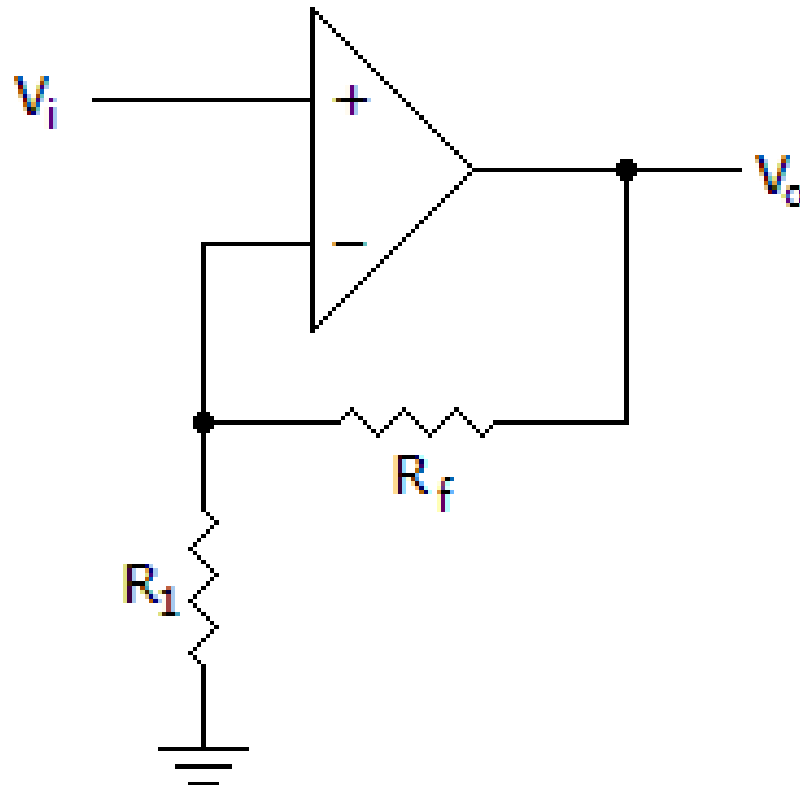Exercise – Op Amp


- Calculate the output gain of the circuit if $R_1 = 100(\text{Ohm})$ and $R_f = 1(\text{KOhm})$



Answer

- 11

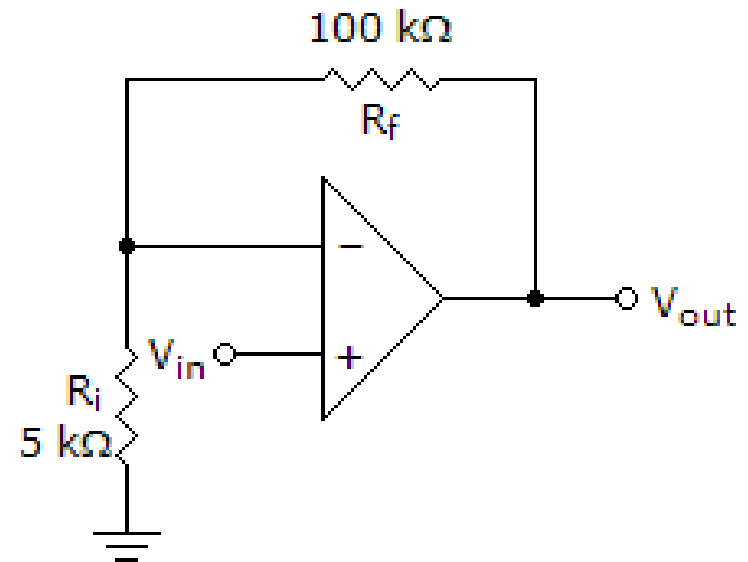- Refer to the given figure. A dc input signal of -50 mV is applied. You would measure _____ from the inverting input to ground.
 - 50mV
 - 1.05V
 - -1.05V
 - -50mV



- Calculate the input voltage if the final output is 10.08 V
 - 0.168V

