
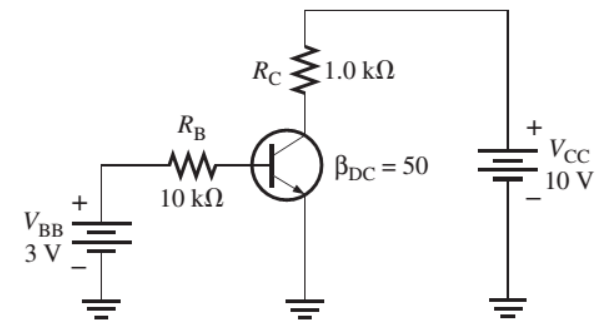


C02015

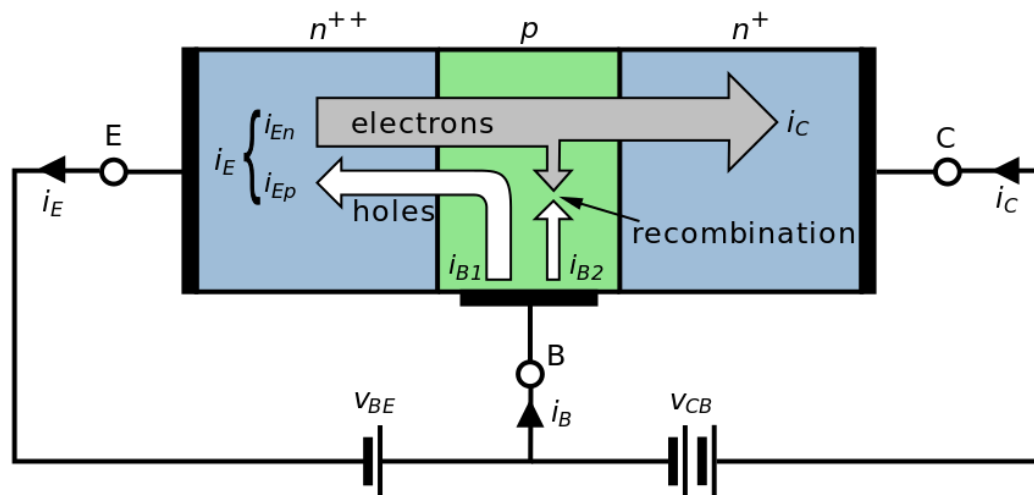
Exercise on Bipolar Junction Transistor (NPN)





DCE

BJT Operation Modes

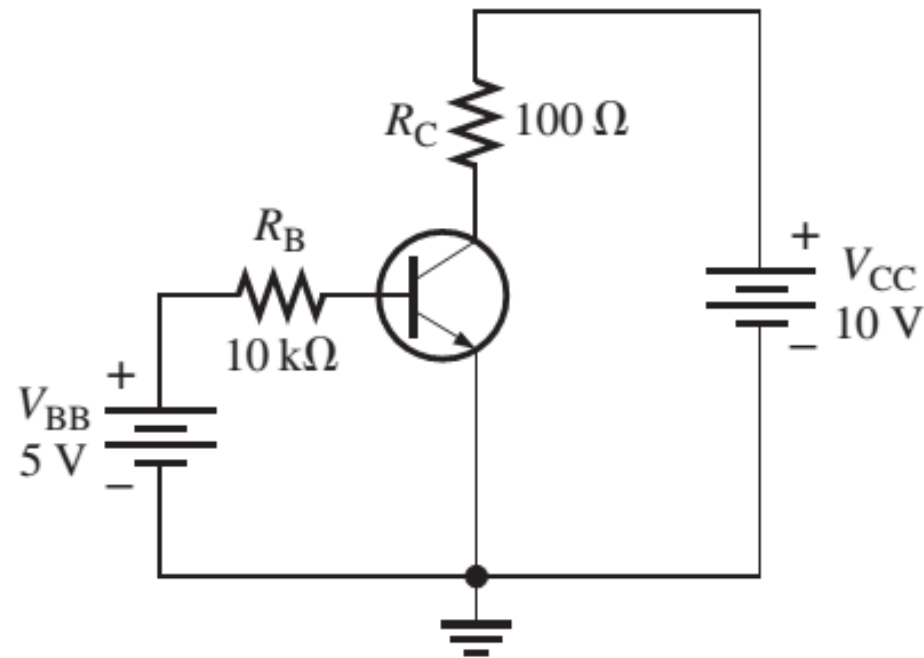- $I_B = 0$: Cut-off mode
- V_B is increased (higher than 0.7V), I_B is increased:
 - $I_C = \beta_{DC} I_B$
 - Amplifier mode (Active mode)
 - V_C is increased
- $V_C = V_{CC} - V_{CE}$
 - Saturation mode
 - V_{CE} is small (0.2V)



BJT in Amplifier Mode

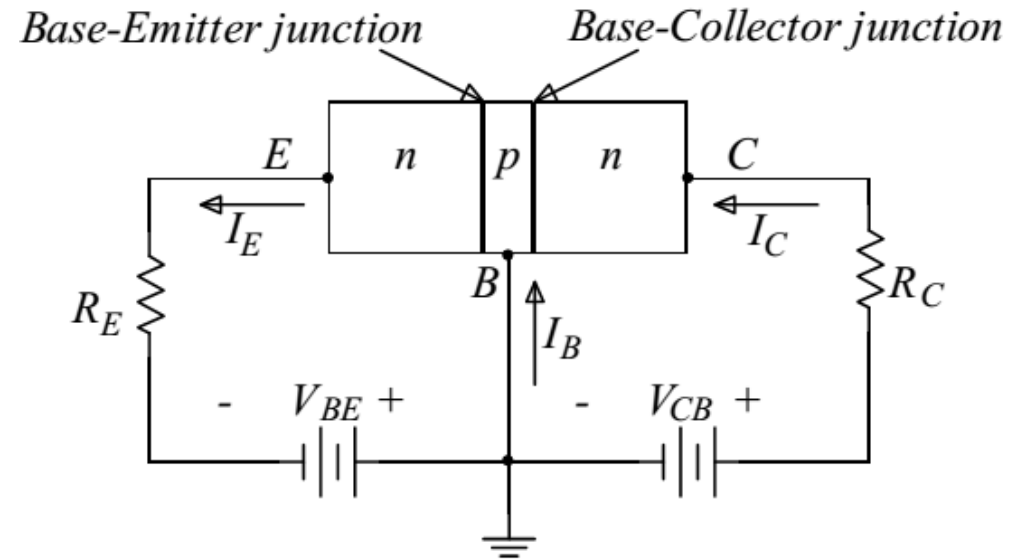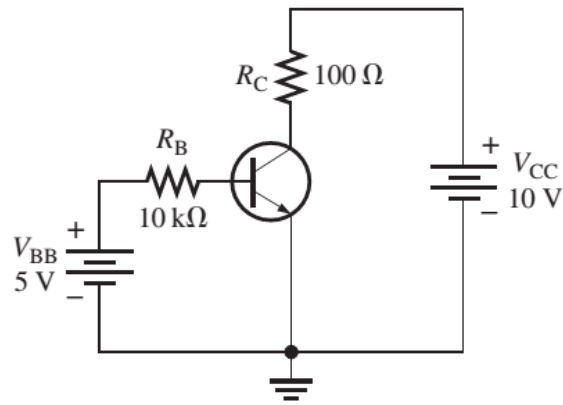


$$I_E = I_C + I_B$$


$$\beta_{DC} = \frac{I_C}{I_B}$$

$$\alpha_{DC} = \frac{I_C}{I_E}$$

DC Load on I-V Curve

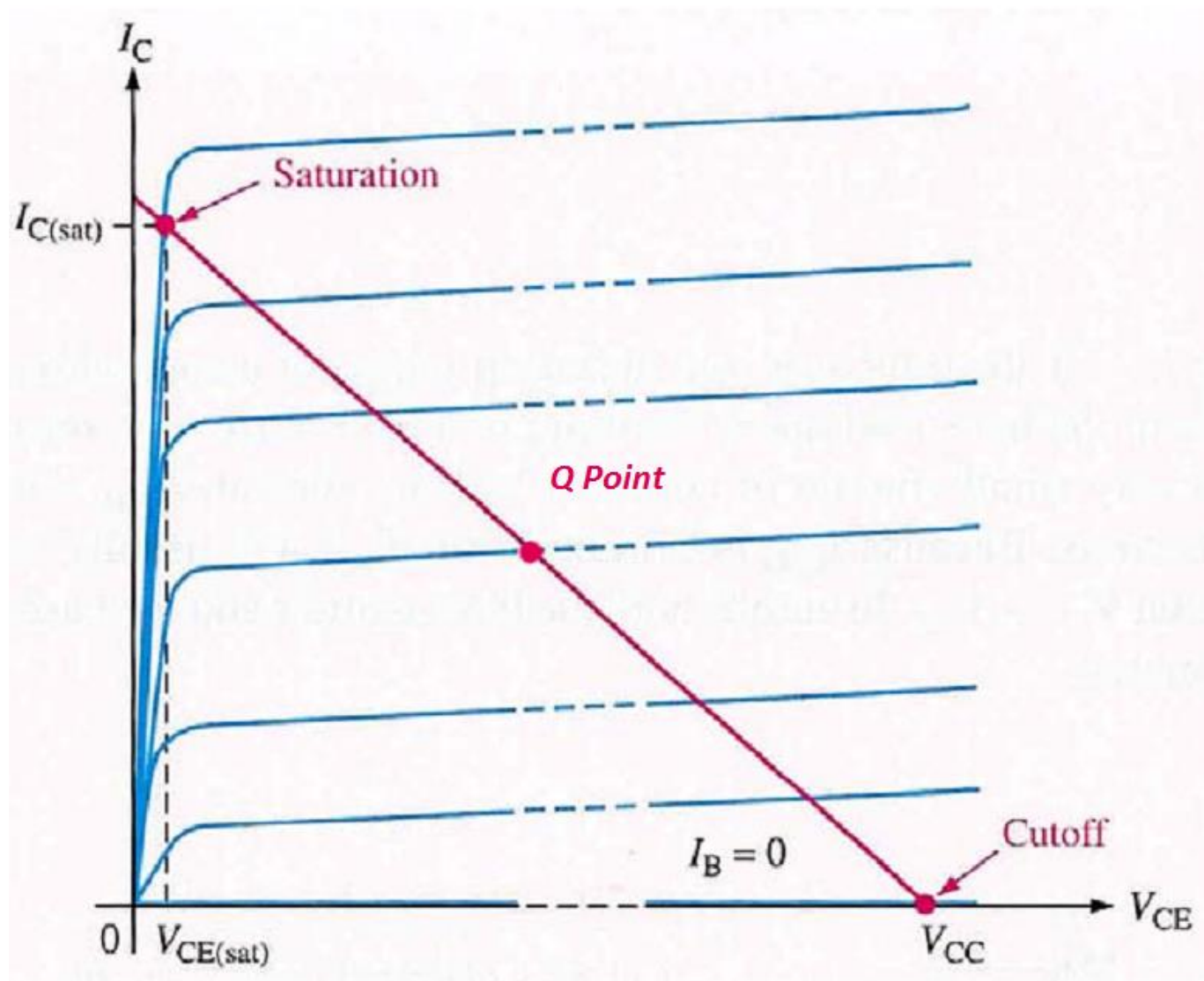

Example

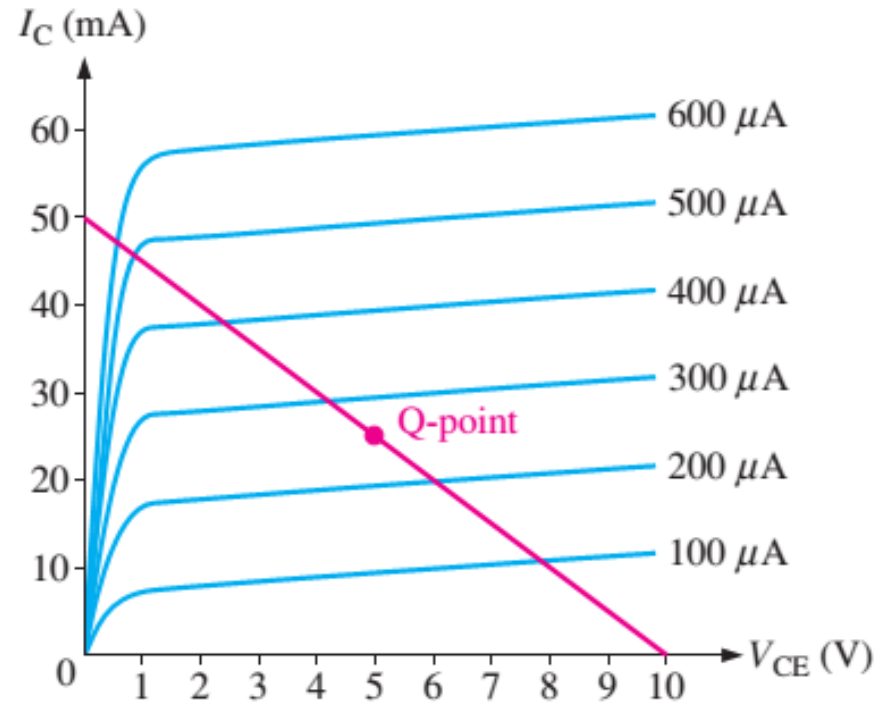


- Determine $I_C(\text{Sat})$
- Determine β_{DC}
- I_B , I_C and V_{CE} at Q point

Answer

- $I_C (\text{Sat}) = 50 \text{ (mA)}$
- $\beta_{DC} = 10\text{mA} / 100\mu\text{A} = 100$
- At Q-point:
 - $I_C = 25 \text{ (mA)}$
 - $V_{CE} = 5 \text{ (V)}$
 - $I_B = 0.25 \text{ (mA)}$

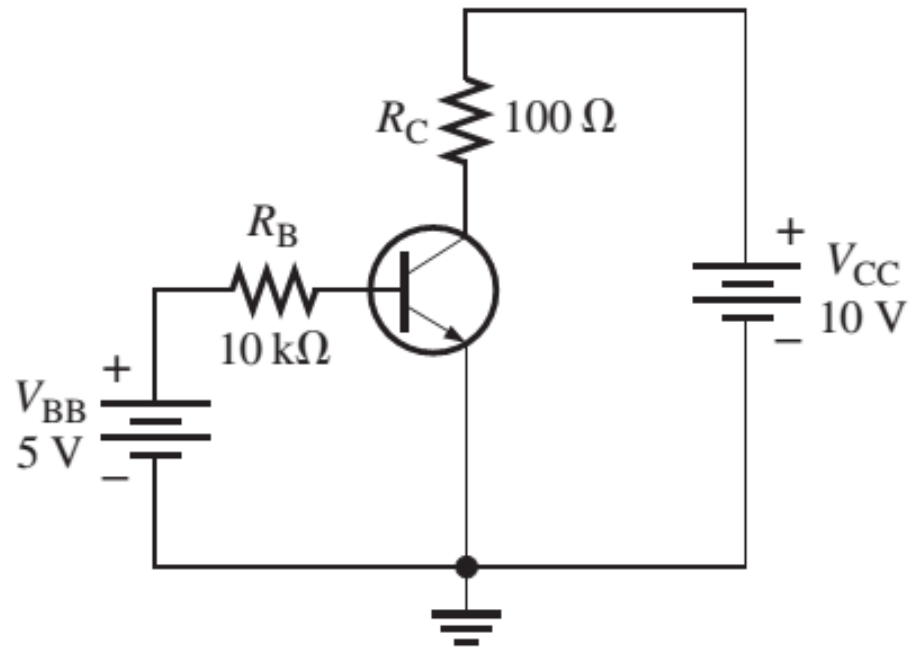
- Determine I_B , I_C , I_E , V_{BE} , V_{CE} and V_{CB} for the given circuit when $\beta_{DC} = 150$



$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5\text{ V} - 0.7\text{ V}}{10\text{ k}\Omega} = \mathbf{430\text{ }\mu\text{A}}$$

$$I_C = \beta_{DC} I_B = (150)(430\text{ }\mu\text{A}) = \mathbf{64.5\text{ mA}}$$

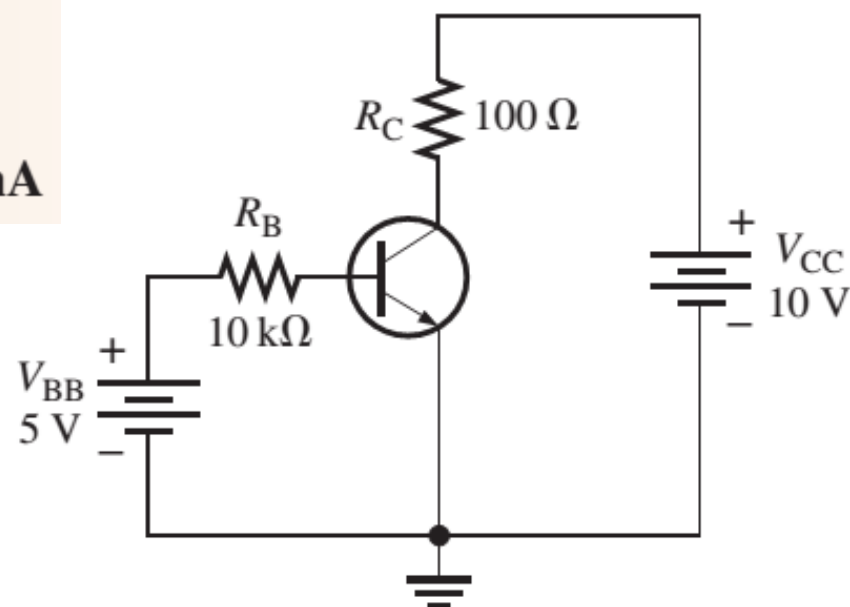
$$I_E = I_C + I_B = 64.5\text{ mA} + 430\text{ }\mu\text{A} = \mathbf{64.9\text{ mA}}$$




$$V_{CE} = V_{CC} - I_C R_C = 10\text{ V} - (64.5\text{ mA})(100\text{ }\Omega) = 10\text{ V} - 6.45\text{ V} = \mathbf{3.55\text{ V}}$$

$$V_{CB} = V_{CE} - V_{BE} = 3.55\text{ V} - 0.7\text{ V} = \mathbf{2.85\text{ V}}$$

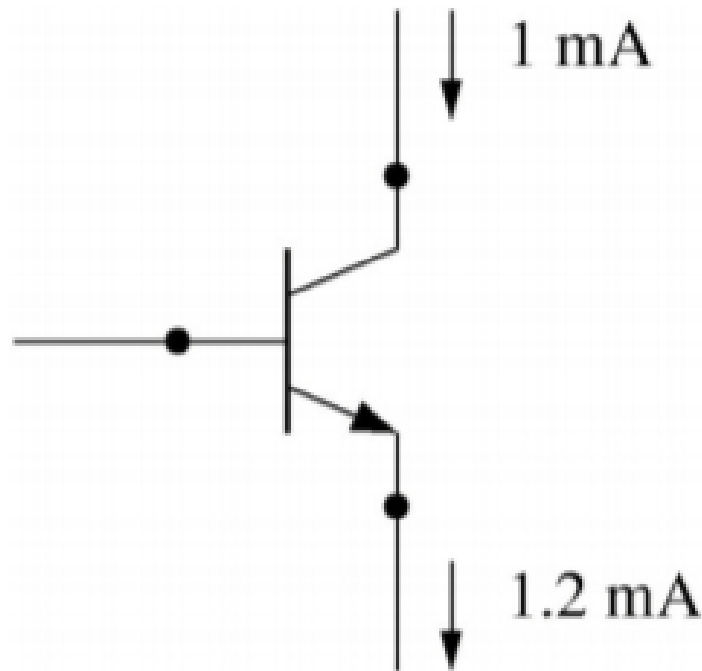- Find state of transistor (cut-off, amplifier or saturation) and its currents/voltages



Answer

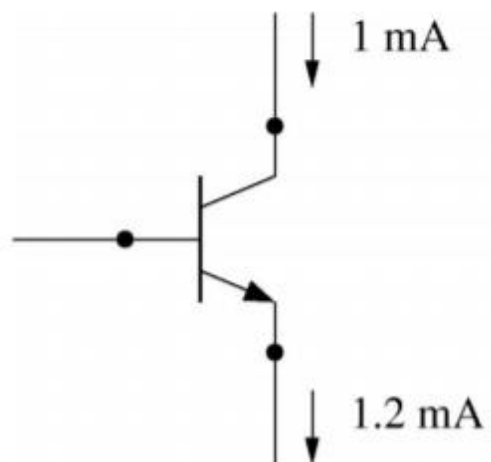

$i_C = 1 \text{ mA} > 0$: BJT is NOT in cut-off

$$i_E = 1.2 \text{ mA}$$

$$i_B = i_E - i_C = 0.2 \text{ mA}$$

$$i_C / i_B = 1 / 0.2 = 5 < \beta_{min}$$

BJT is in saturation:

$$v_{CE} = V_{sat} = 0.2 \text{ V}$$


$$v_{BE} = V_{D0} = 0.7 \text{ V}$$

- When a transistor is used as a switch, it is stable in which two distinct regions?
 - saturation and active
 - active and cutoff
 - saturation and cutoff
 - none of the above


- For a silicon transistor, when a base-emitter junction is forward-biased, it has a nominal voltage drop of
 - 0.7
 - 0.3
 - 0.2
 - V_{CC}

- A certain BJT has $I_B = 167\mu\text{A}$, $I_C = 15\text{mA}$, the amplifier DC factor is:
 - 15
 - 167
 - 90
 - All are not correct

Exercise

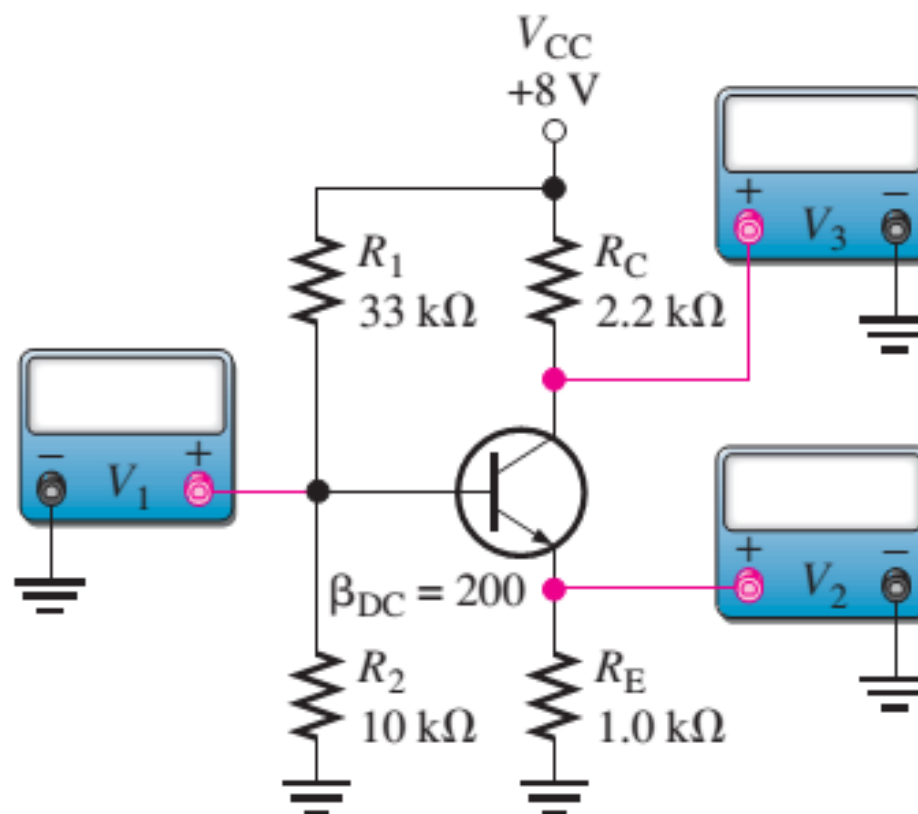


- Determine values on V_1 , V_2 , V_3

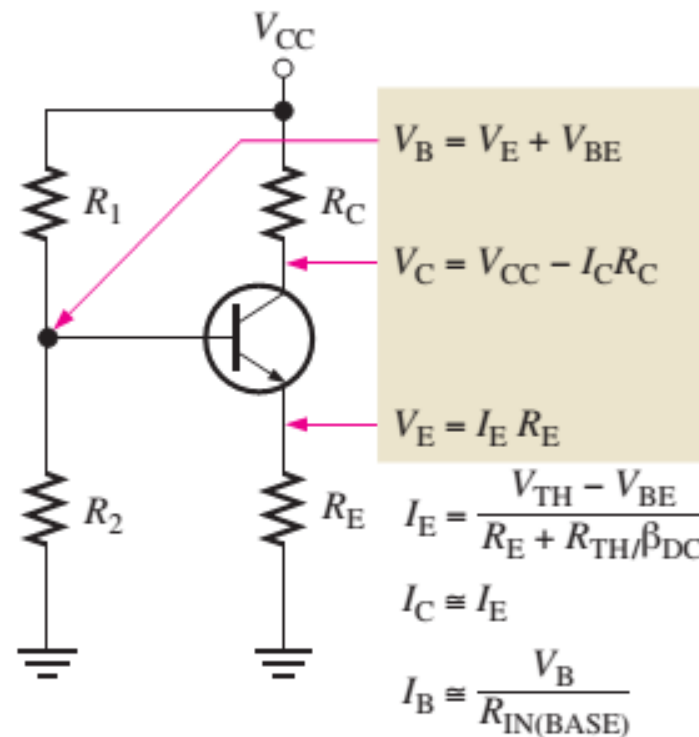


$$R_{IN(BASE)} = V_B / I_B = V_B / (I_E / \beta_{DC})$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} \quad R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$$

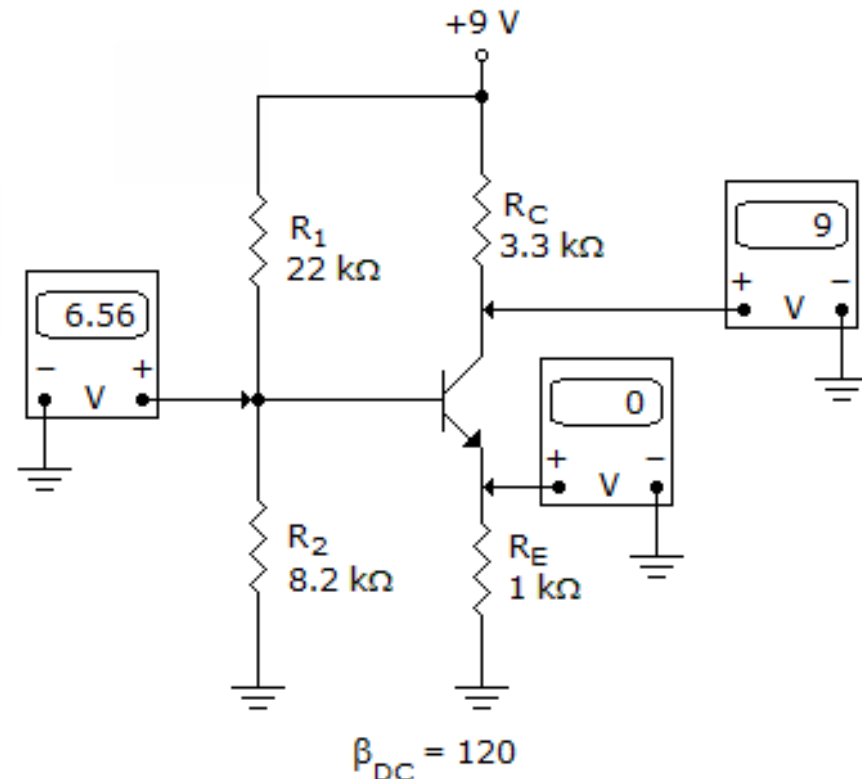
- Refer to the given figure. The most probable cause of trouble, if any, from these voltage measurements is



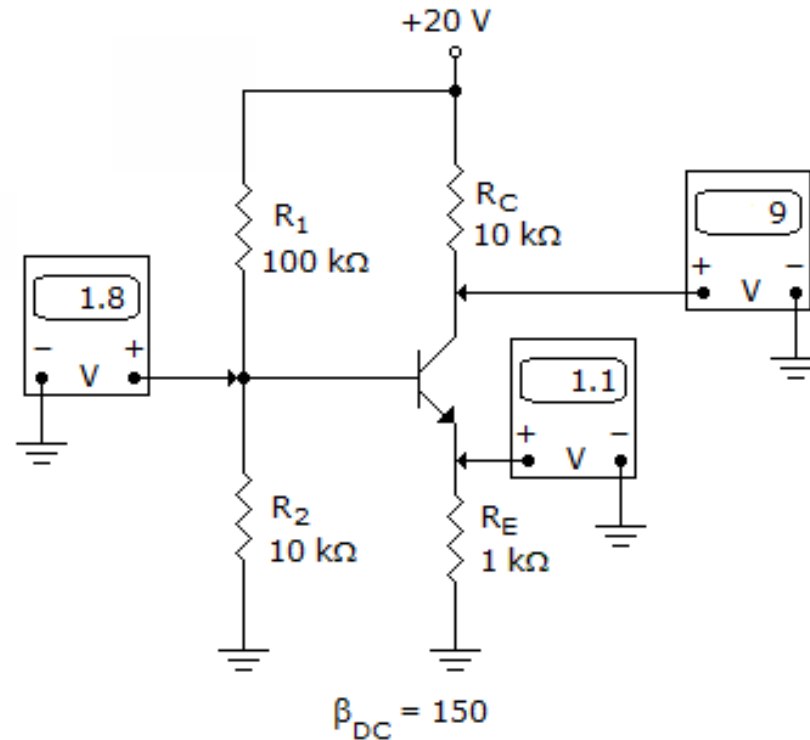
- Refer to the given figure. The most probable cause of trouble, if any, from these voltage measurements is



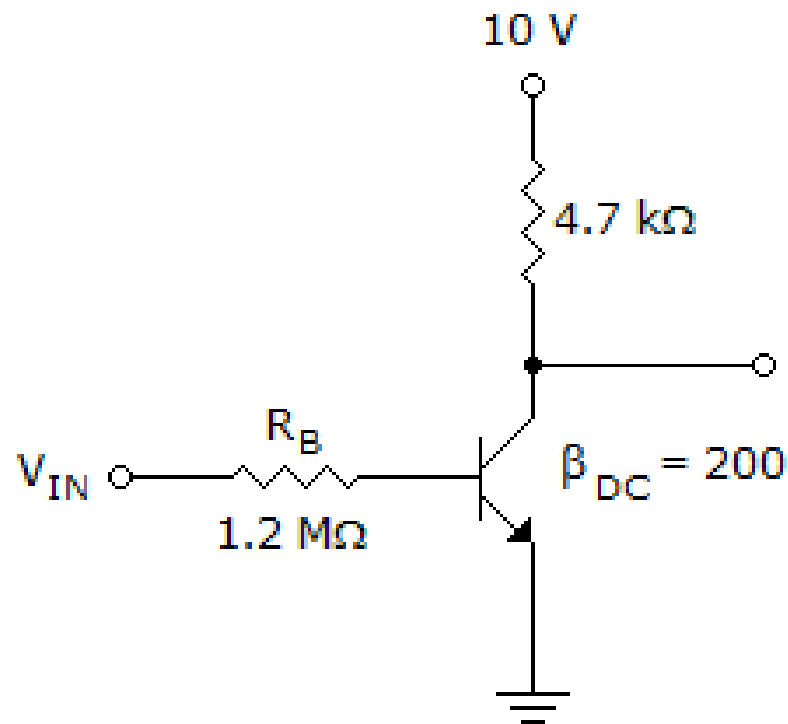
- Refer to this figure. If $V_{CE} = 0.2 \text{ V}$, $I_{C(\text{sat})}$ is




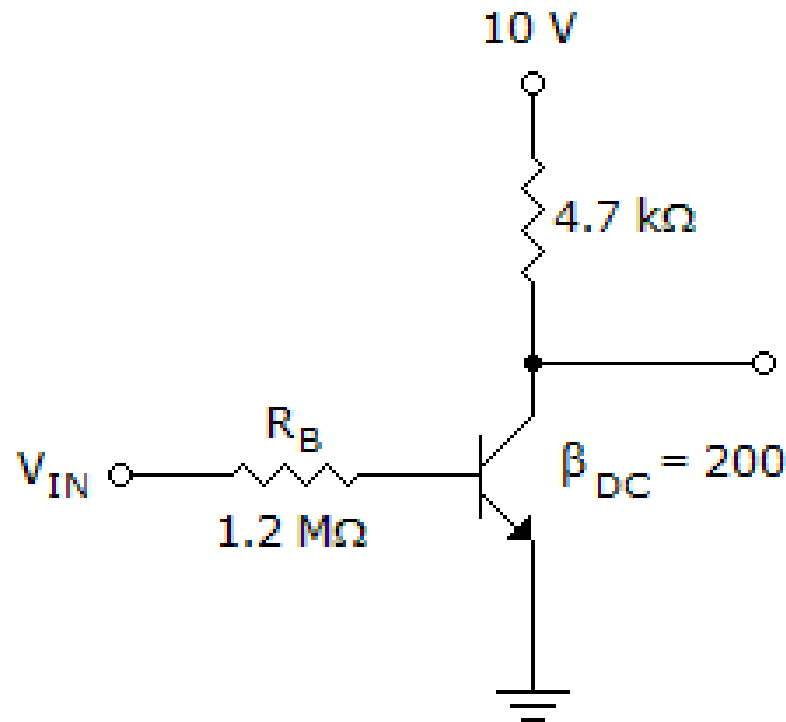- Refer to this figure. Determine the minimum value of I_B that will produce saturation ($V_{CE}(\text{sat}) = 0.2\text{V}$).




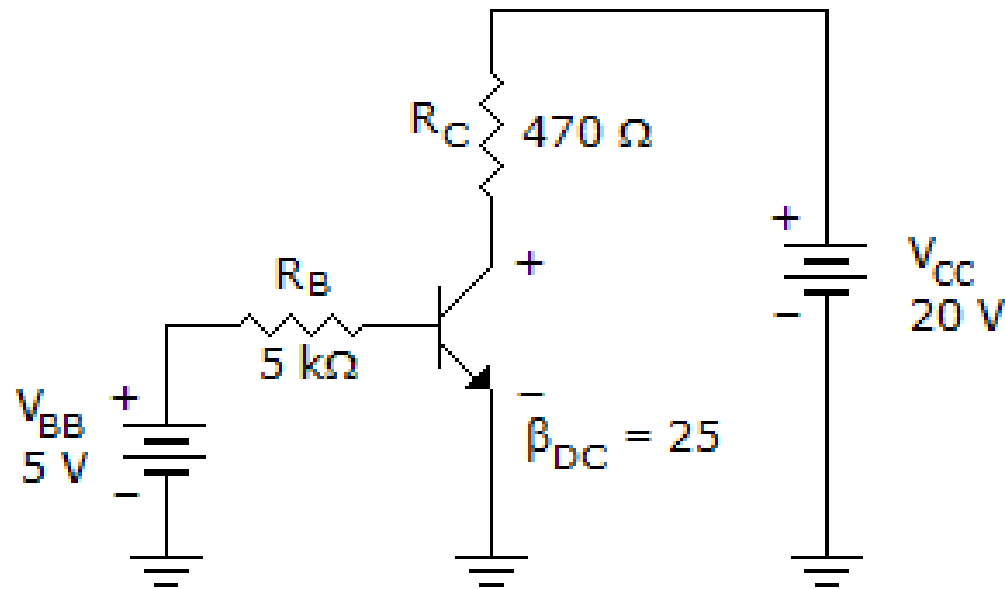- Refer to this figure. The value of V_{BC} is




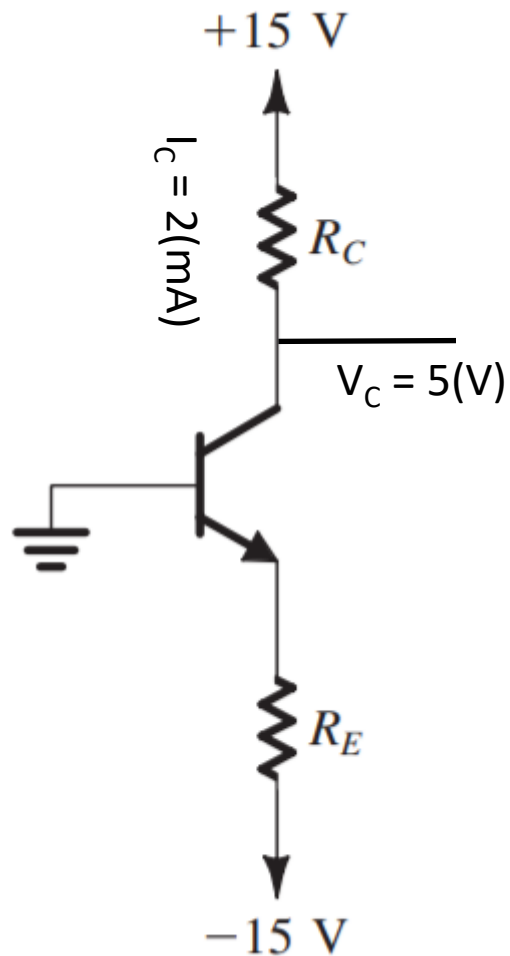

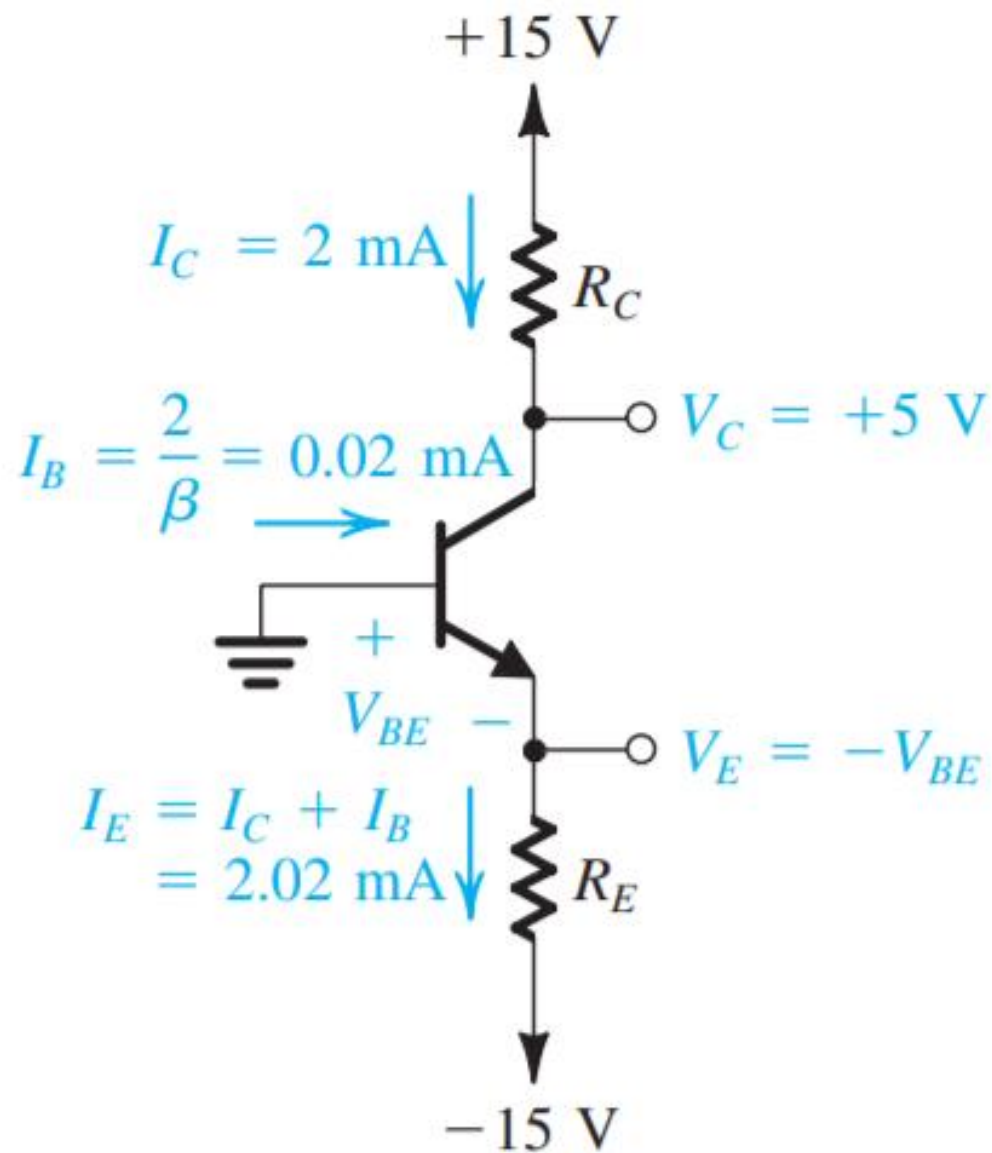- Determine R_C , R_E
- $V_C = 5V$, $I_C = 2mA$
- $\beta_{DC} = 100$



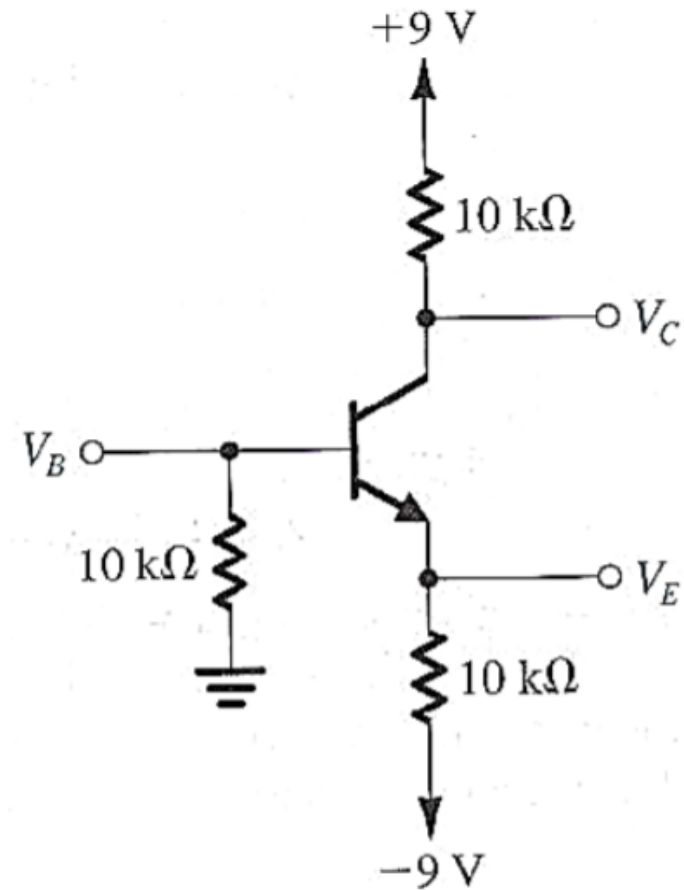- $V_B = -1.5V$
- Calculate I_B , I_C , I_E



Midterm (60 mins – Closed Book)

- 28/03/2019
- Multichoice + Written

- Chapter 1: Basic Electronic Components
 - Determine the resistor values (4-band colors, 5-band colors)
 - LEDs connectors (Serial + Parallel)

- Chapter 2: Diode
 - Diode Principles and Models
 - Applications using Diodes

- Chapter 3: BJT (npn)
 - Amplifier Coefficient, Applications
 - Cutoff, Saturation and Amplifier modes
 - $V_{be} = 0.7$ (for default)