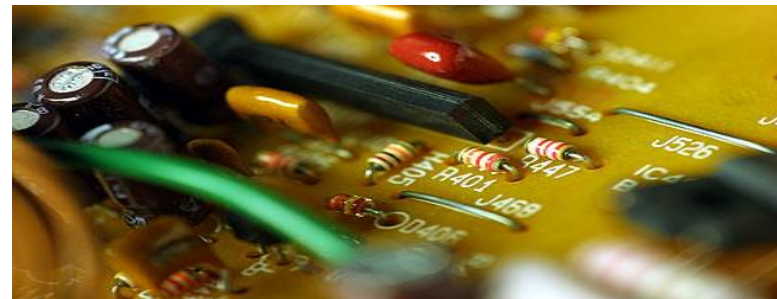





**C02015**

# **Introduction to Transistors and Applications**






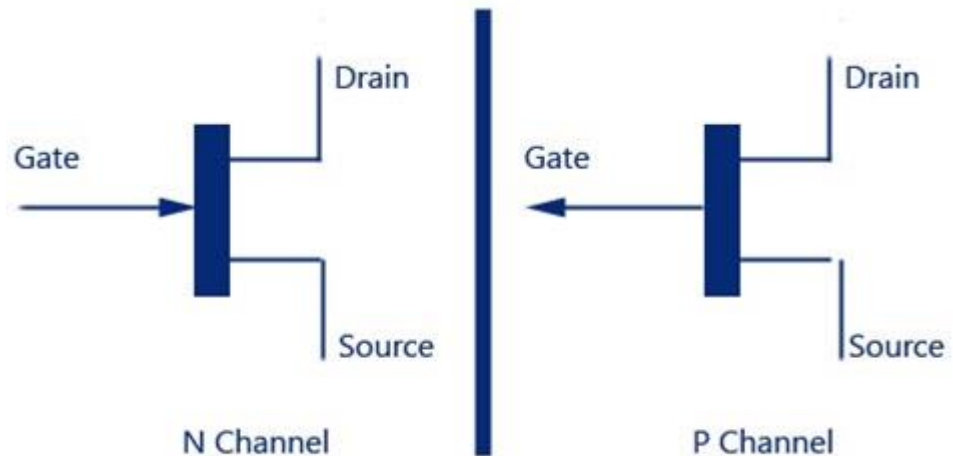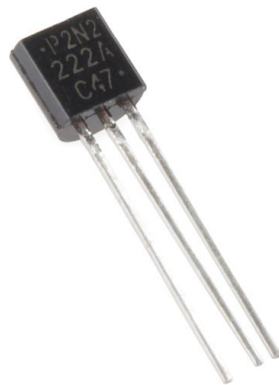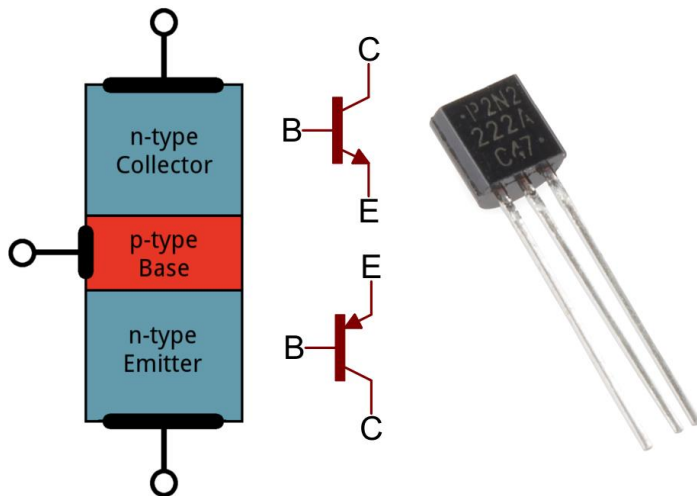
# What is Transistor?

- Transistor is a semiconductor device used to:
  - Amplifier signal
  - Switch signal or electrical power
- There are two types of basic transistor out there: Bi-Polar Junction (BJT) and Metal-Oxide Field-Effect (MOSFET)






# Transistor

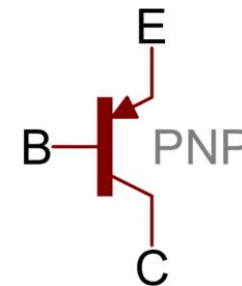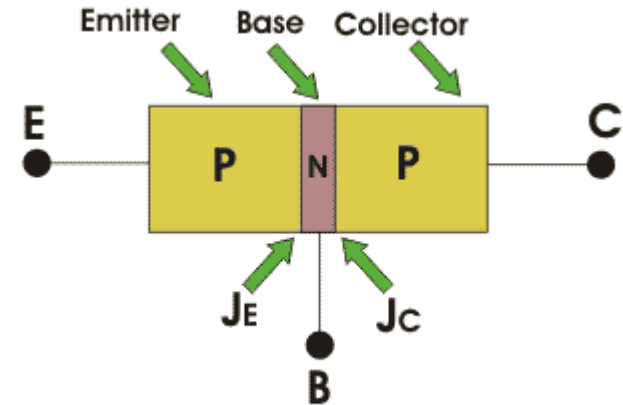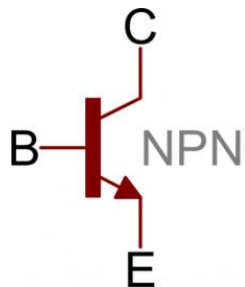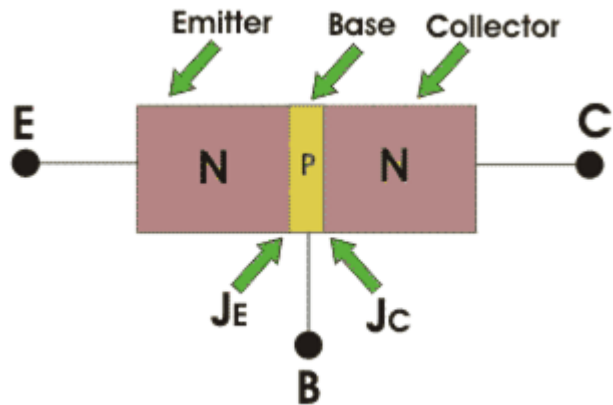

- Bi-polar Junction Transistor (BJT)
- **Collector (C), Base (B), and Emitter (E)**



# Transistor = 2 Diodes

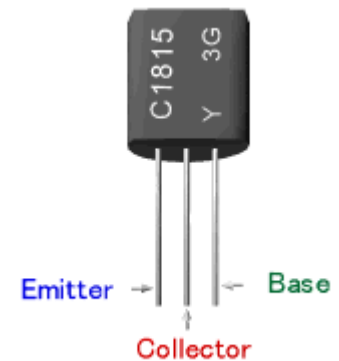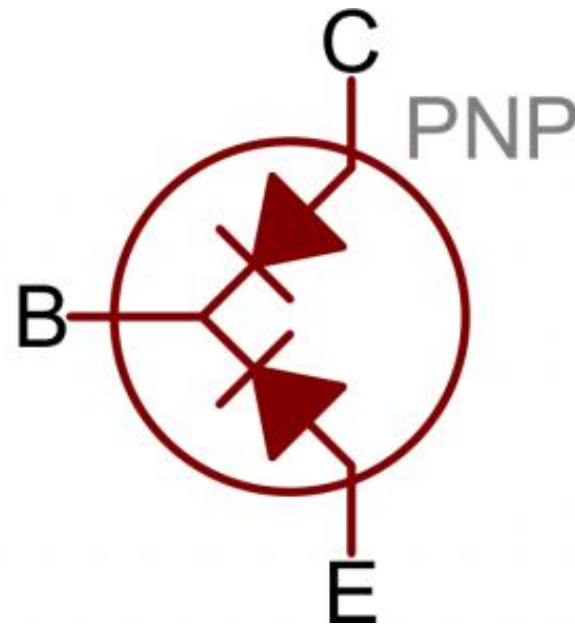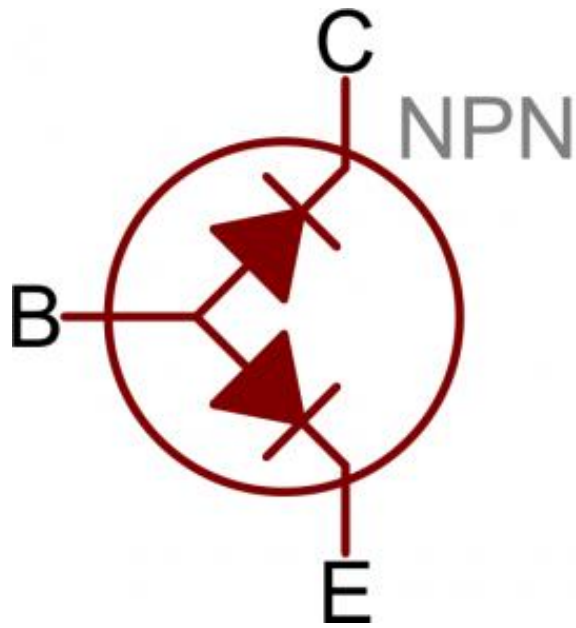

- Checking transistors is similar to diodes
- Pin order: ECB or BCE
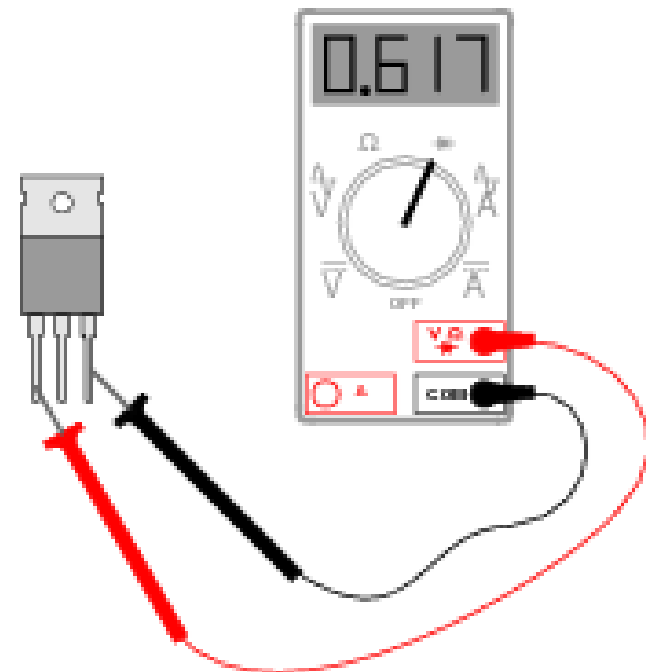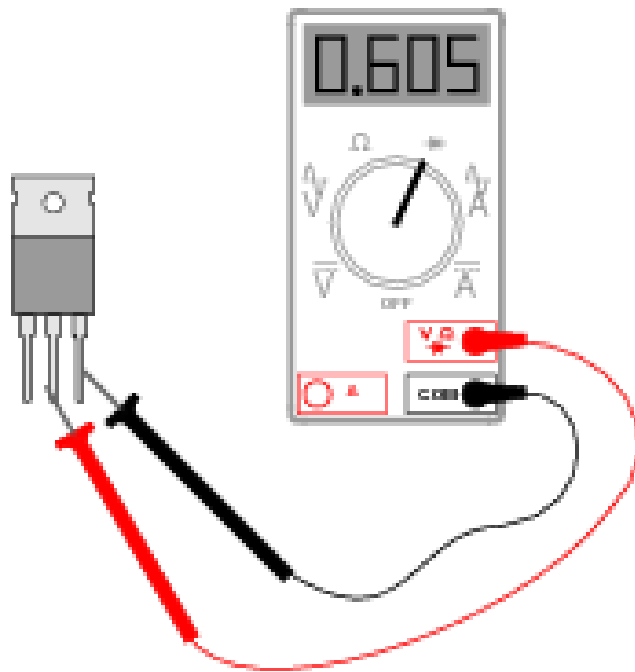
# Exercise


- From these measurements, determine what type of BJT this is (PNP or NPN)




# Answer

- PNP transistor

PNP transistor

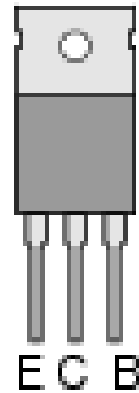


# Saturation Mode

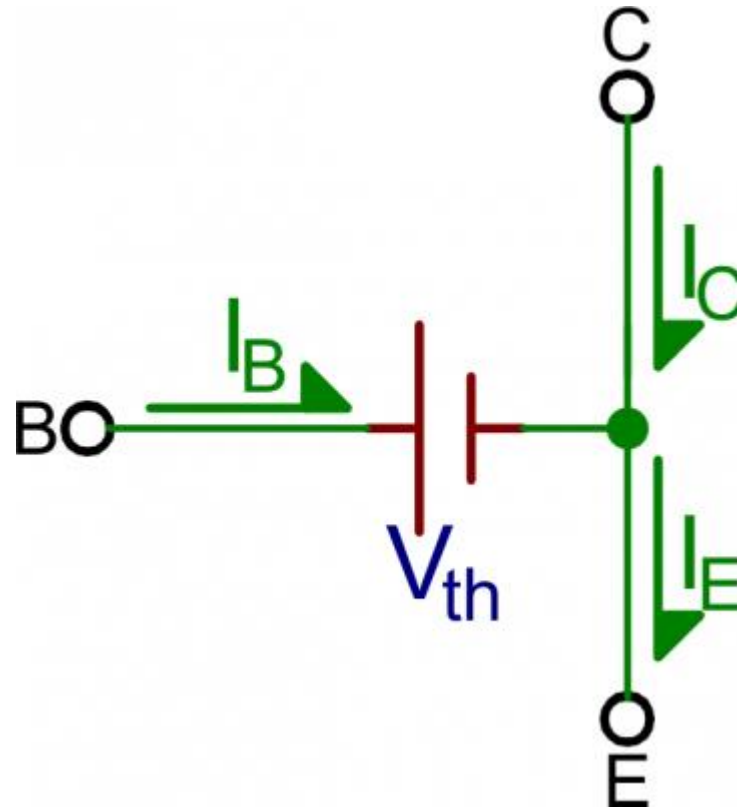

- Saturation is the **ON MODE** of a transistor
- A transistor in saturation mode acts like a short circuit between collector and emitter

# Cut-Off Mode

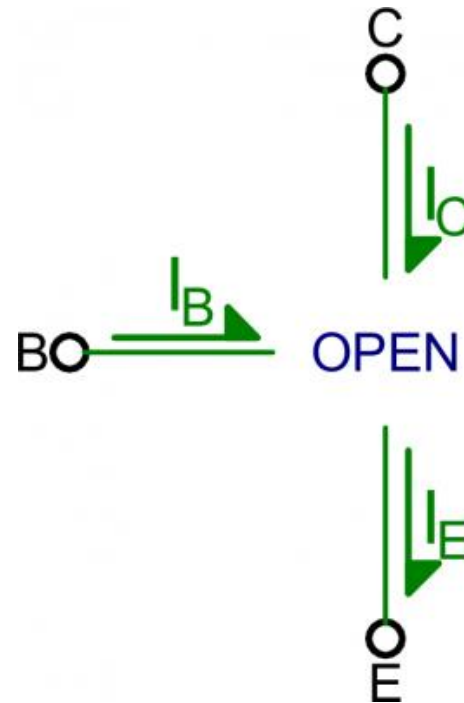


- Cutoff mode is the opposite of saturation
- There is no collector current, and therefore no emitter current
- It almost looks like an open circuit



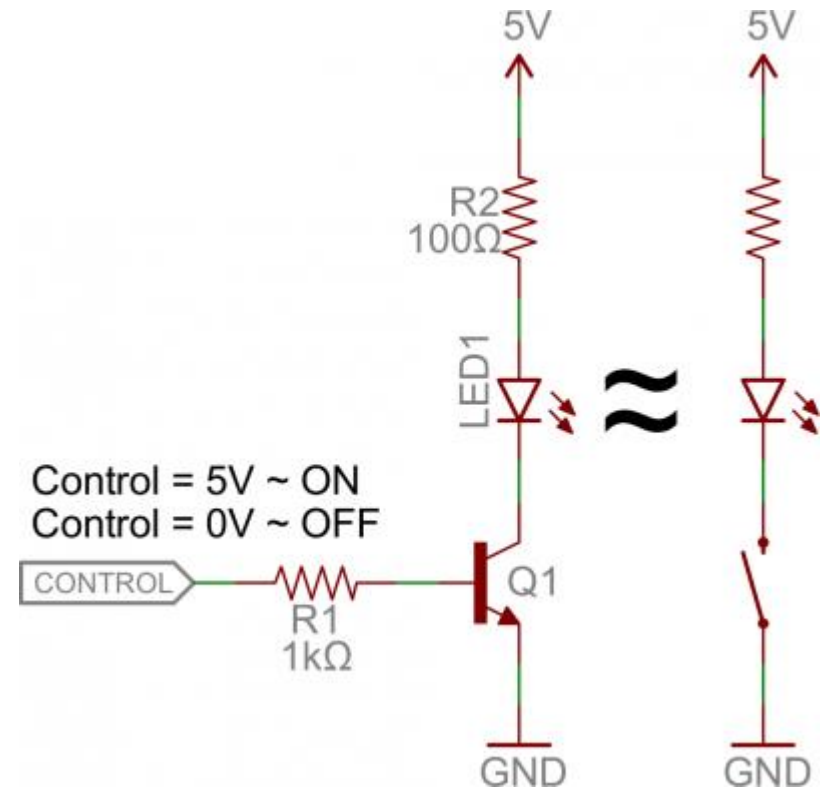
# Applications I: Switches

- When the voltage at the base is greater than 0.6V, the transistor starts saturating ☐ **short circuit**
- When the voltage at the base is less than 0.6V the transistor is in cutoff mode ☐ **open circuit**
- Low-side switch**




# Applications I: Switches

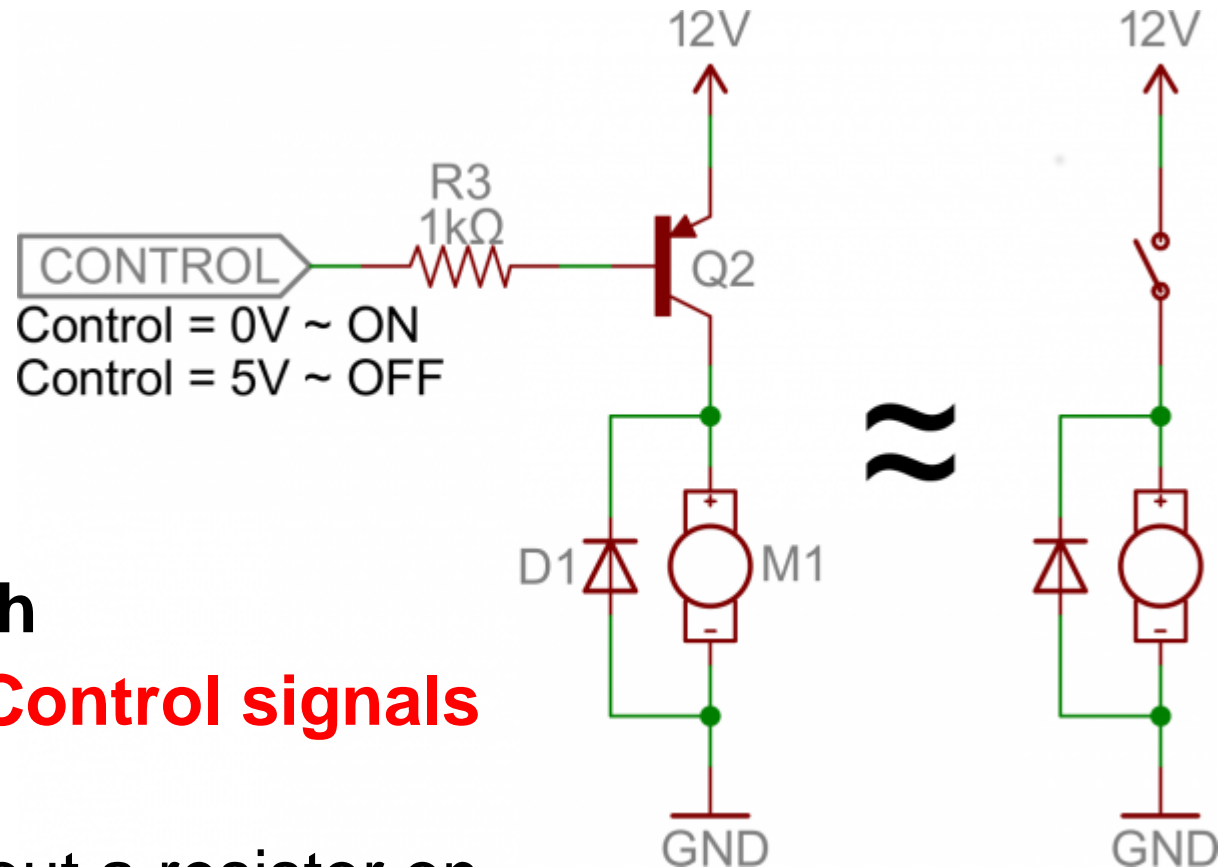


- **High side switch**
- PNP transistor: **Control signals are reversed**
- A transistor without a resistor on the base is like an LED with no current-limiting resistor


# Logic Gate - NOT

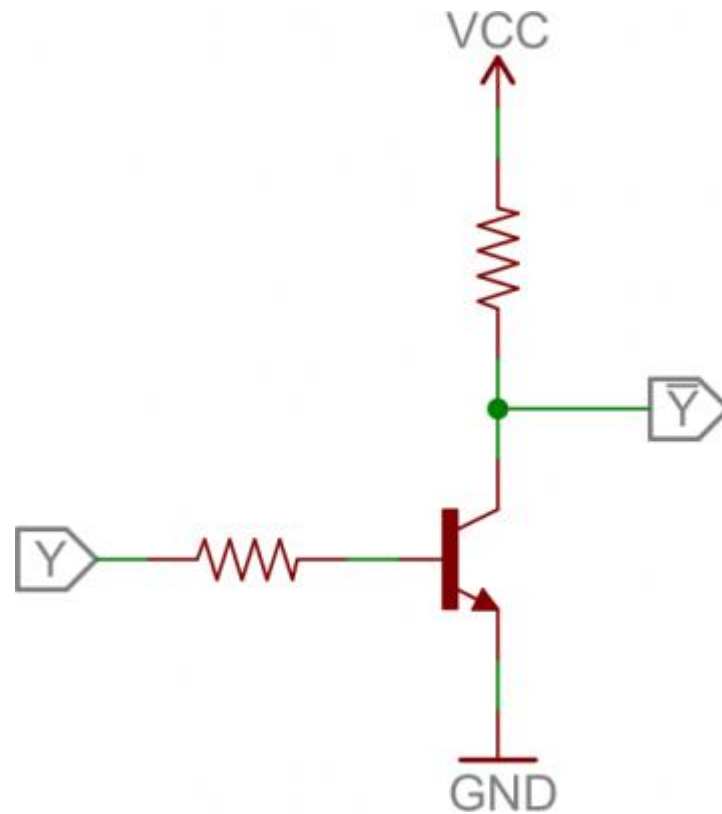


# Logic Gates

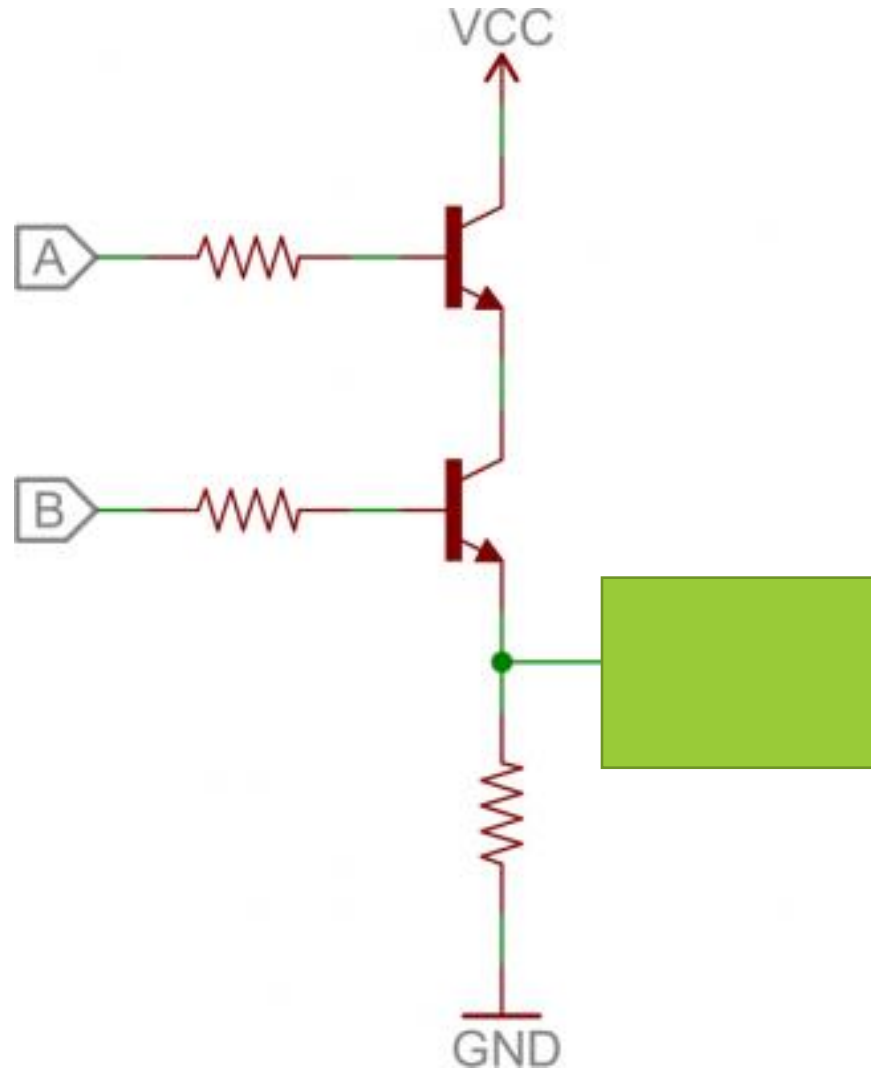


# Logic Gate

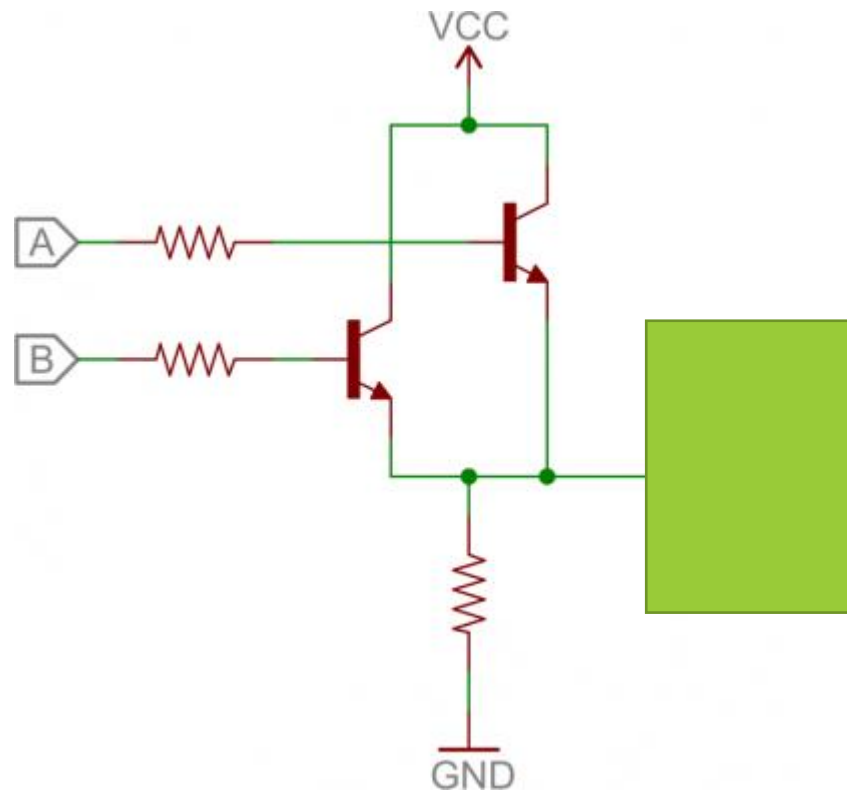

# H-Bridge

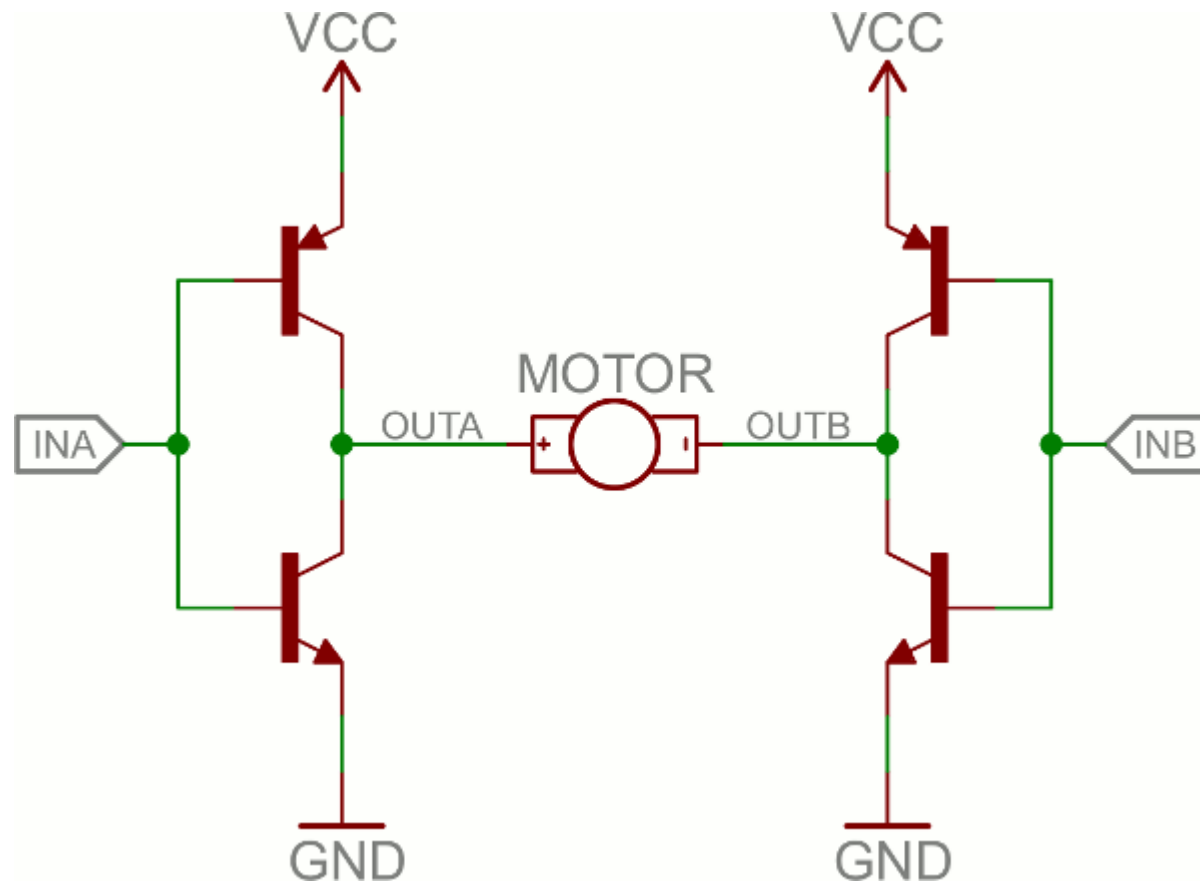


# Oscillator

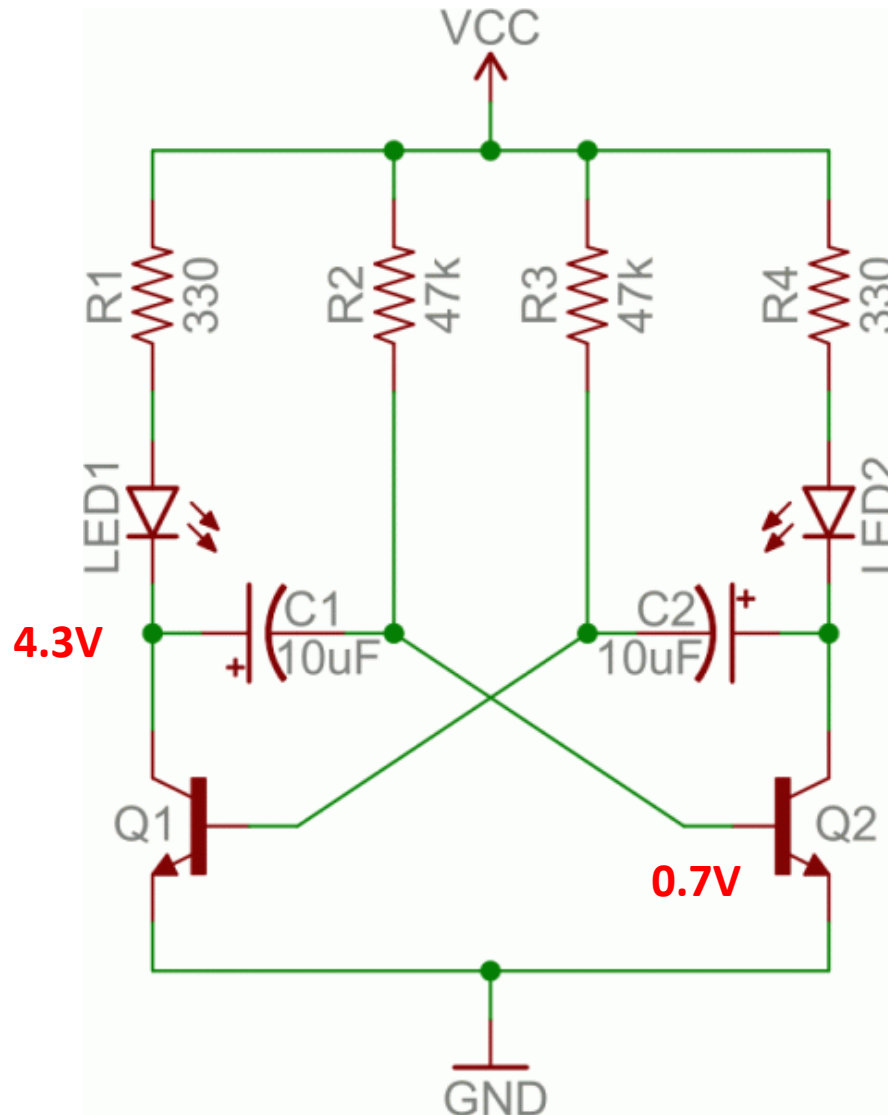

- Q2 ON – Q1 OFF
- $V_{BE} (Q2) = 0.7V$
- The voltage from  $V_{CC}$  charges C1 to 4.3V


# Oscillator

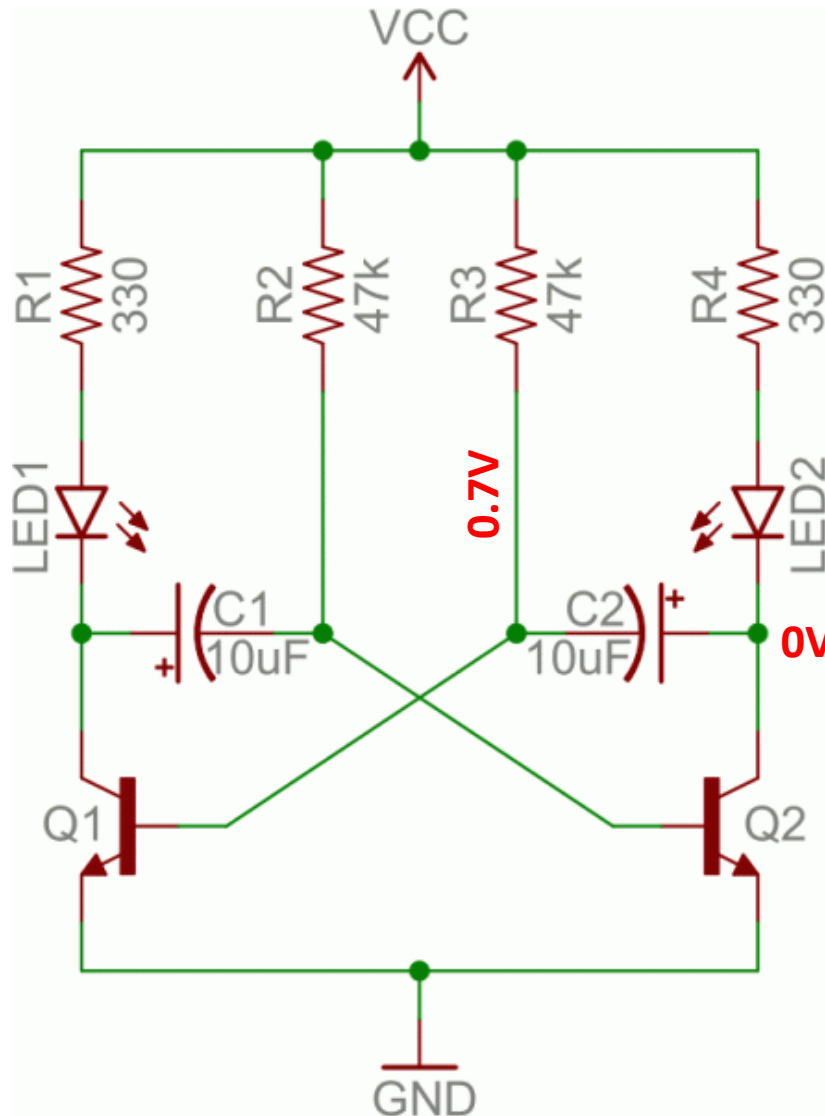

- Positive of C2 is connected to GND (due to Q2 is ON)
- VCC slowly charges C2 until 0.7V → Q1 ON




# Oscillator

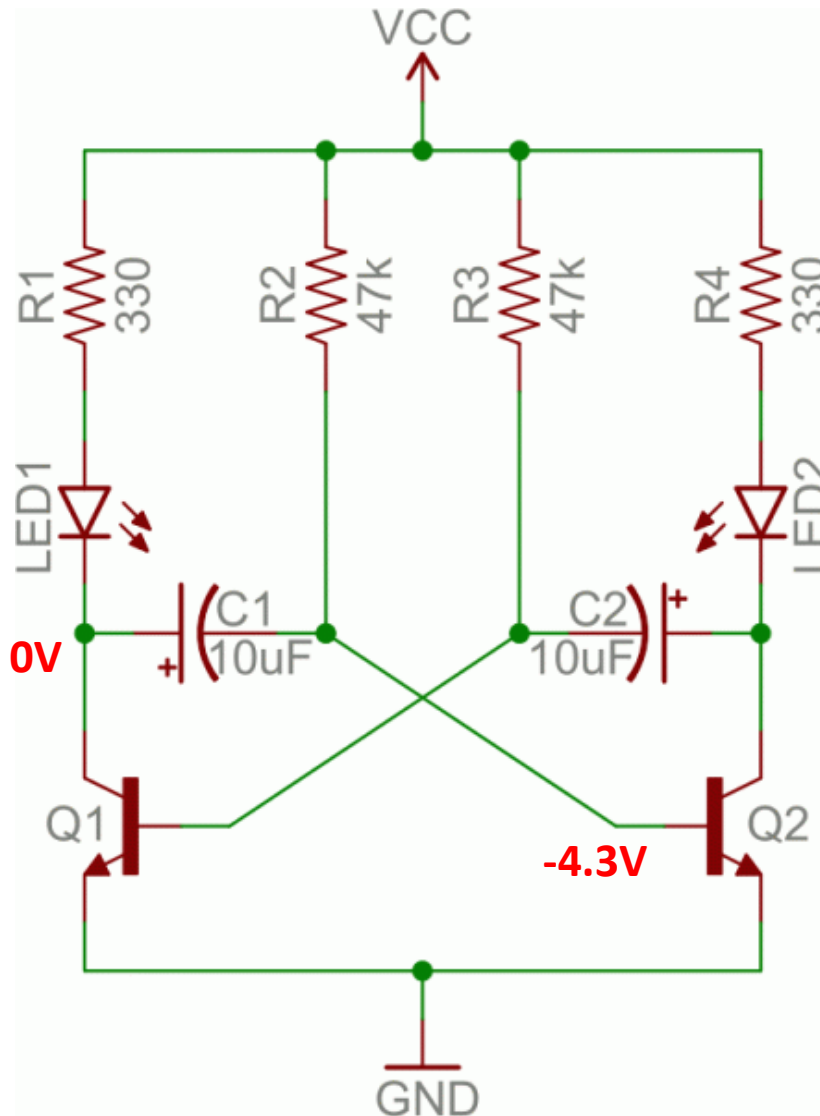

- VC1 is currently 4.3V
- Positive pin returns to 0V
- Negative pin goes to minus 4.3V → Q2 OFF



# Oscillator

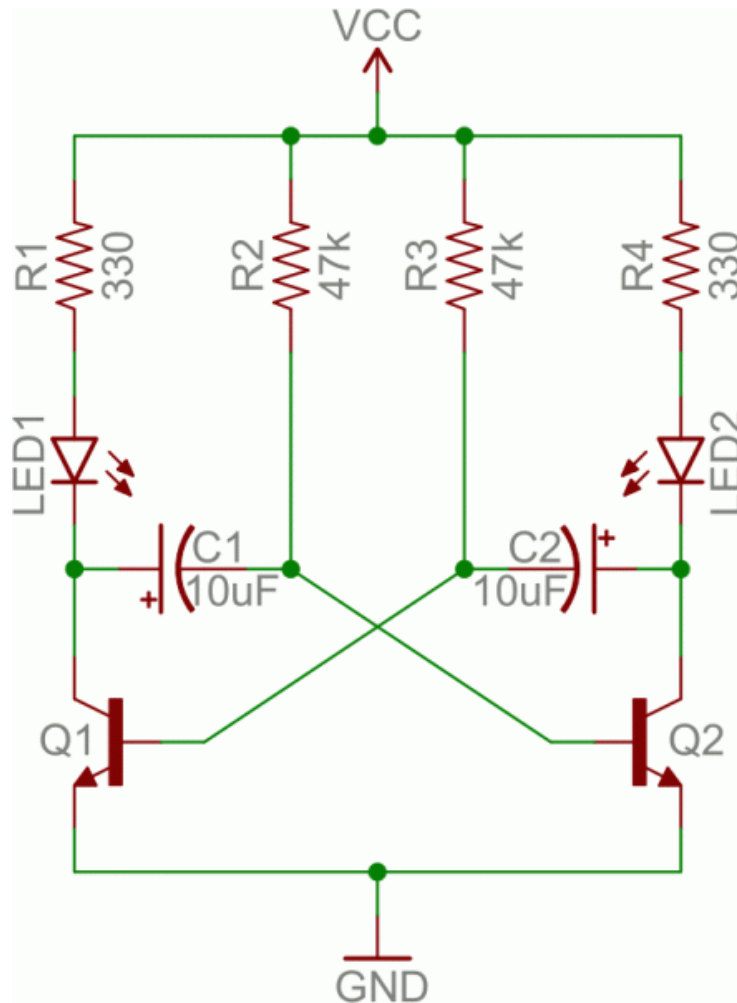






$$f = \frac{1}{\ln(2) \cdot (R_2 C_1 + R_3 C_2)}$$

C02015

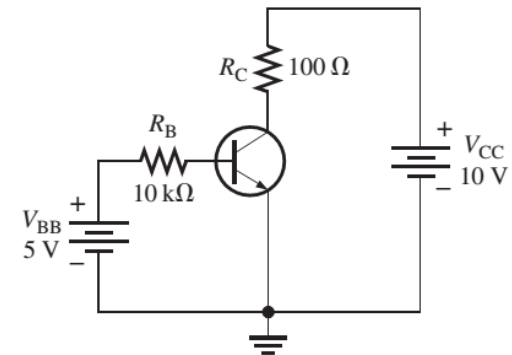
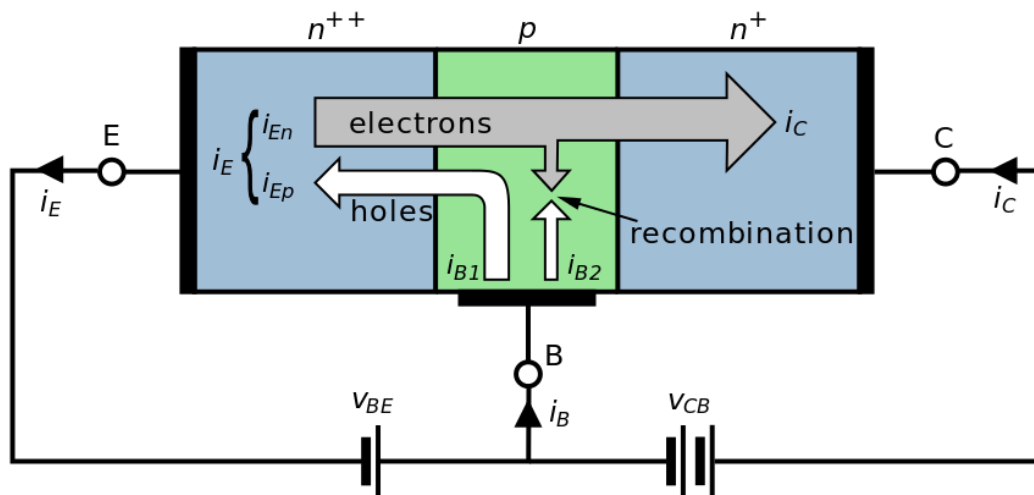
# Amplifier using Bipolar Junction Transistor



# Bipolar Junction Transistor

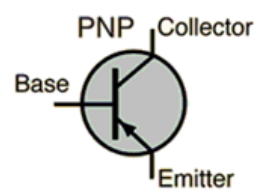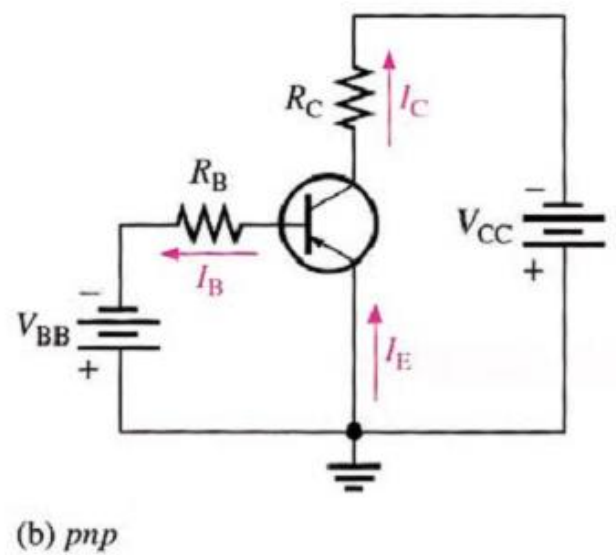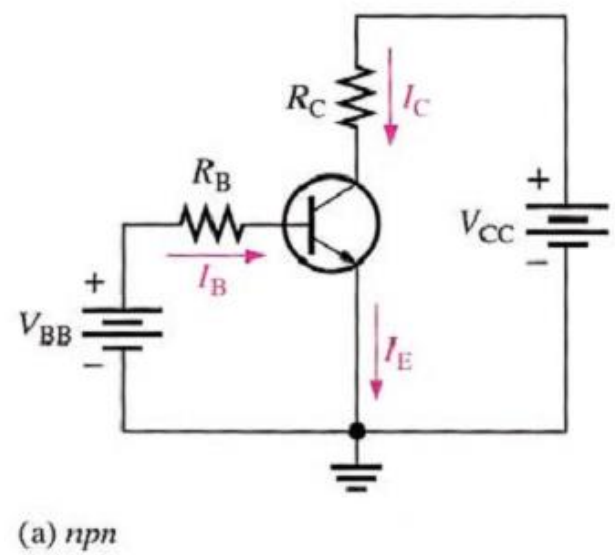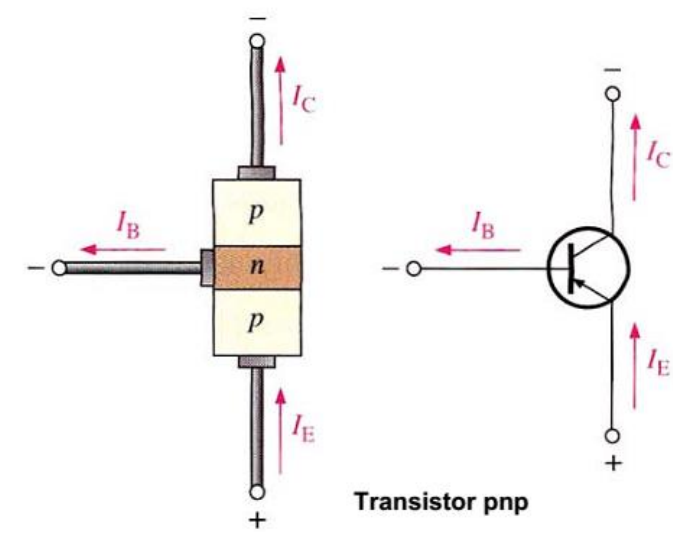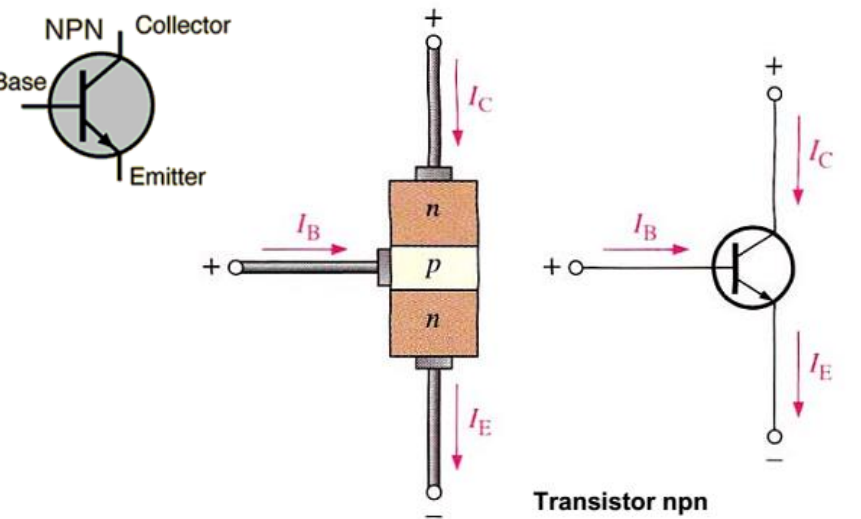

# BJT as Amplifier

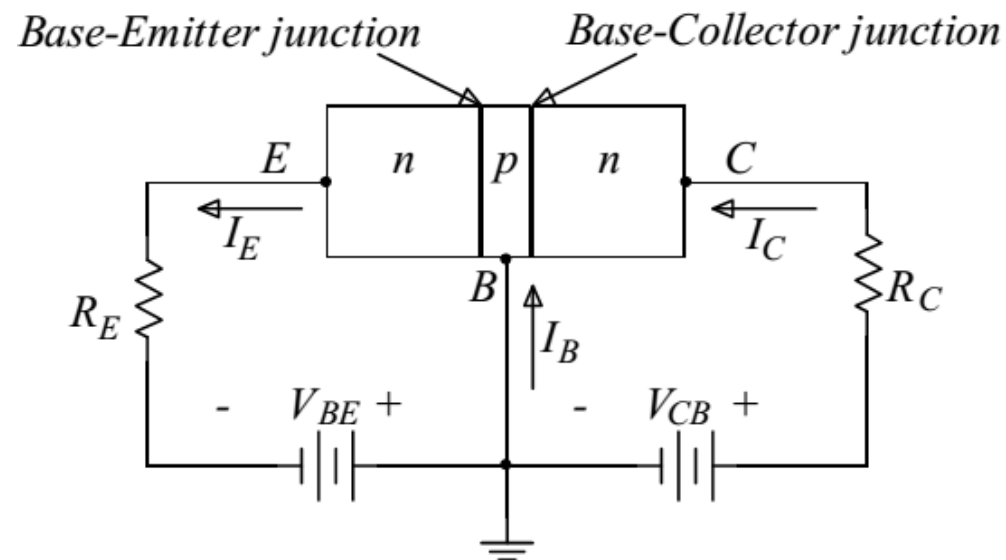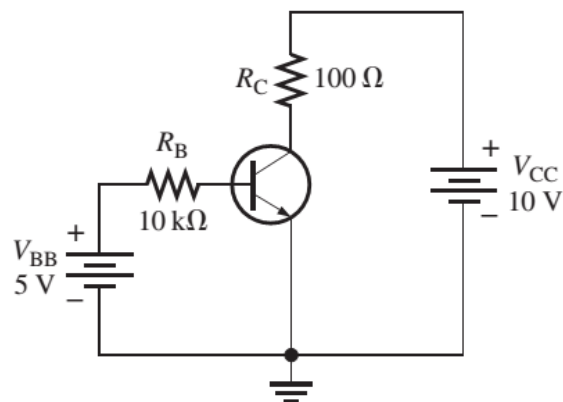




$$I_E = I_C + I_B$$

$$\beta_{DC} = \frac{I_C}{I_B}$$

$$\alpha_{DC} = \frac{I_C}{I_E}$$
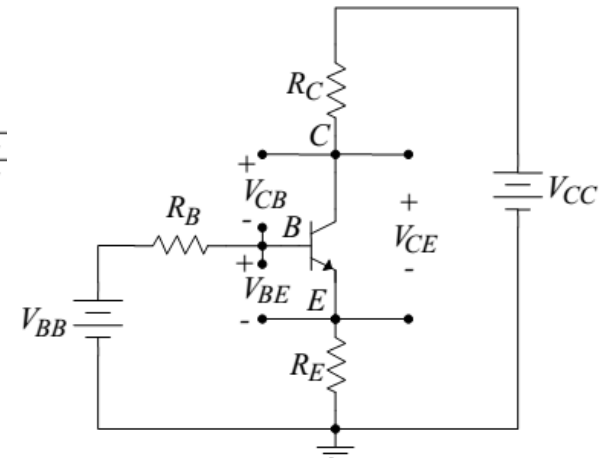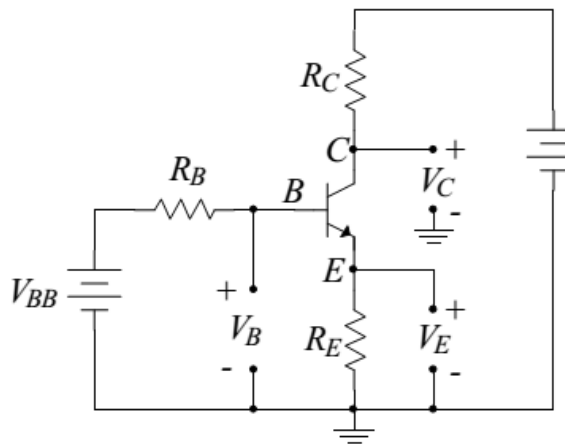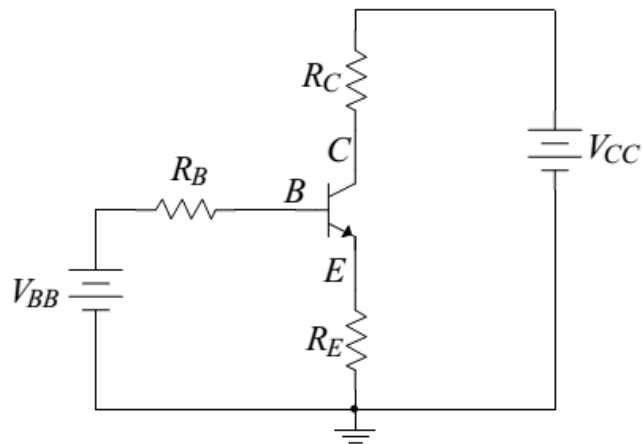
# Voltages in a BJT

- $V_{CC}$  ,  $V_{BB}$
- $V_C$  ,  $V_B$  ,  $V_E$
- $V_{BE}$  ,  $V_{CE}$  ,  $V_{CB}$



# Current and Voltage Analysis

- E-B: Forward Bias (like diode)
  - $V_{BE} \approx 0.7V$
- Base Circuit


$$V_{BB} = R_B \cdot I_B + V_{BE}$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

- Collector Circuit


$$V_{CC} = R_C \cdot I_C + V_{CE}$$
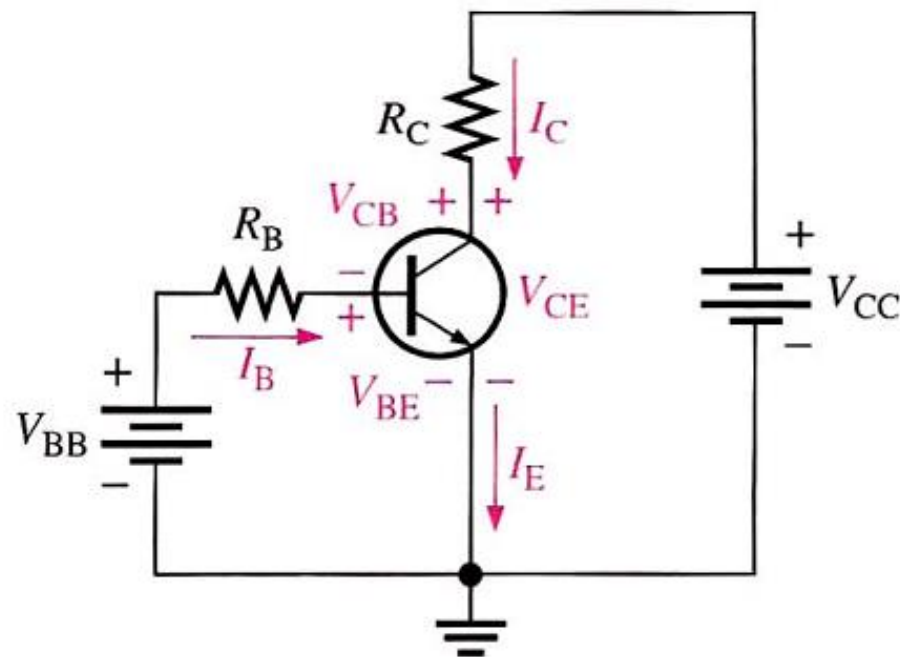
$$V_{CE} = V_{CC} - R_C \cdot I_C = V_{CC} - R_C \cdot (\beta_{DC} \cdot I_B)$$


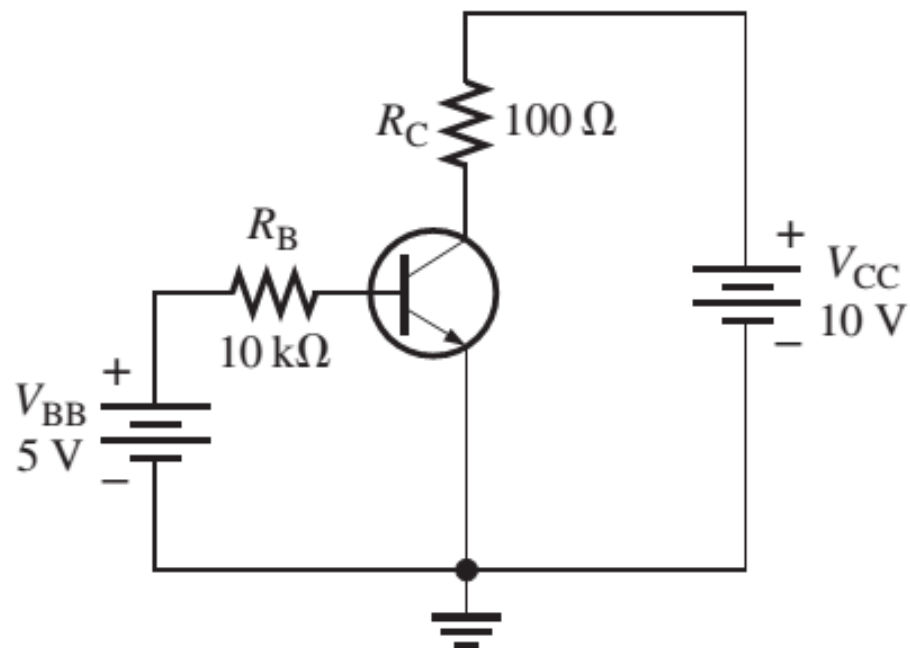
# Exercise 1

- Determine  $I_B, I_C, I_E, V_{BE}, V_{CE}$  and  $V_{CB}$  for the given circuit when  $\beta_{DC} = 150$






# Solution 1

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5\text{ V} - 0.7\text{ V}}{10\text{ k}\Omega} = 430\text{ }\mu\text{A}$$

$$I_C = \beta_{DC} I_B = (150)(430\text{ }\mu\text{A}) = 64.5\text{ mA}$$

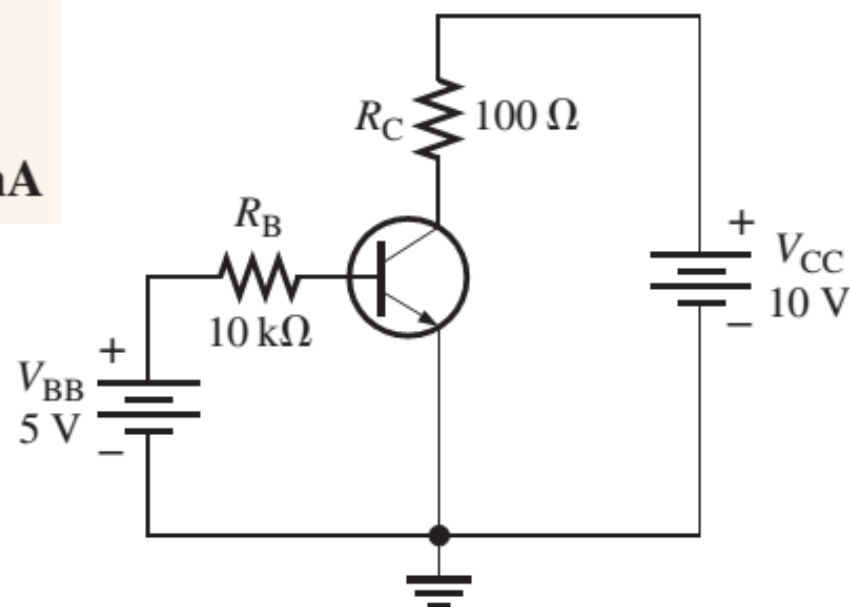
$$I_E = I_C + I_B = 64.5\text{ mA} + 430\text{ }\mu\text{A} = 64.9\text{ mA}$$



$$V_{CE} = V_{CC} - I_C R_C = 10\text{ V} - (64.5\text{ mA})(100\text{ }\Omega) = 10\text{ V} - 6.45\text{ V} = 3.55\text{ V}$$


$$V_{CB} = V_{CE} - V_{BE} = 3.55\text{ V} - 0.7\text{ V} = 2.85\text{ V}$$

## Exercise 2

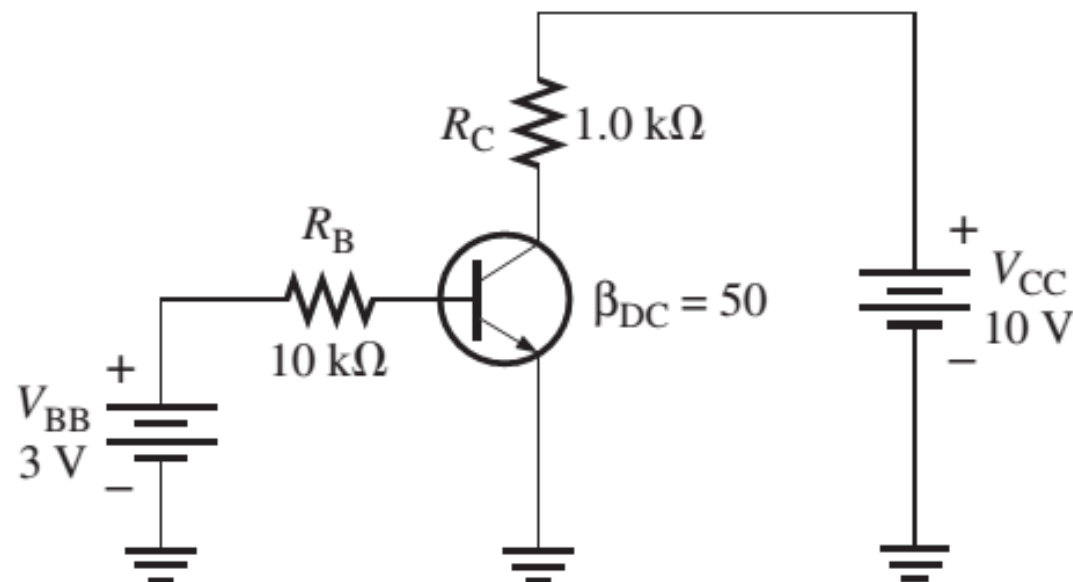

- Determine  $I_B, I_C, I_E, V_{BE}, V_{CE}$  and  $V_{CB}$

# Solution 2

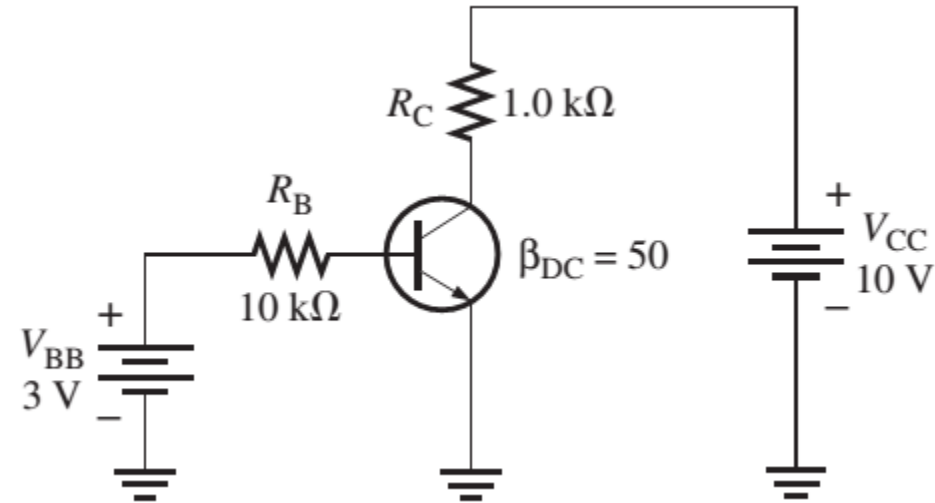

- Assume that the circuit is working linearly

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{3\text{ V} - 0.7\text{ V}}{10\text{ k}\Omega} = \frac{2.3\text{ V}}{10\text{ k}\Omega} = 0.23\text{ mA}$$


$$I_C = \beta_{DC} I_B = (50)(0.23\text{ mA}) = 11.5\text{ mA}$$

# Solution 2

- $I_C = (V_{CC} - V_{CE}) / R_C$
- Saturation Mode


# Exercise 3


- Determine  $\beta_{DC}$

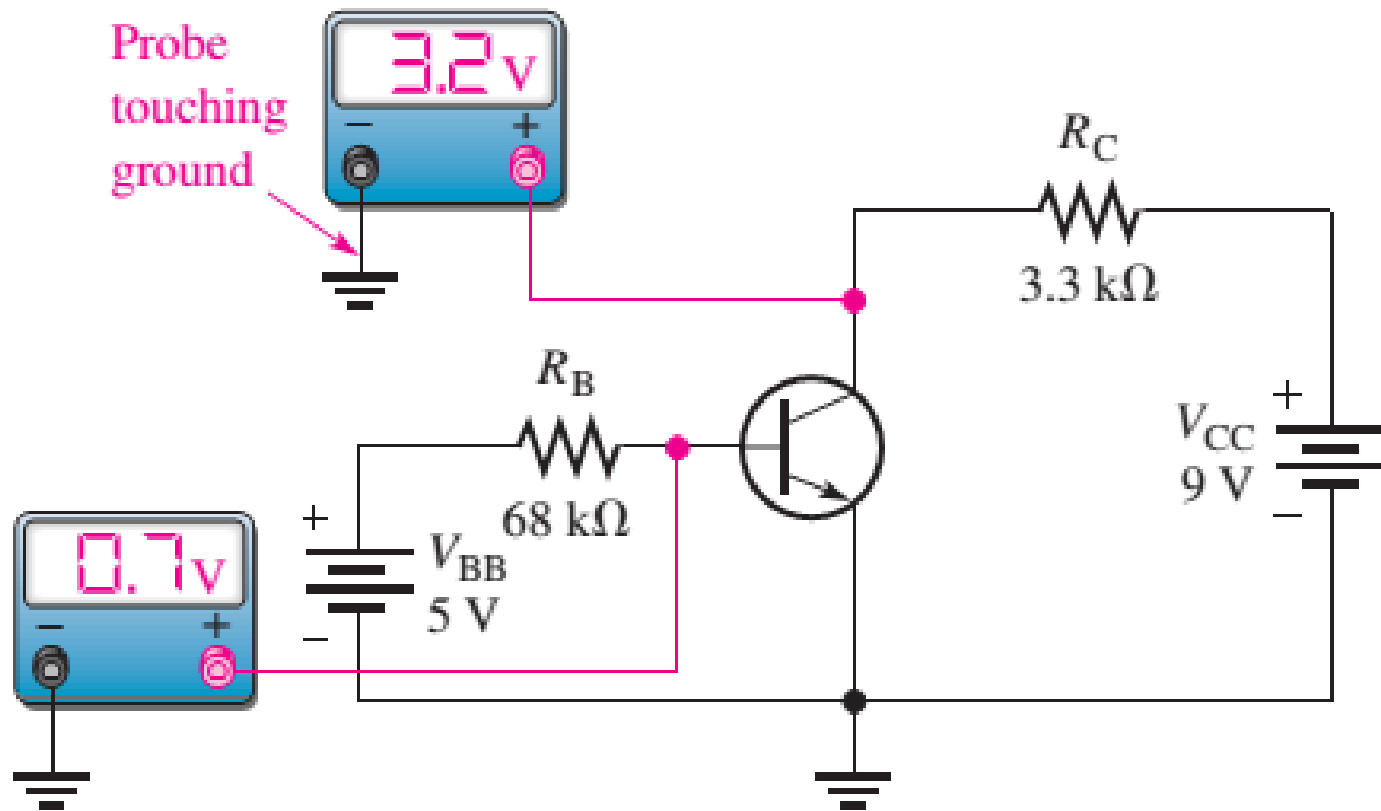


# Exercise 4

- Explain why  $V_C$  is 15V

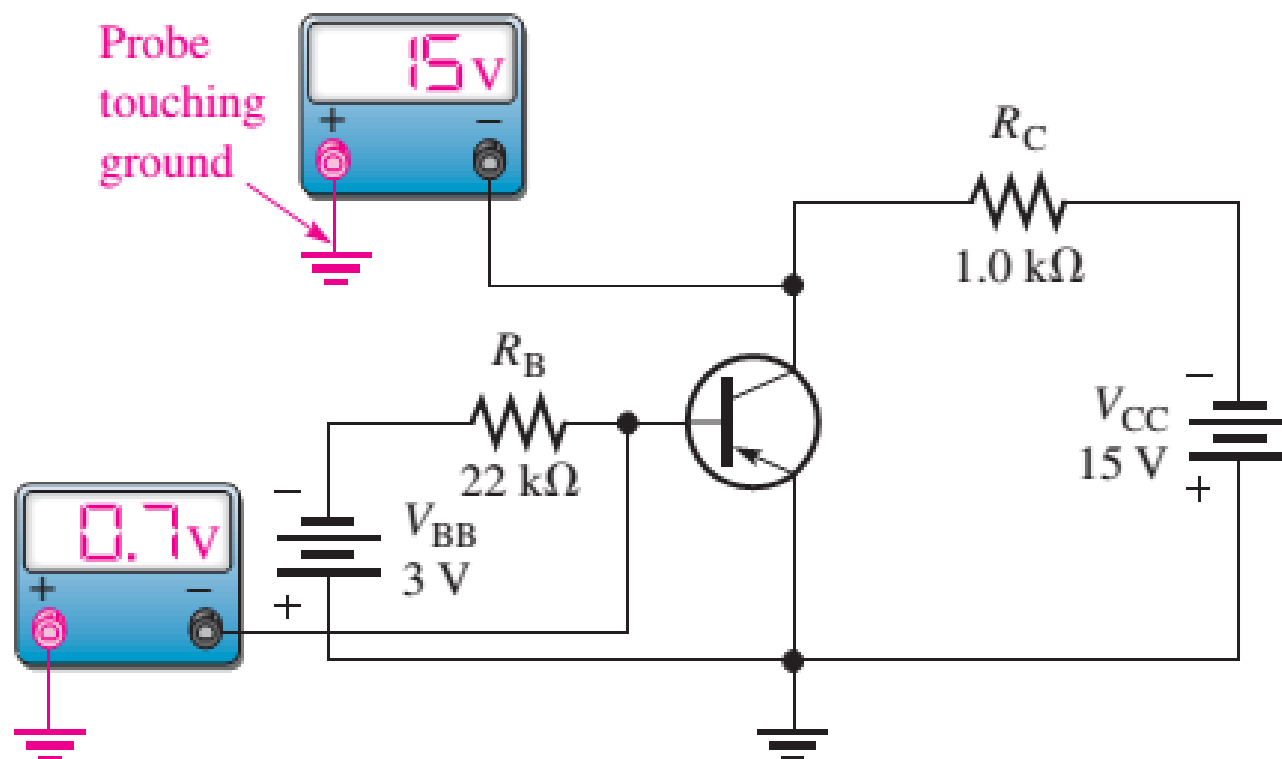

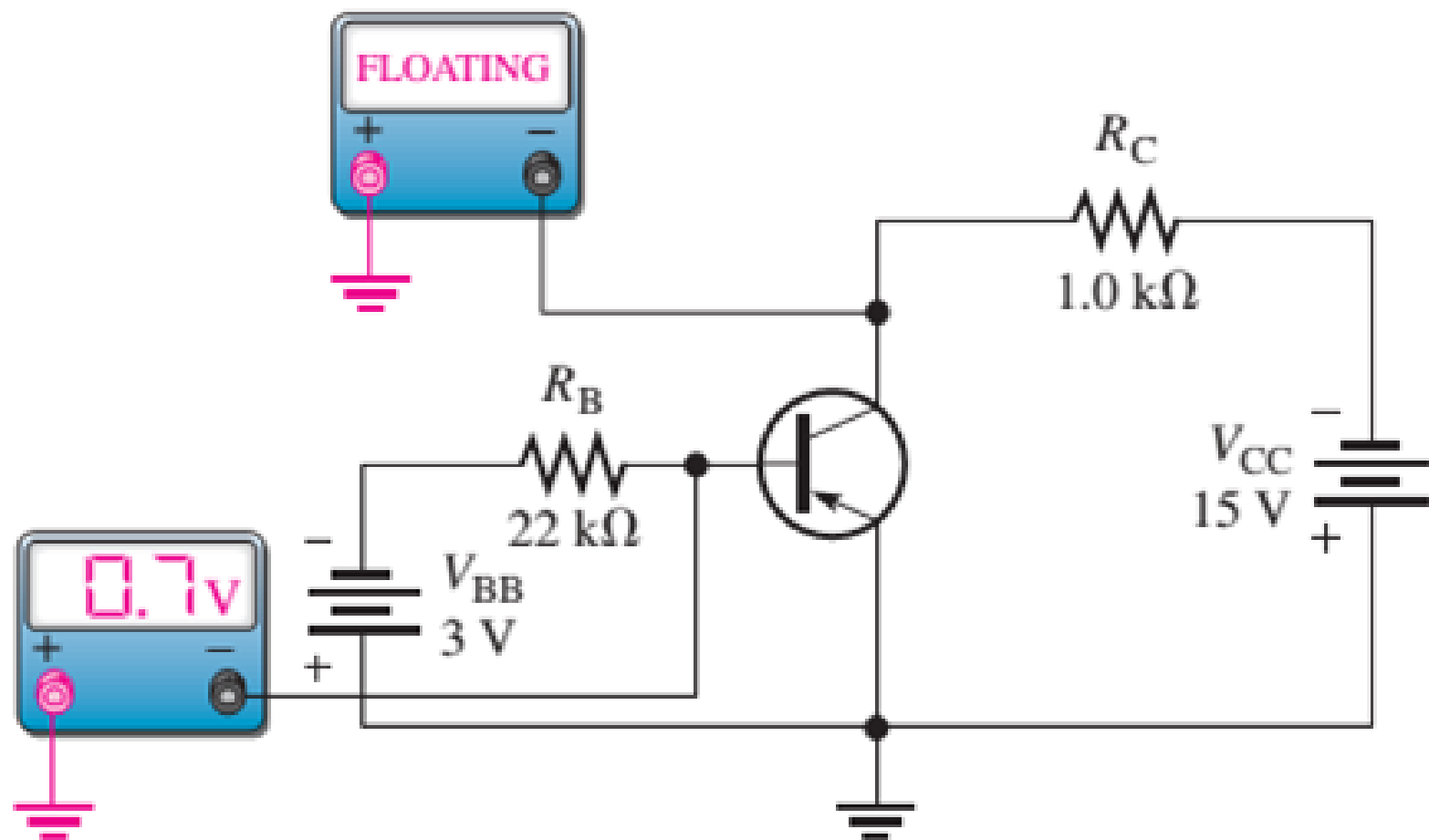


# Exercise 4

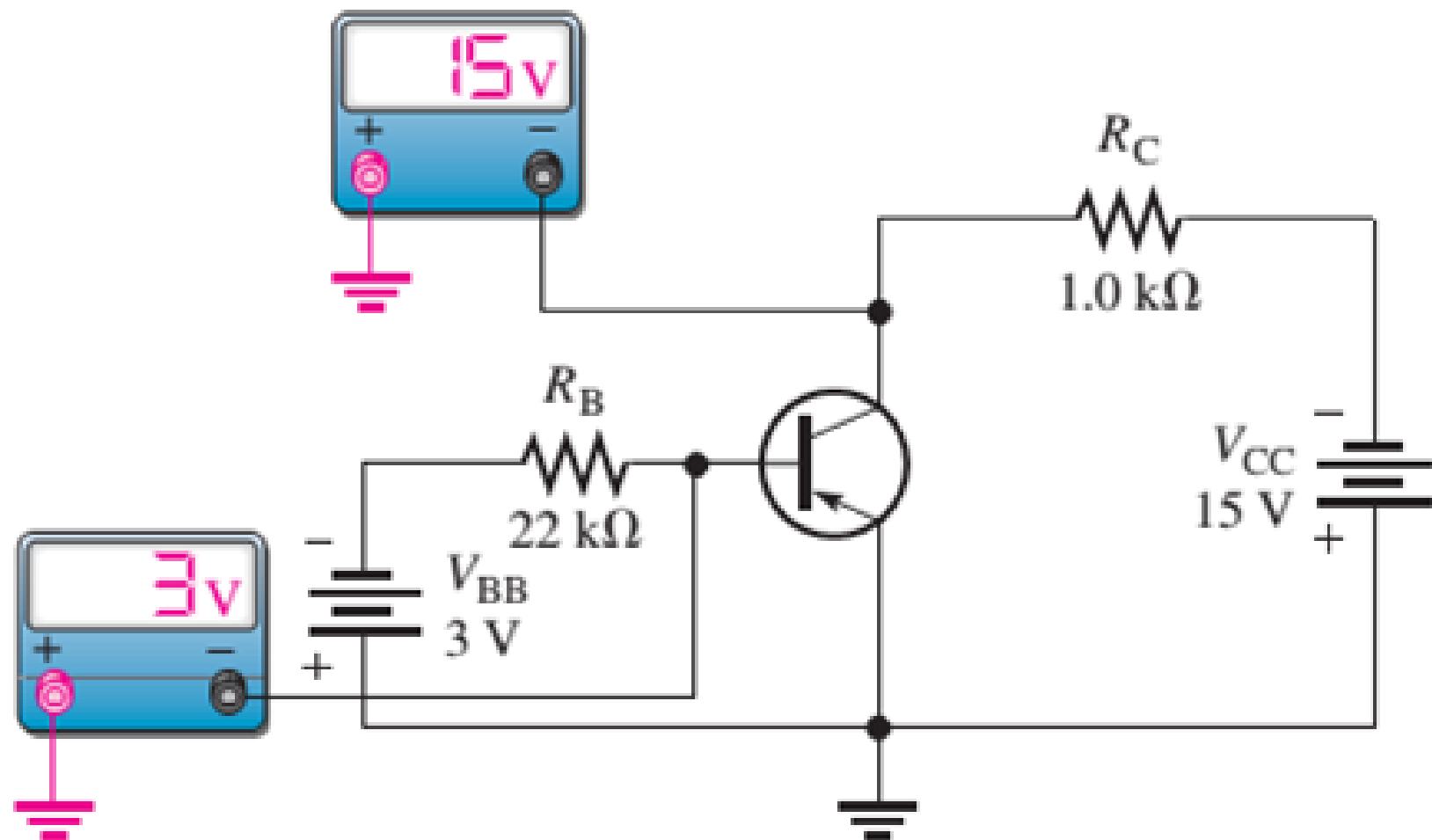





(d)




# Exercise 4

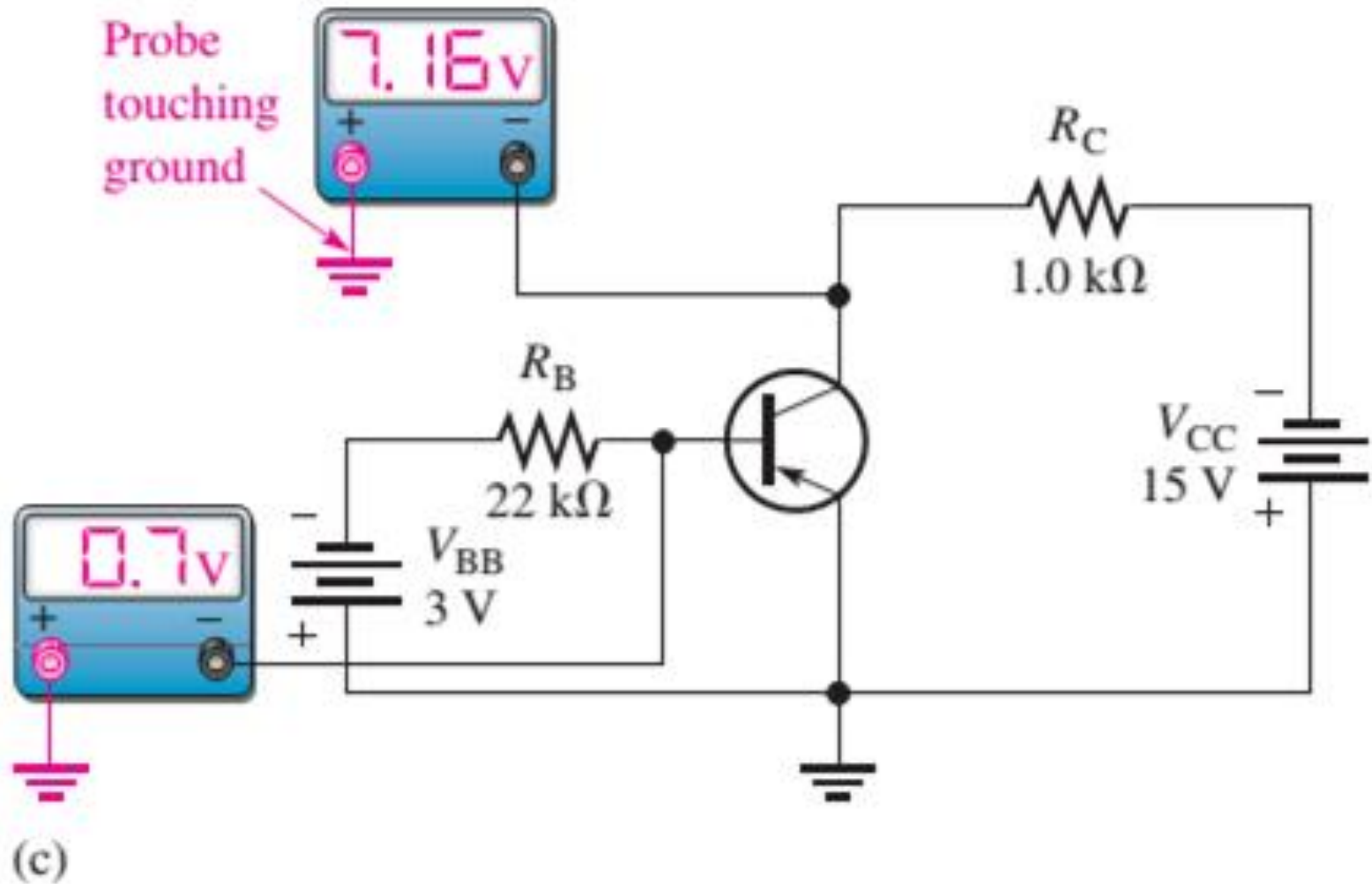

# Exercise 4

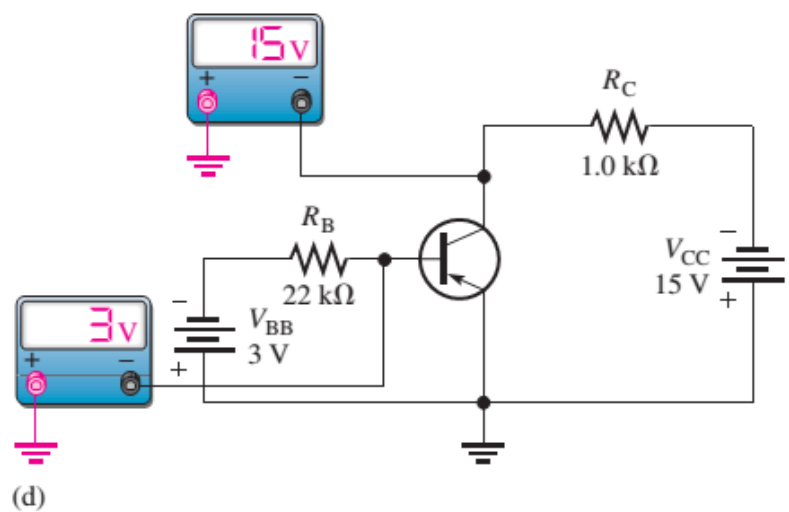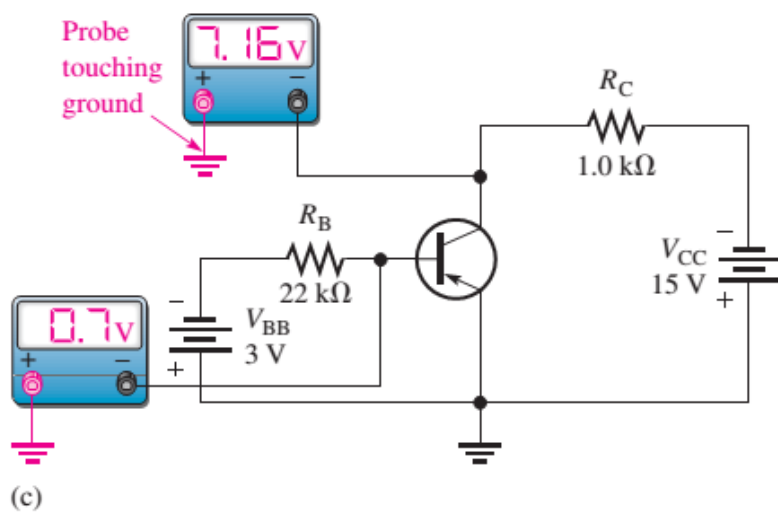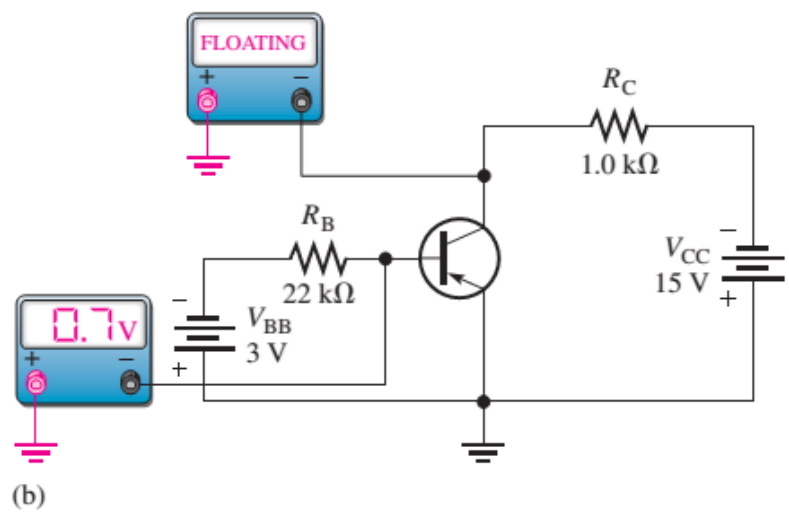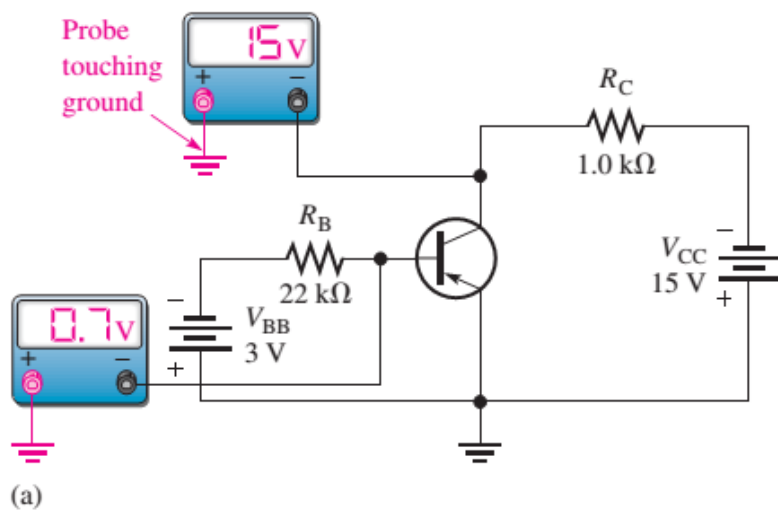

# Exercise 5

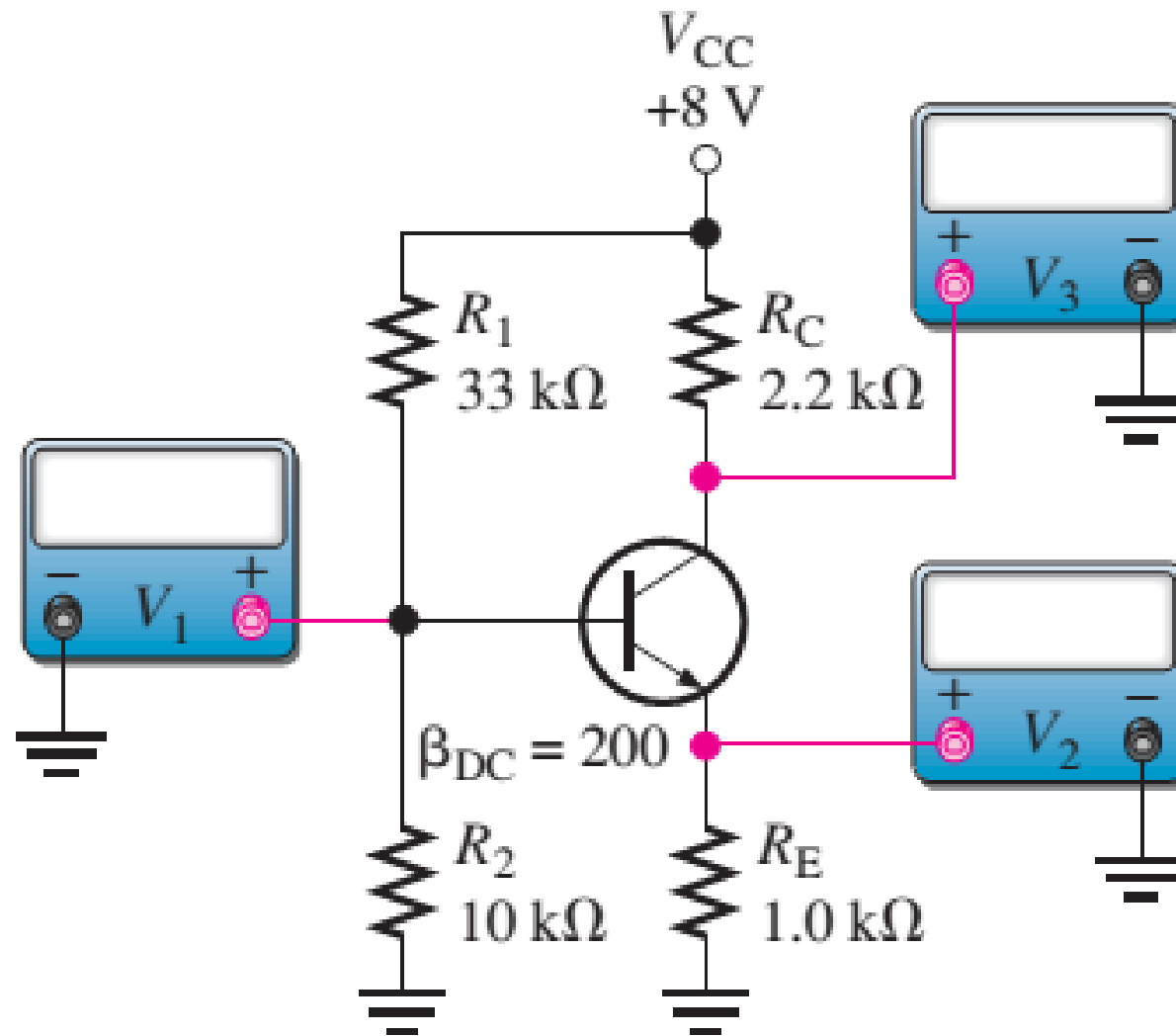

# Midterm (45 mins – Closed Book)

- Multichoice + Written
- Chapter 1: Basic Electronic Components
  - Determine the resistor values (4-band colors, 5-band colors)
  - LEDs connectors (Serial + Parallel)
- Chapter 2: Diode
  - Diode Principles and Models
  - Applications using Diodes
- Chapter 3: BJT (npn)
  - Amplifier Coefficient, Applications
  - $V_{be} = 0.7$  (for default)