
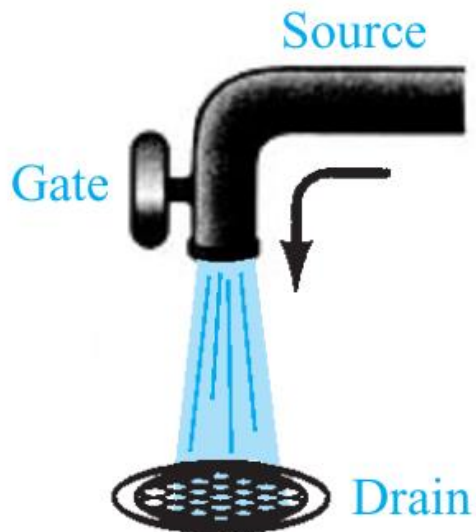


C02015


Field Effect Transistor

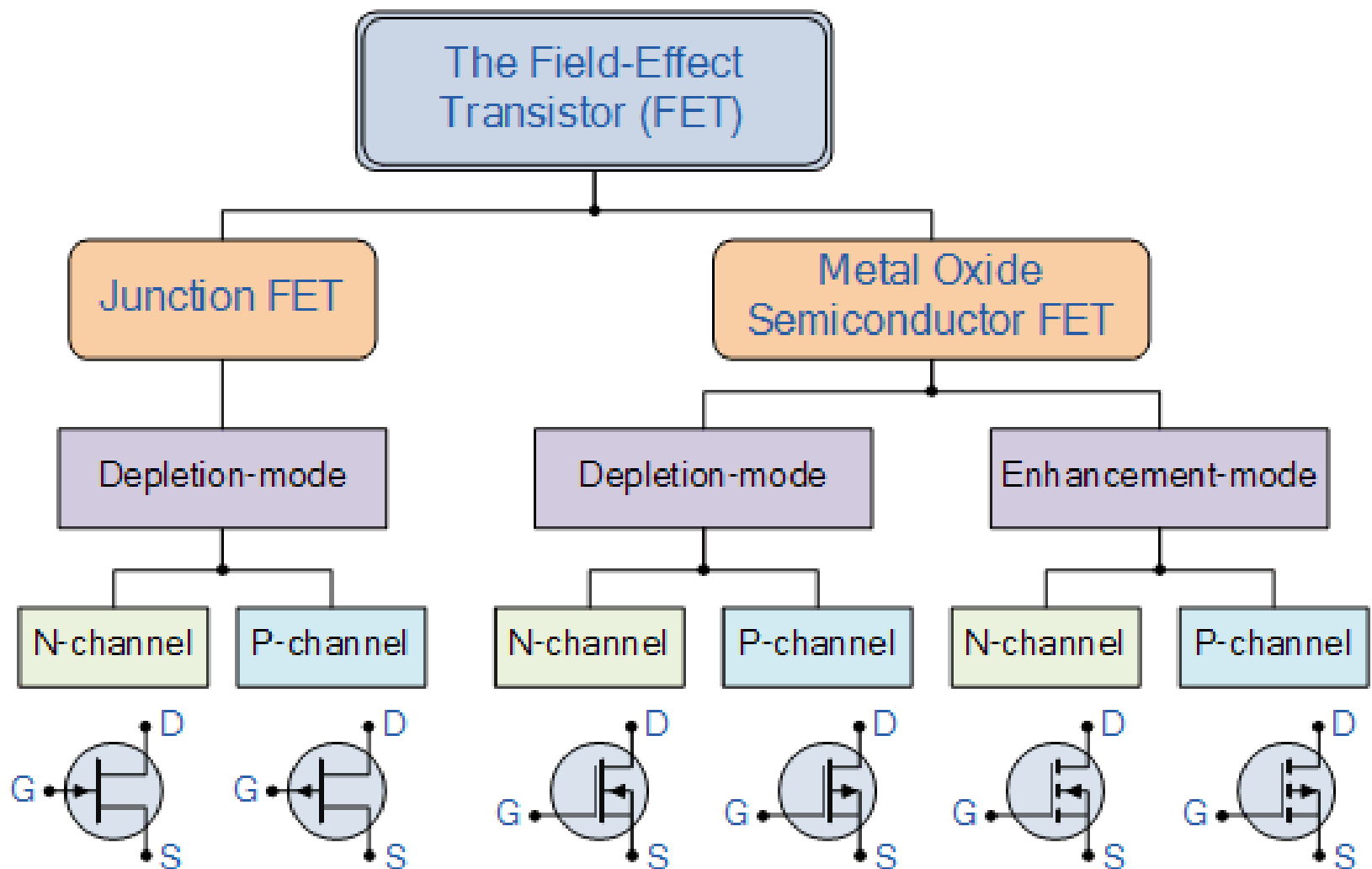


Field-Effect Transistor (FET)





JFET

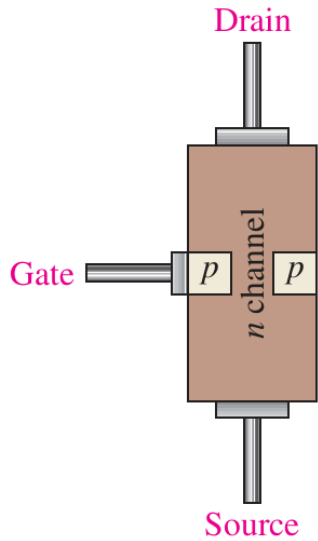

(a) *n* channel

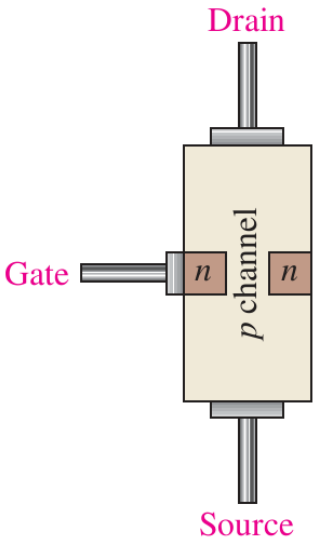


(b) *p* channel




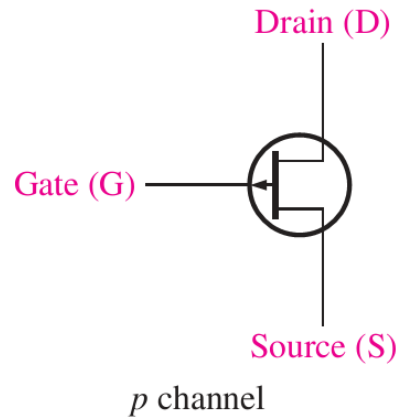
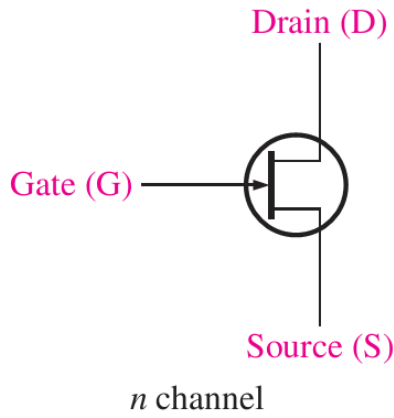


JFET Operations

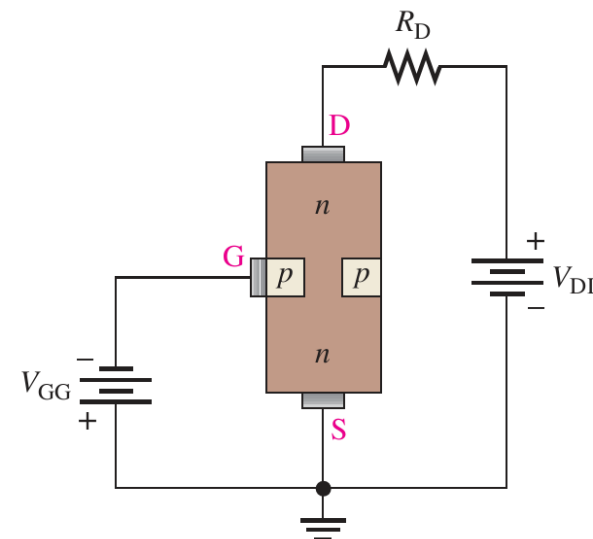- G and S always in reversed-bias:
 - V_{GS} is negative: Depletion area is increased → Resistance between D and S is increased
 - V_{GS} is increased (to Zero): Depletion area is decreased → Resistance between D and S is decreased
- G and S is in forward-bias:
 - JFET likes a resistor



JFET Operations

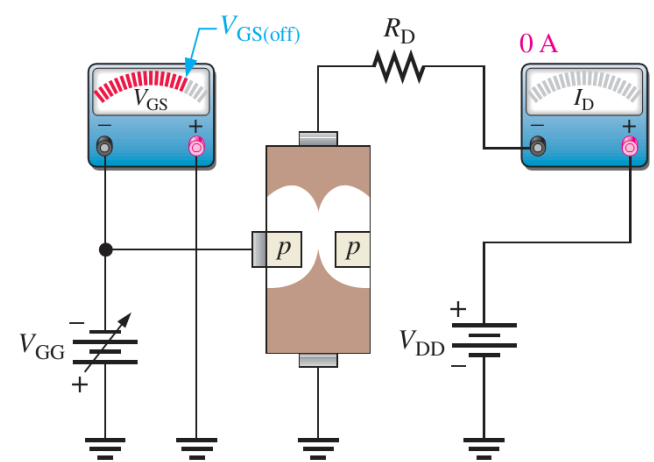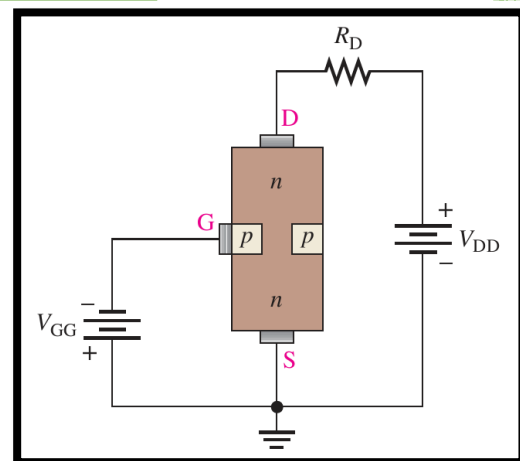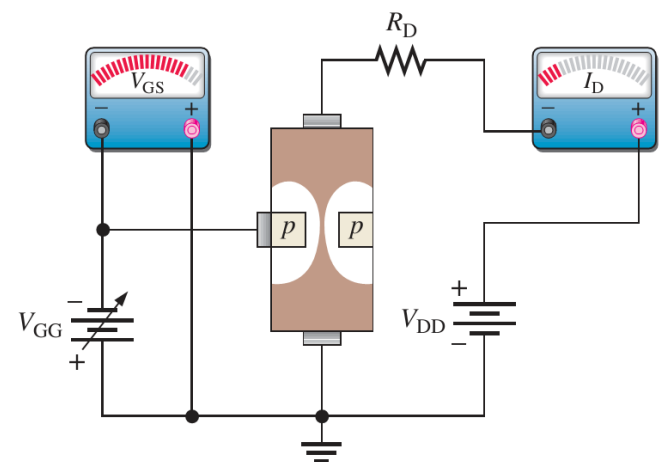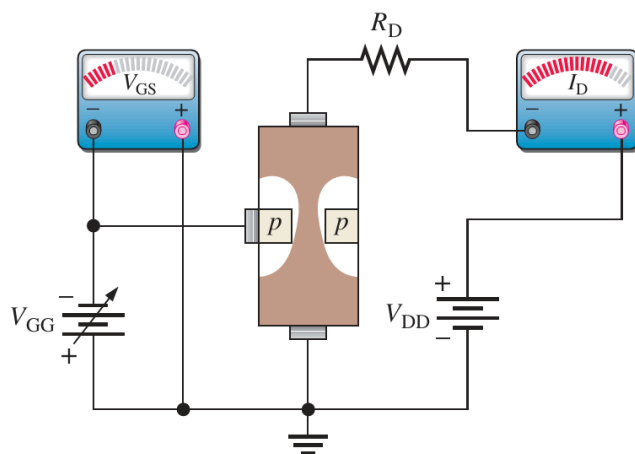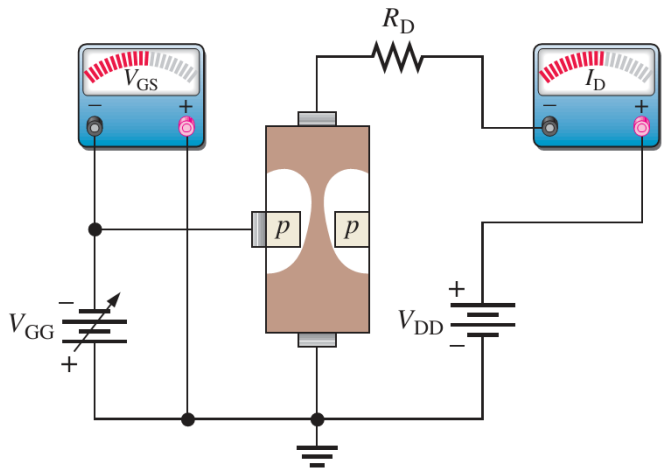


JFET Characteristics

- JFET n-channel has three operation modes when $V_{DS} > 0$

A. $V_{GS} = 0$, JFET is in saturation, $I_D = \text{Max}$





B. $V_{GS} < 0$, JFET is in linear status, $I_D \downarrow$

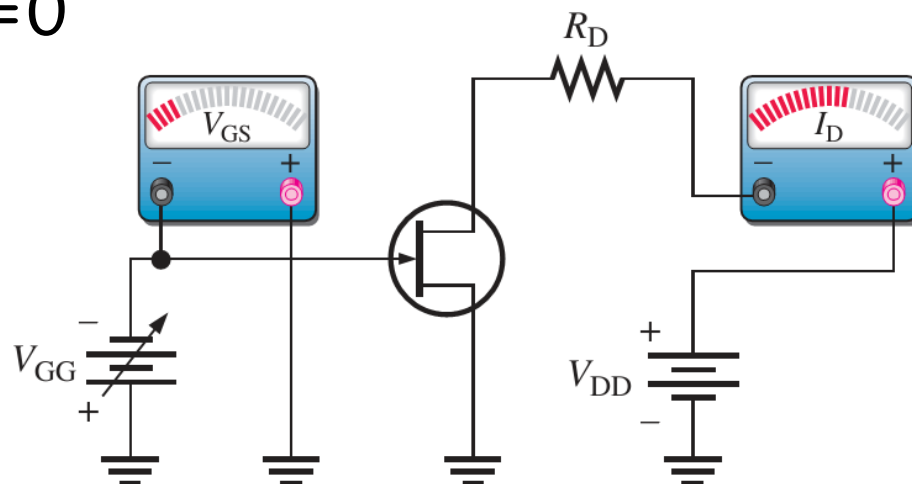C. $V_{GS} = -V_{\text{off}}$, JFET is OFF, $I_D = 0$





JFET Saturation Mode

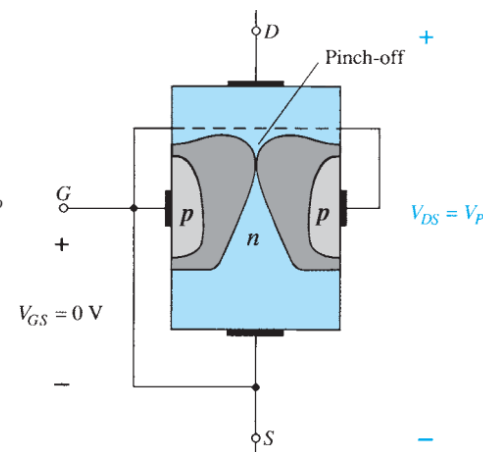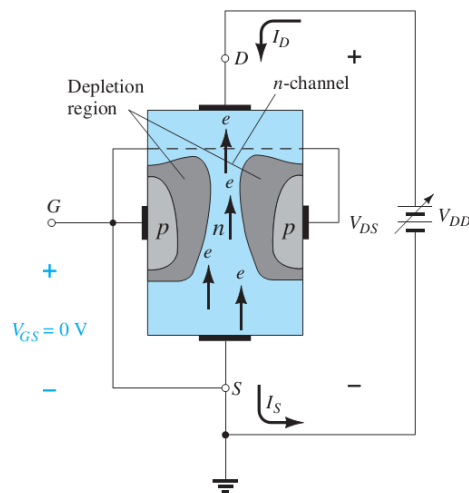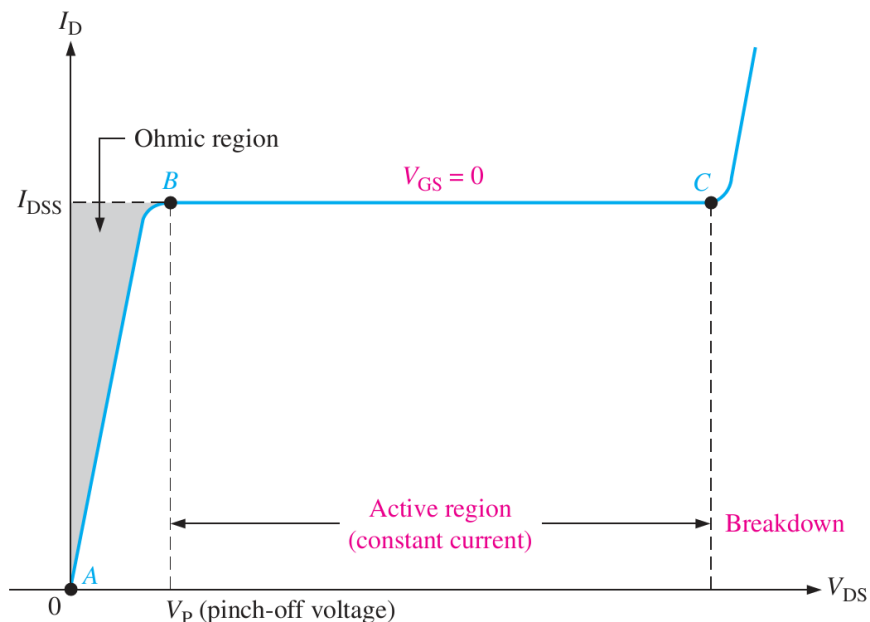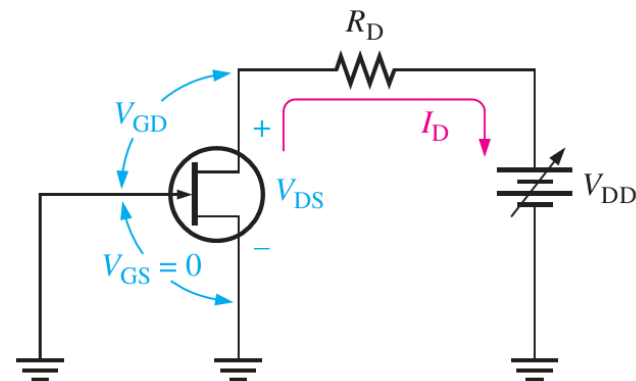
- $V_{GS} = 0V$, V_{DD} is increased slowly
 - Linear region A-B: $V_{DS} = R I_D$
 - Saturation region B-C: I_D is constant
 - Pinch off region due to the increase of depletion area.






Cut-off State

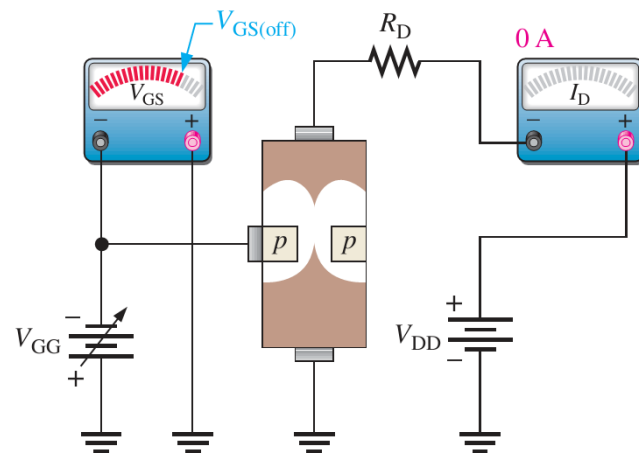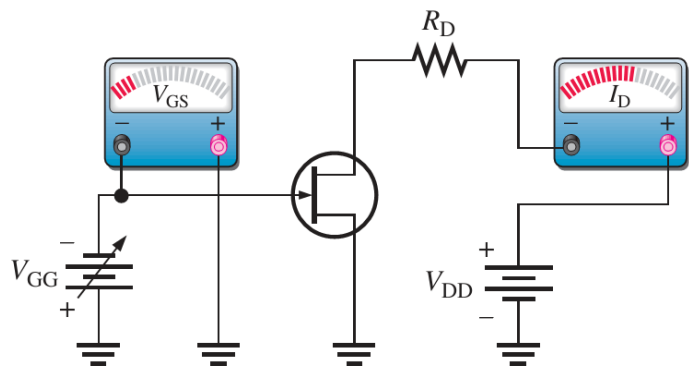

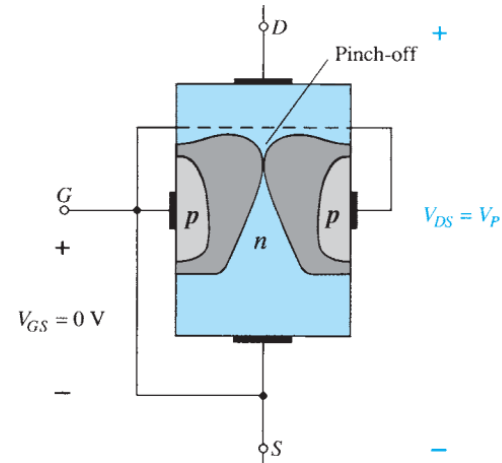- Reversed-bias: $0 < V_{GS} < V_{GS(off)}$
 - Depletion area is increased \rightarrow closer to Pinch-off state




JFET Characteristic

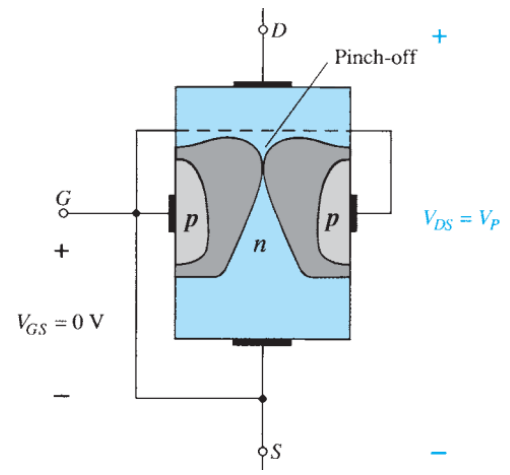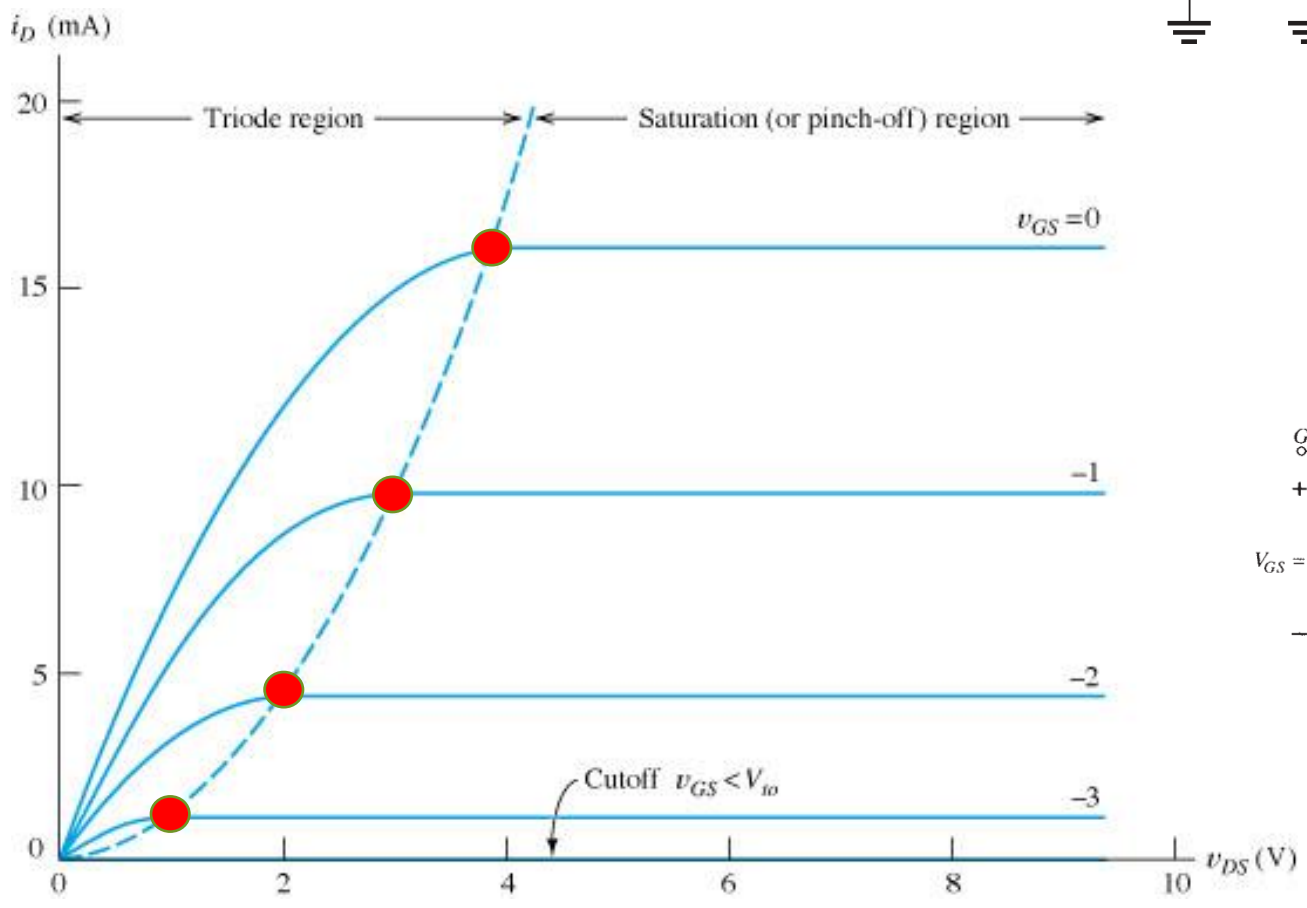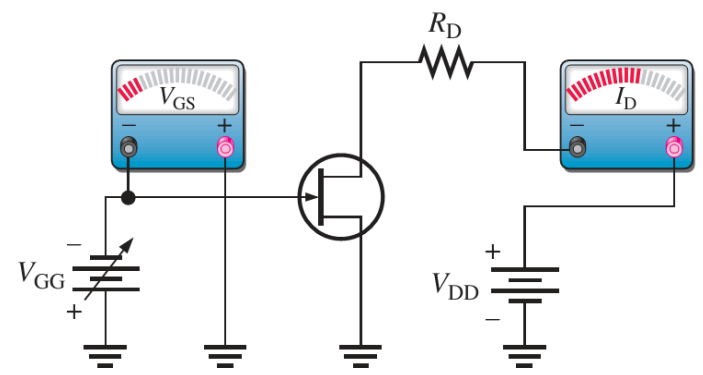



JFET Transfer Curve
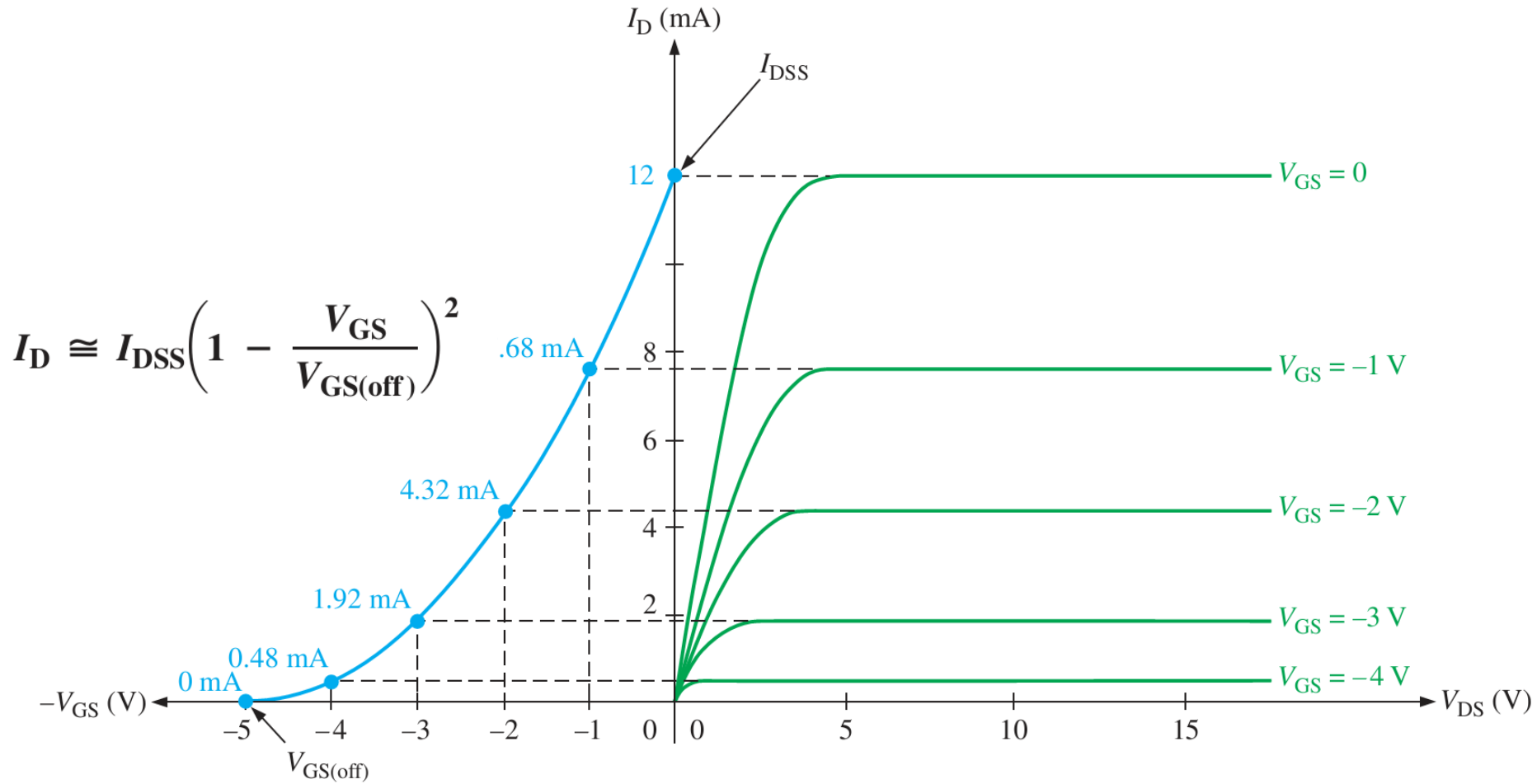
$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$




JFET vs. BJT

<i>JFET</i>		<i>BJT</i>
$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$	\Leftrightarrow	$I_C = \beta I_B$
$I_D = I_S$	\Leftrightarrow	$I_C \cong I_E$
$I_G \cong 0 \text{ A}$	\Leftrightarrow	$V_{BE} \cong 0.7 \text{ V}$

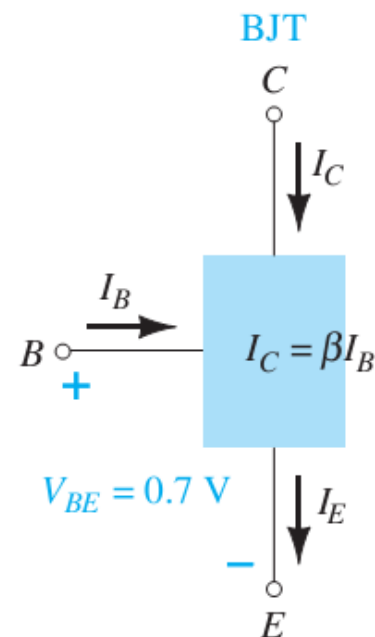
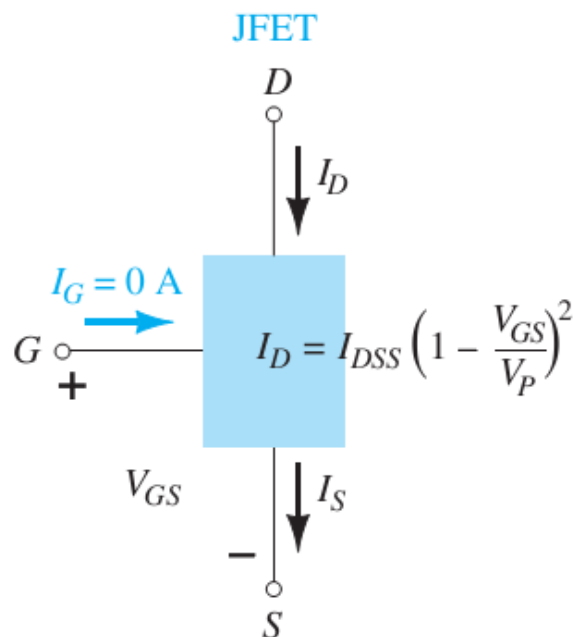


Example


- JFET normal state

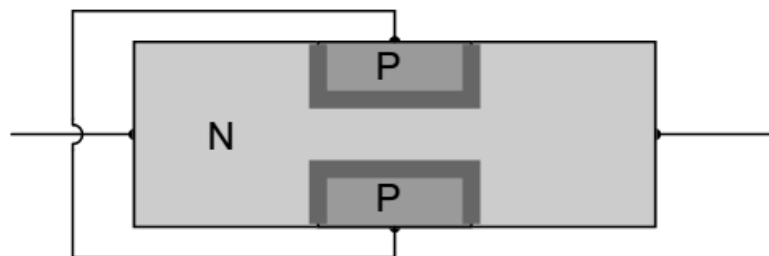

- Determine depletion area in follows:

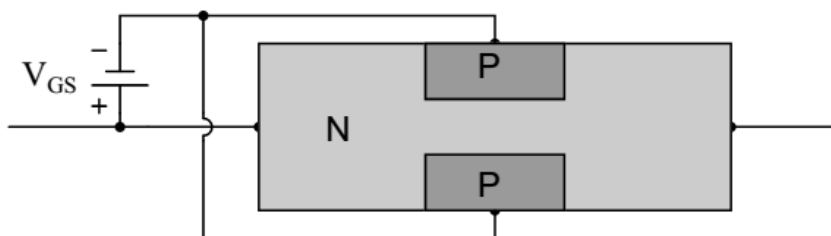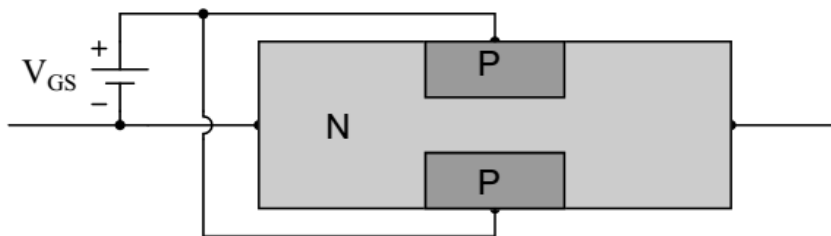


Answer

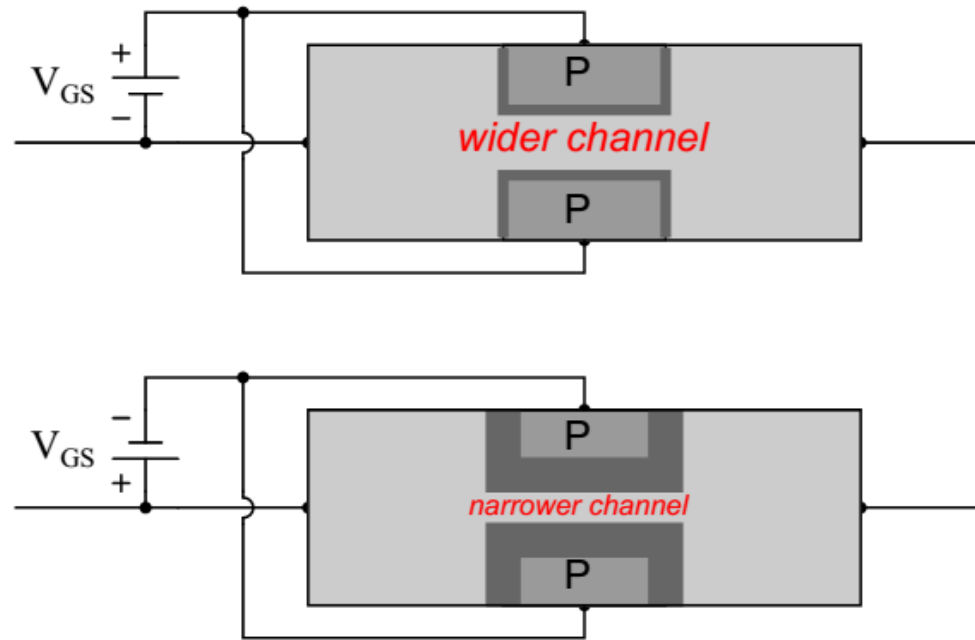

- First figure: Forward-bias \rightarrow depletion area is wider
- Second figure: Inverse-bias \rightarrow depletion area is narrower





Example

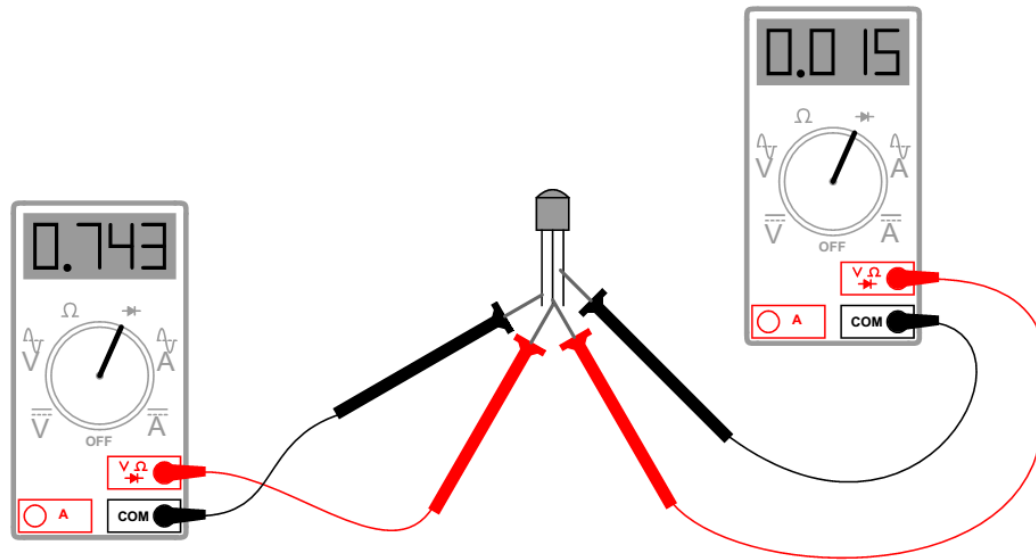





- Determine JFET pins

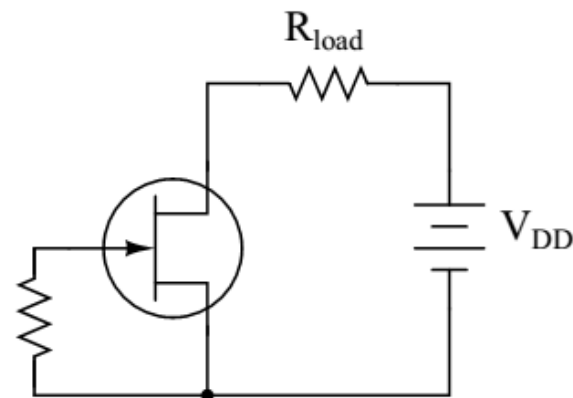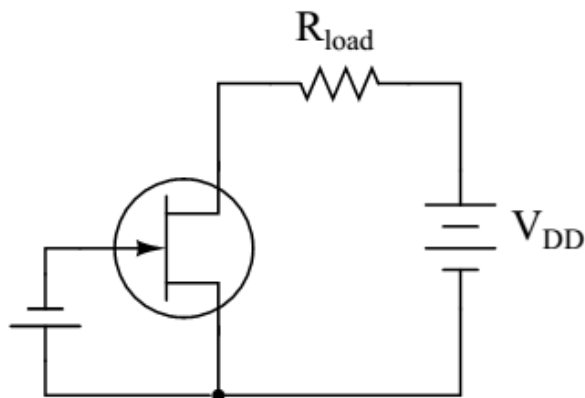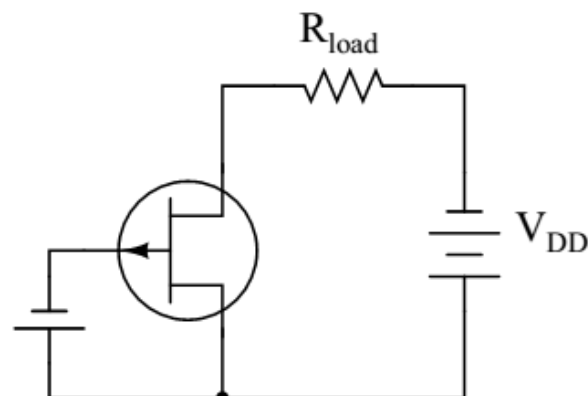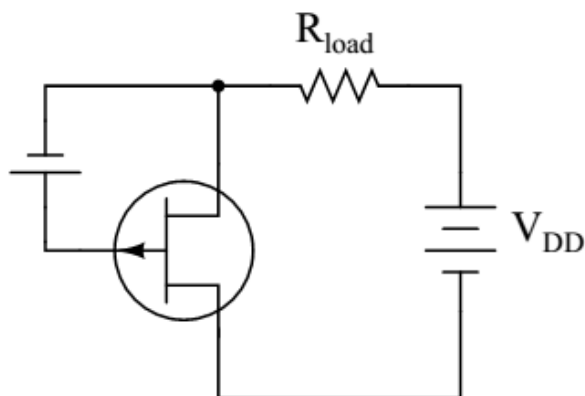Example

- Determine the correct type (p-channel or n-channel) of the following JFETs and its state (ON or OFF)




Answer

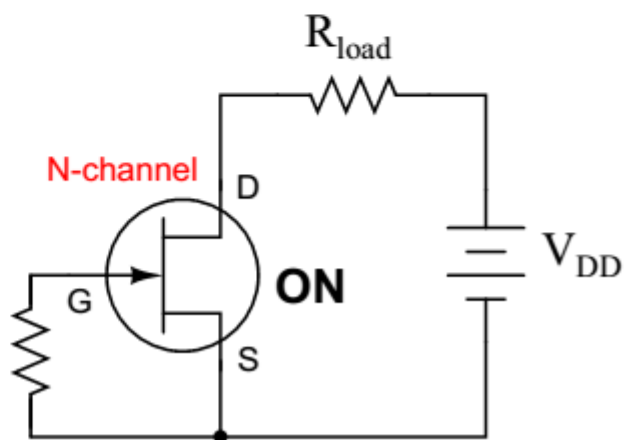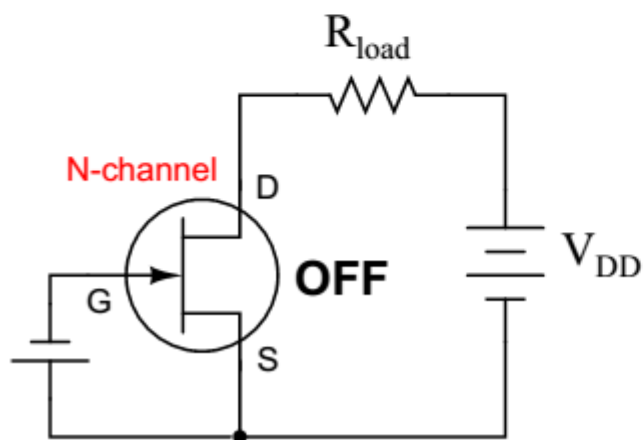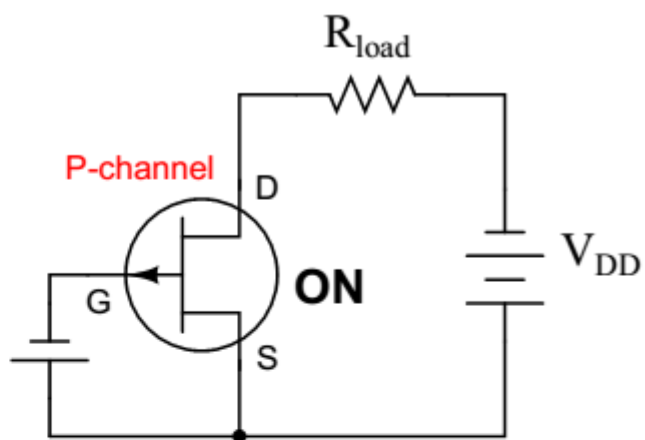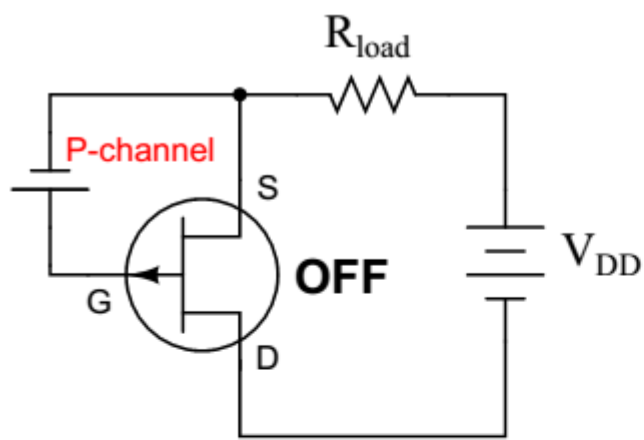

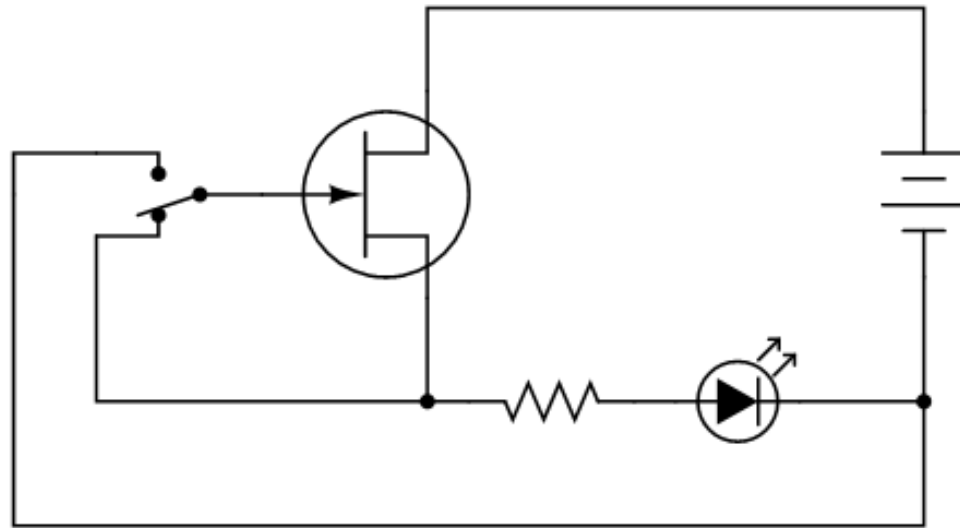
Example

- Determine the LED status (ON or OFF) regarding each position of switch.




Answer

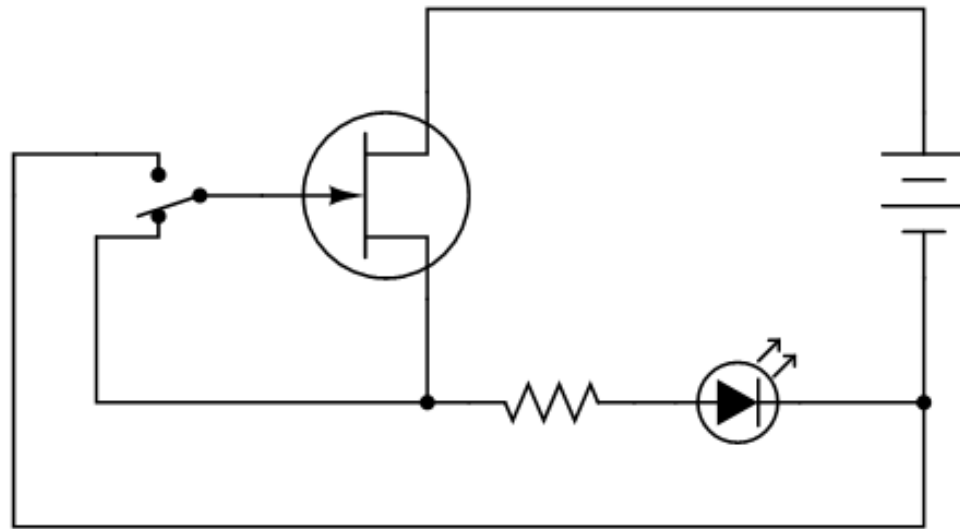- ON State: $V_{GS} = 0V$ (Saturation mode)
- Next: OFF state: Inversed-bias with very negative V_{GS}



Example

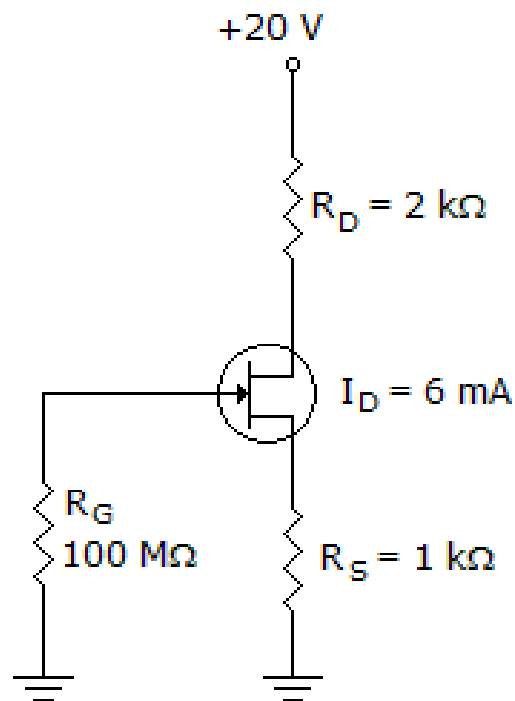

- Determine V_{DS}
- Determine V_S



Answer

- $V_{DS} = V_{DD} - I_D R_D - I_S R_S$

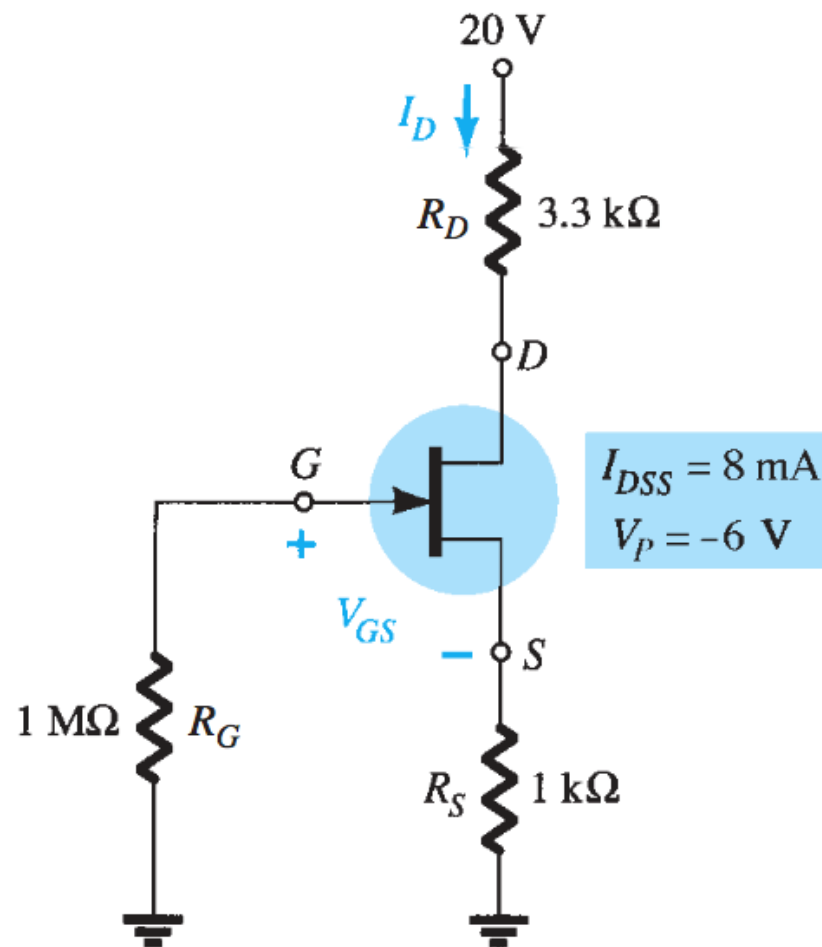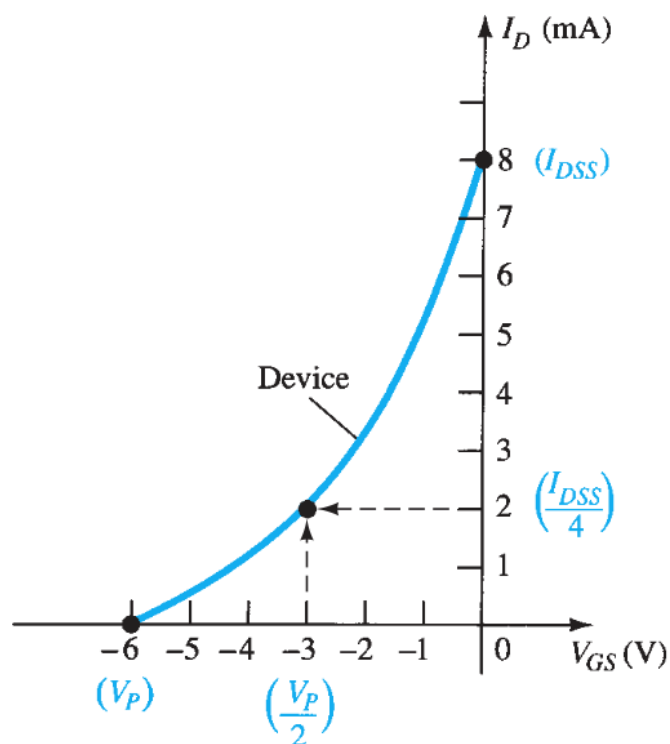Exercise

■ Determine



- V_{GS_Q} .
- I_{D_Q} .
- V_{DS} .
- V_S .
- V_G .
- V_D .



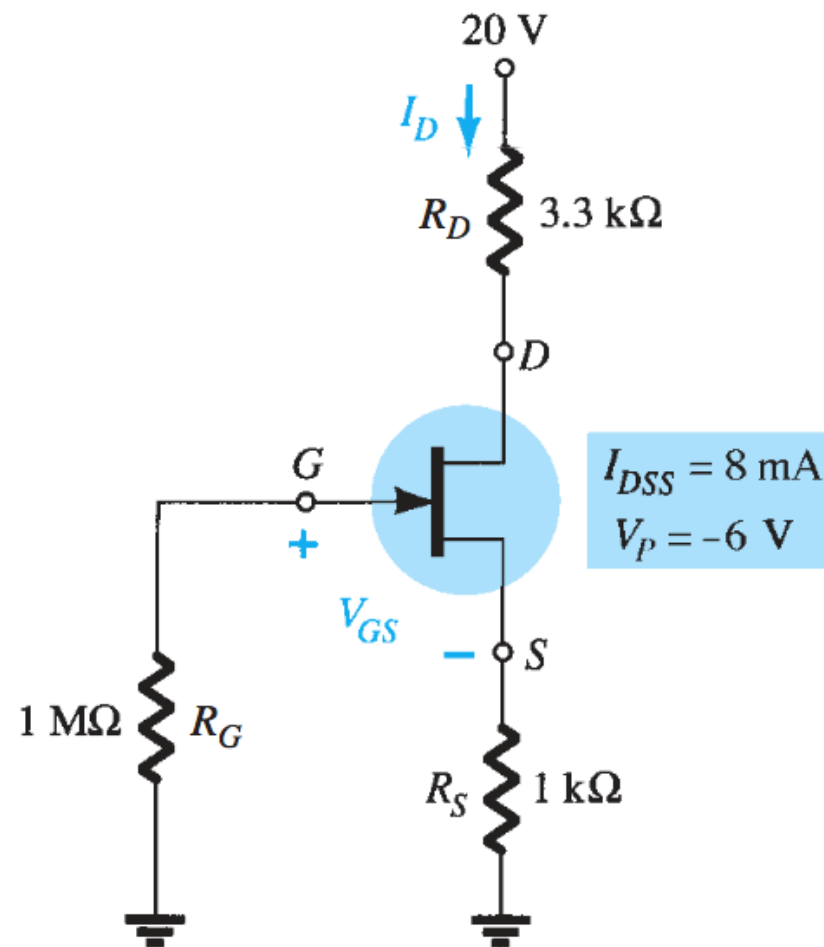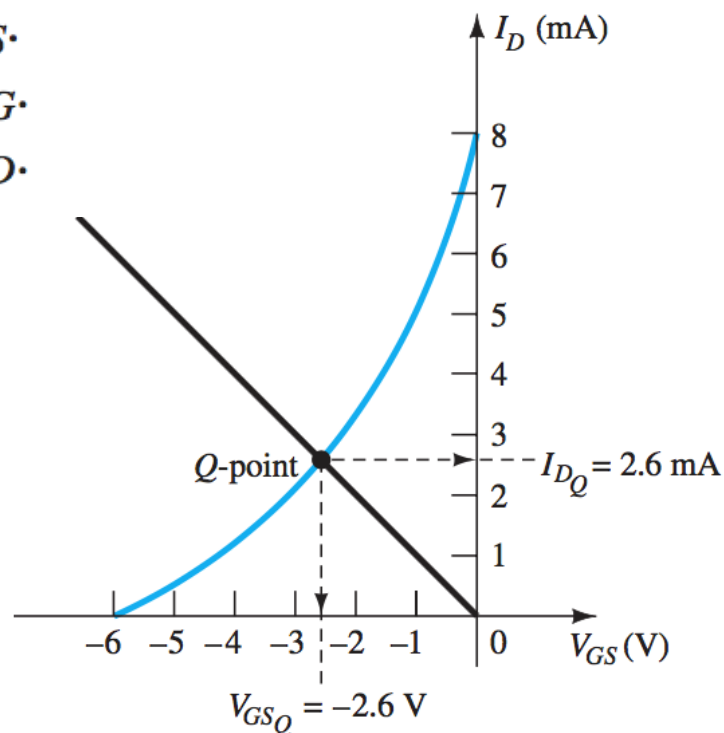Exercise


■ Determine

- V_{GS_Q} .
- I_{D_Q} .
- V_{DS} .
- V_S .
- V_G .
- V_D .



Example

- Determine V_{GS} and I_D

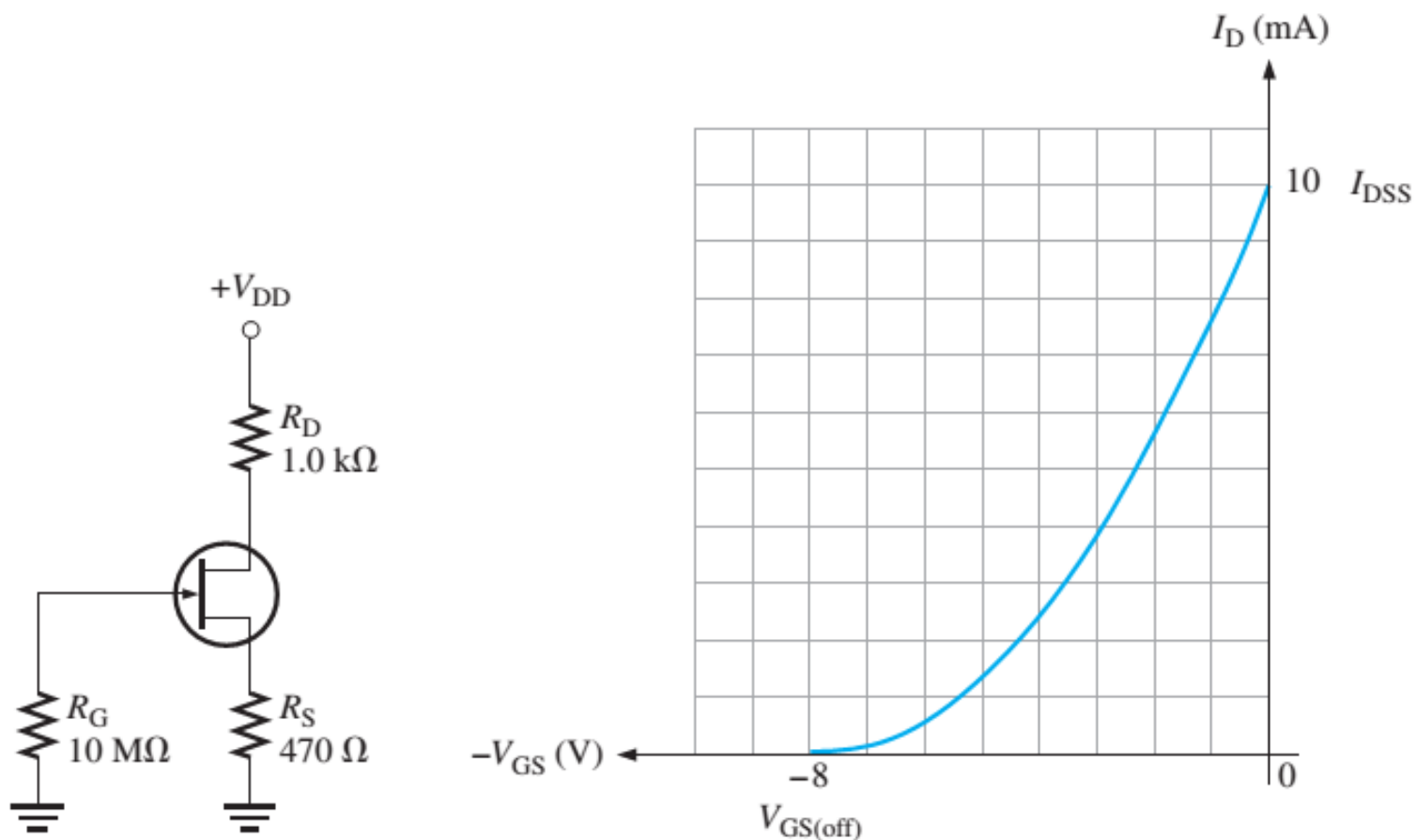

Answer

■ Determine the Load line

■ $I_D = 0$

$$V_{GS} = -I_D R_S = (0)(470 \Omega) = 0 \text{ V}$$



■ $I_D = I_{DSS}$

$$V_{GS} = -I_D R_S = -(10 \text{ mA})(470 \Omega) = -4.7 \text{ V}$$


■ Q is the intersection point of the load line & transfer curve.

• $I_D = 5.07 \text{ mA}$

• $V_{GS} = -2.3 \text{ V}$

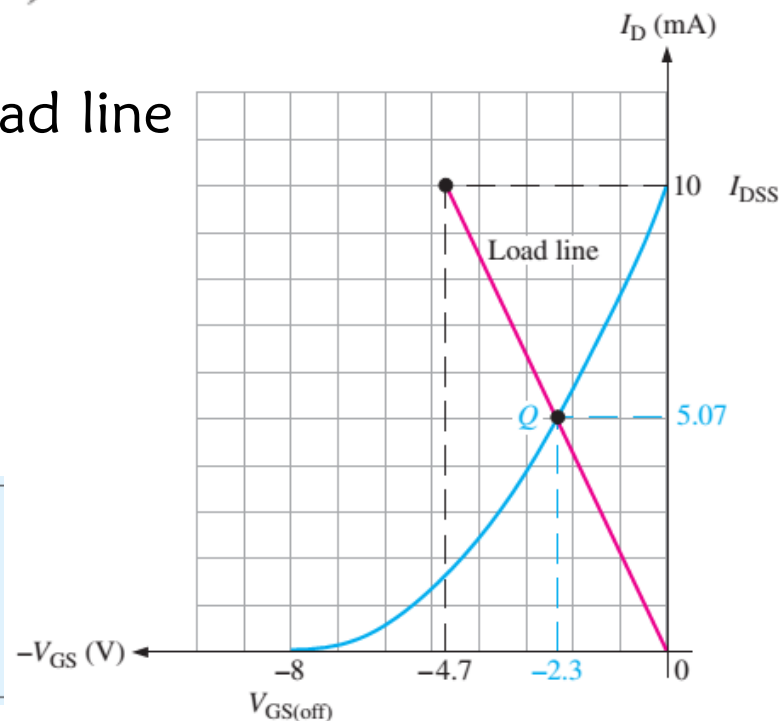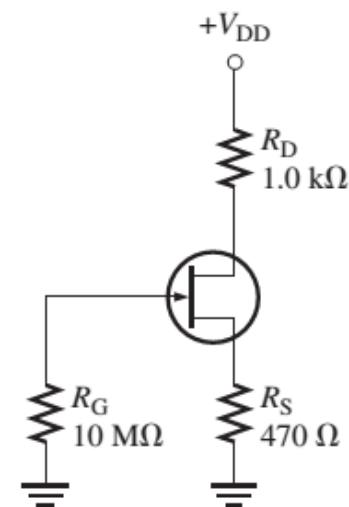

JFET
Self-bias


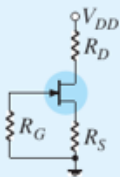


$$V_{GS} = -I_D R_S$$





$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

Home Work


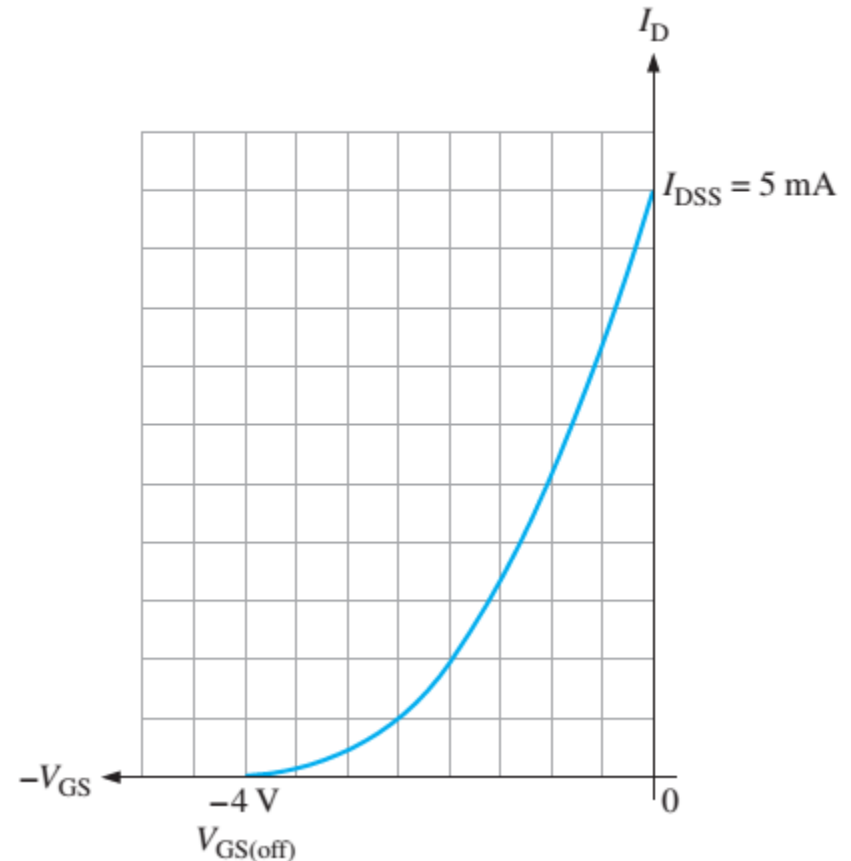
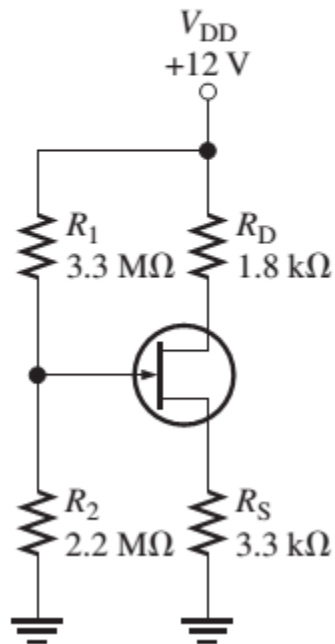
- Determine V_{GS} and V_{DS} for the given JFET, where
 - $I_{DSS} = 5\text{mA}$ and $V_{GS(off)} = -4\text{V}$



D-MOSFET

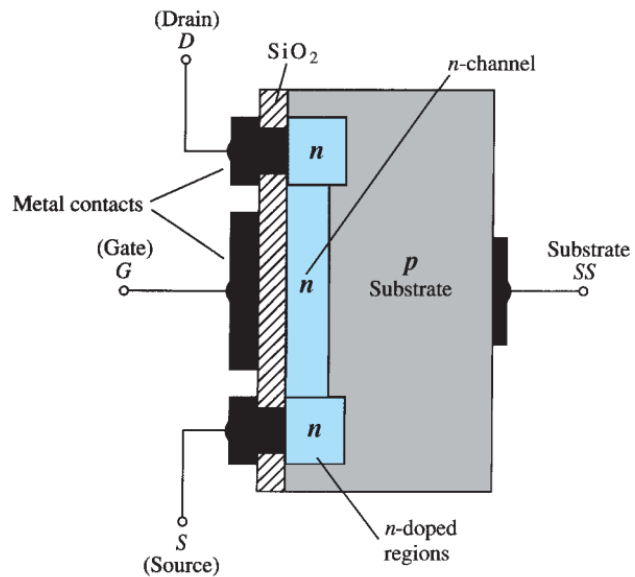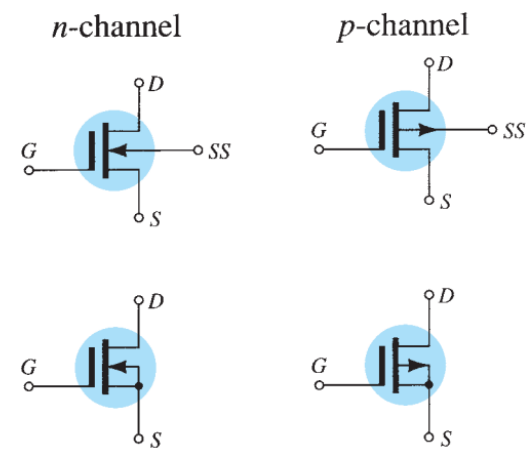
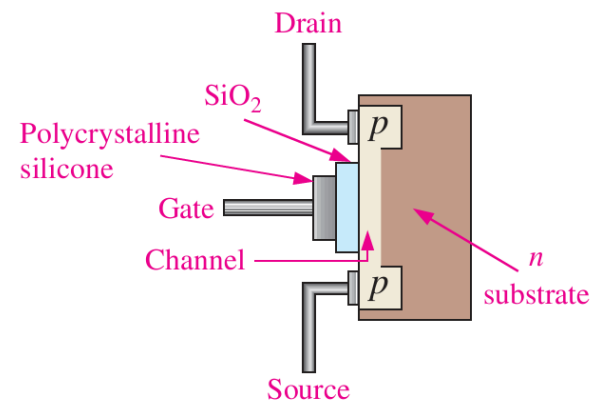
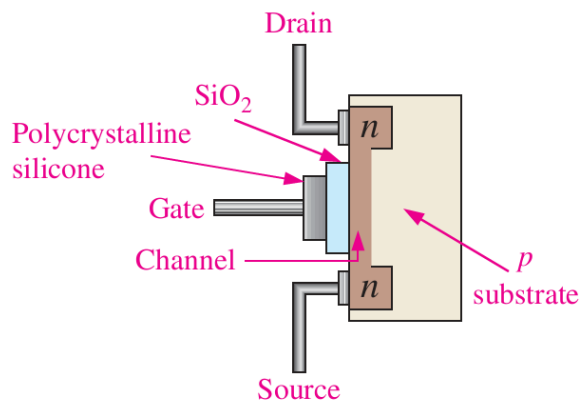


D-MOSFET Operations (N type)



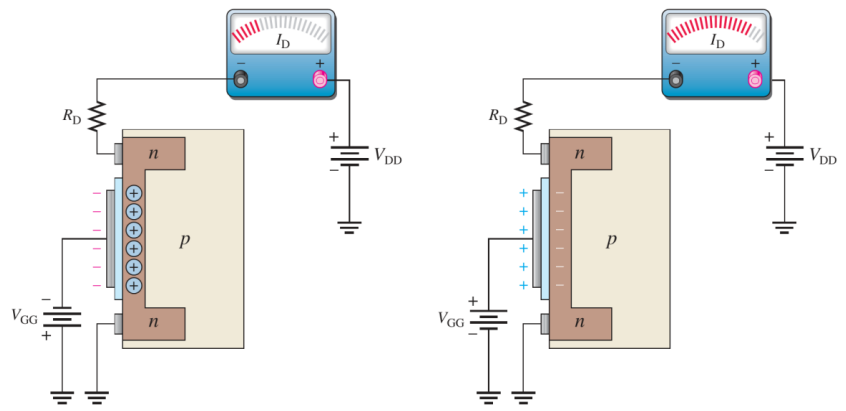
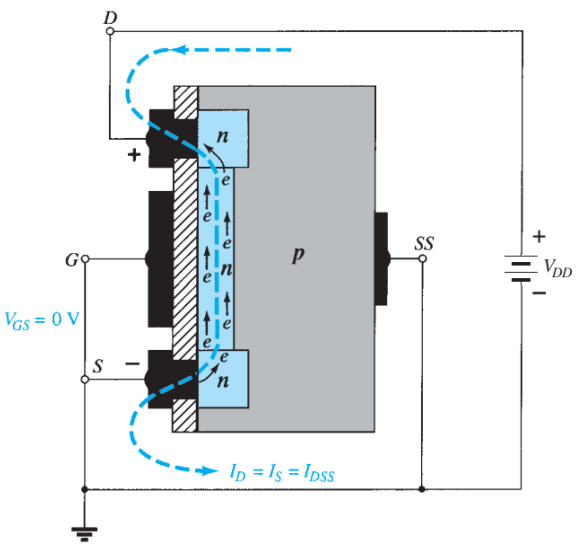
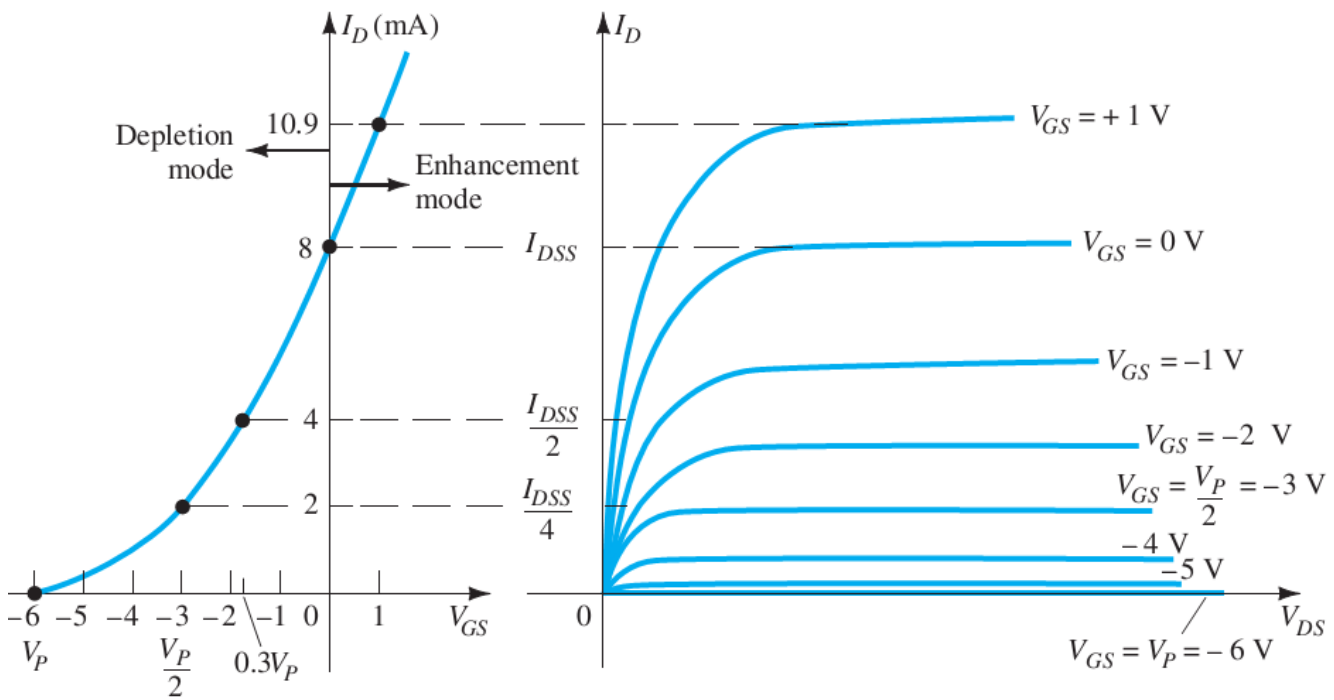


D-MOSFET Operations (P type)

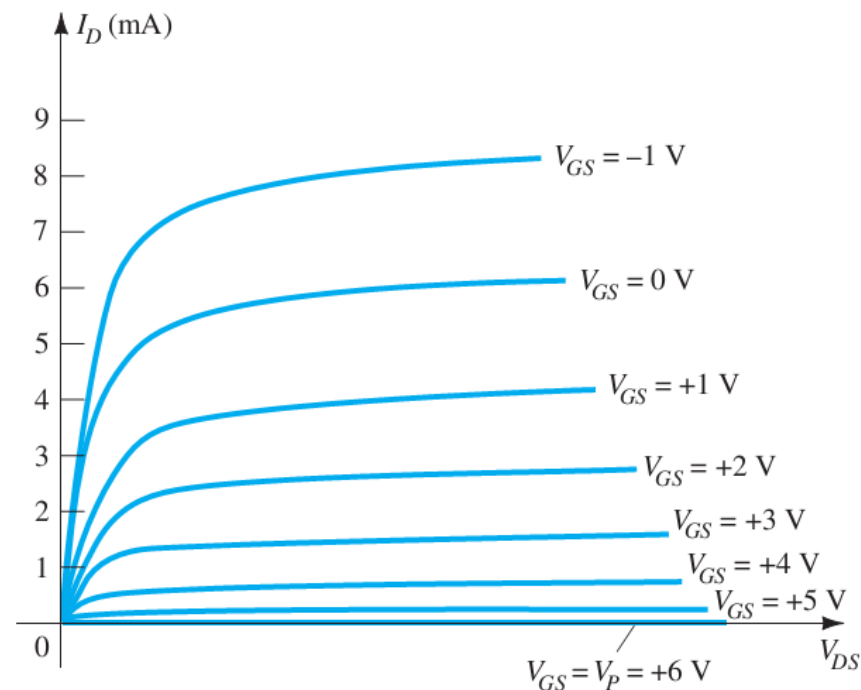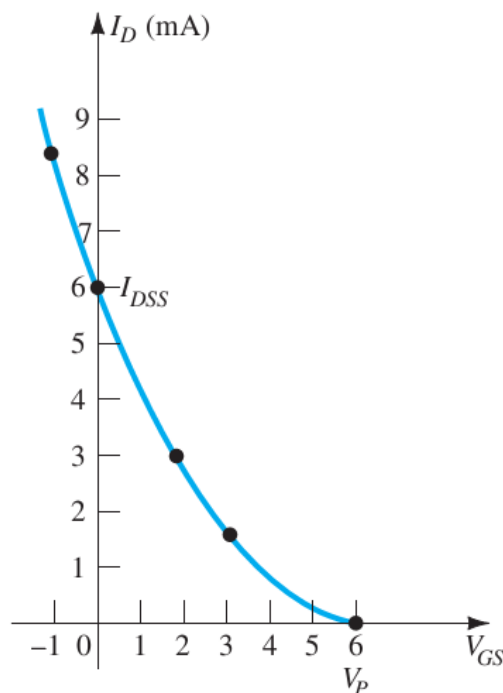
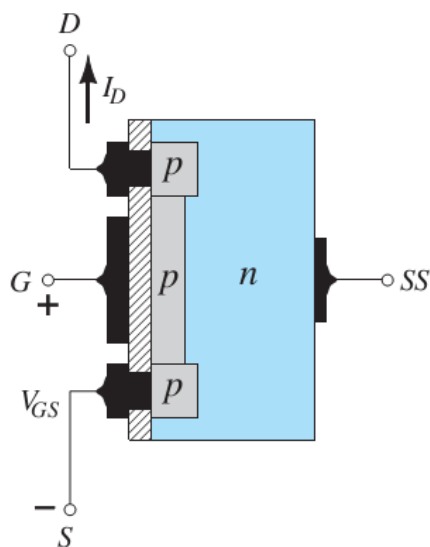
$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$



E-MOSFET

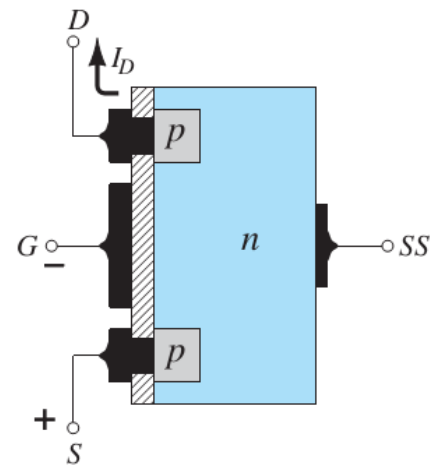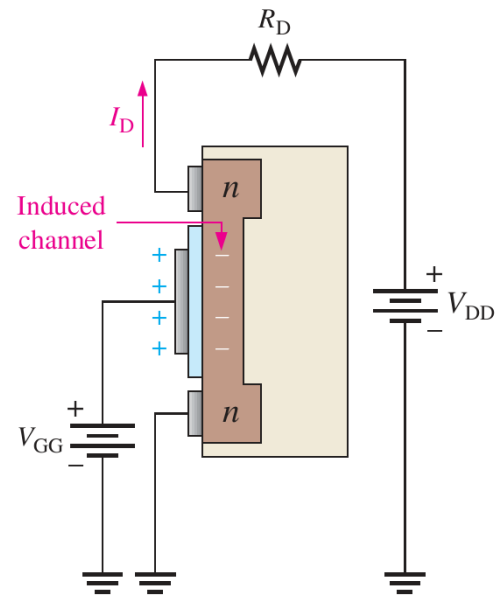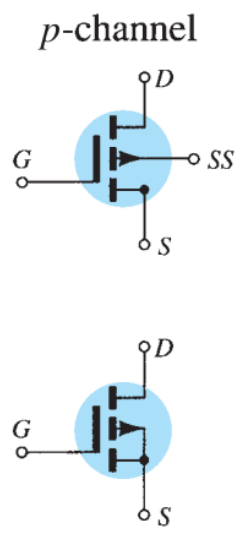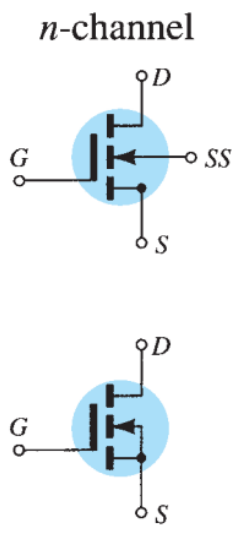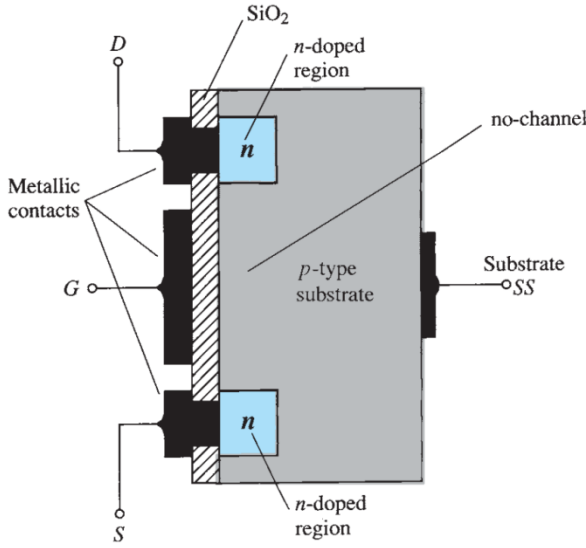

E-MOSFET Operations

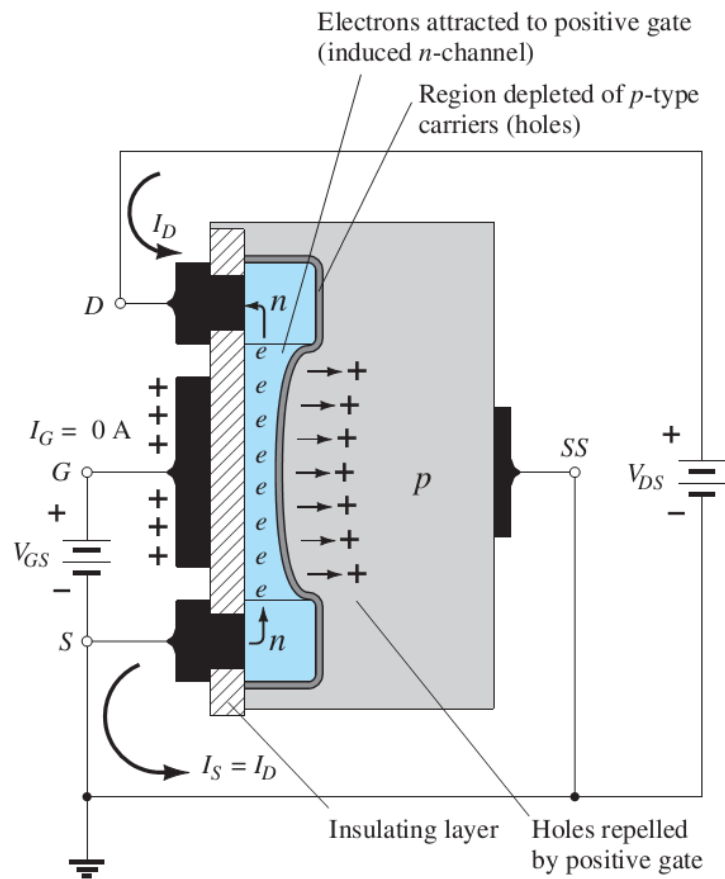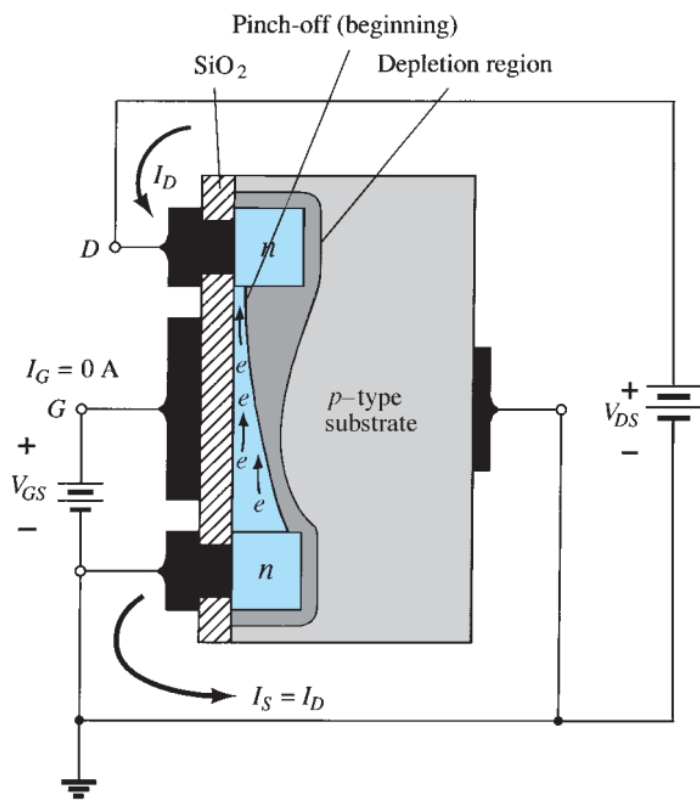


E-MOSFET Transfer Curve

To determine I_D given V_{GS} :

$$I_D = k(V_{GS} - V_T)^2$$

Where:

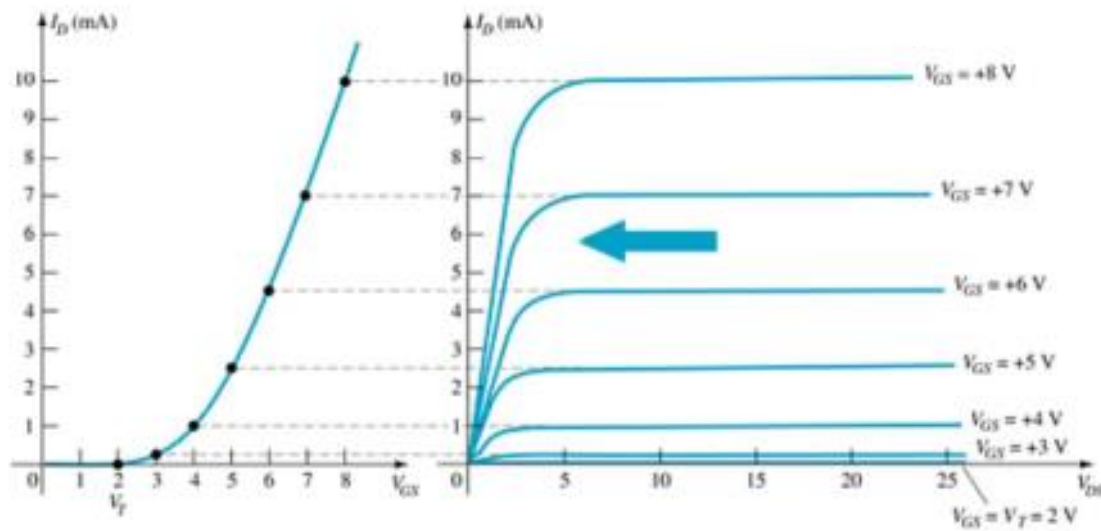V_T = threshold voltage
or voltage at which the
MOSFET turns on



k , a constant, can be determined by using values at a specific point and the formula:


$$k = \frac{I_{D(ON)}}{(V_{GS(ON)} - V_T)^2}$$

V_{DSsat} can be calculated by:

$$V_{Dsat} = V_{GS} - V_T$$

Example

- Determine k , I_D , V_{GS} and V_{DS} for given E-MOSFET where
 - $V_{GS(on)} = 4V$ and $I_{D(on)} = 200mA$
 - $V_{GS(th)} = 2V$ ($=V_T$)
- Hint:

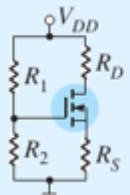
Enhancement type MOSFET Voltage-divider bias (and MESFETs)		$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$ $V_{GS} = V_G - I_D R_S$
--	--	---

To determine I_D given V_{GS} :

$$I_D = k(V_{GS} - V_T)^2$$

k , a constant, can be determined by using values at a specific point and the formula:
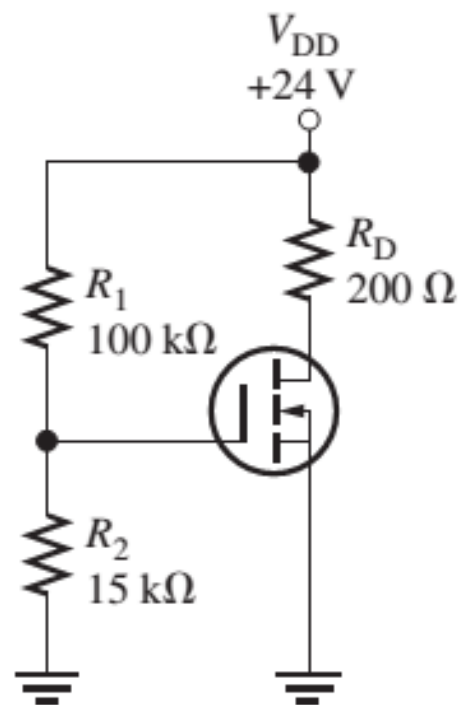
$$k = \frac{I_{D(ON)}}{(V_{GS(ON)} - V_T)^2}$$




Answer

$$K = \frac{I_{D(on)}}{(V_{GS} - V_{GS(th)})^2} = \frac{200 \text{ mA}}{(4 \text{ V} - 2 \text{ V})^2} = \frac{200 \text{ mA}}{4 \text{ V}^2} = 50 \text{ mA/V}^2$$

$$V_{GS} = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD} = \left(\frac{15 \text{ k}\Omega}{115 \text{ k}\Omega} \right) 24 \text{ V} = 3.13 \text{ V}$$

$$\begin{aligned} I_D &= K(V_{GS} - V_{GS(th)})^2 = (50 \text{ mA/V}^2)(3.13 \text{ V} - 2 \text{ V})^2 \\ &= (50 \text{ mA/V}^2)(1.13 \text{ V})^2 = 63.8 \text{ mA} \end{aligned}$$
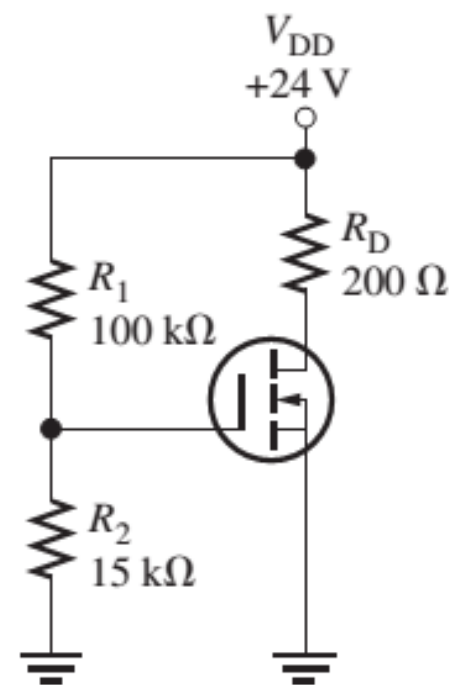
$$V_{DS} = V_{DD} - I_D R_D = 24 \text{ V} - (63.8 \text{ mA})(200 \Omega) = 11.2 \text{ V}$$



E-MOSFET Datasheet

MAXIMUM RATINGS

Rating	Symbol	Value	Unit
Drain–Source Voltage	V_{DS}	25	Vdc
Drain–Gate Voltage	V_{DG}	30	Vdc
Gate–Source Voltage*	V_{GS}	30	Vdc
Drain Current	I_D	30	mAdc
Total Device Dissipation @ $T_A = 25^{\circ}\text{C}$ Derate above 25°C	P_D	300 1.7	mW mW/ $^{\circ}\text{C}$
Junction Temperature Range	T_J	175	$^{\circ}\text{C}$
Storage Temperature Range	T_{stg}	-65 to +175	$^{\circ}\text{C}$

* Transient potentials of ± 75 Volt will not cause gate-oxide failure.

ELECTRICAL CHARACTERISTICS ($T_A = 25^{\circ}\text{C}$ unless otherwise noted.)

Characteristic	Symbol	Min	Max	Unit
----------------	--------	-----	-----	------

OFF CHARACTERISTICS

Drain-Source Breakdown Voltage ($I_D = 10\ \mu\text{A}$, $V_{GS} = 0$)	$V_{(BR)DSX}$	25	–	Vdc
Zero-Gate-Voltage Drain Current ($V_{DS} = 10\ \text{V}$, $V_{GS} = 0$) $T_A = 25^{\circ}\text{C}$ $T_A = 150^{\circ}\text{C}$	I_{DSS}	– –	10 10	nAdc μAdc
Gate Reverse Current ($V_{GS} = \pm 15\ \text{Vdc}$, $V_{DS} = 0$)	I_{GSS}	–	± 10	pAdc

ON CHARACTERISTICS

Gate Threshold Voltage ($V_{DS} = 10\ \text{V}$, $I_D = 10\ \mu\text{A}$)	$V_{GS(Th)}$	1.0	5	Vdc
Drain-Source On-Voltage ($I_D = 2.0\ \text{mA}$, $V_{GS} = 10\ \text{V}$)	$V_{DS(on)}$	–	1.0	V
On-State Drain Current ($V_{GS} = 10\ \text{V}$, $V_{DS} = 10\ \text{V}$)	$I_{D(on)}$	3.0	–	mAdc

2N4351

MOSFET

SWITCHING

3 Drain







2 Gate

4 Case









1 Source

N-CHANNEL – ENHANCEMENT

JFET Bias

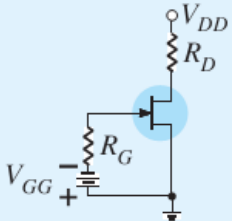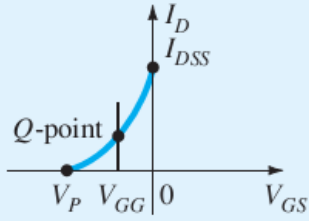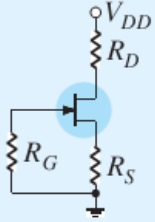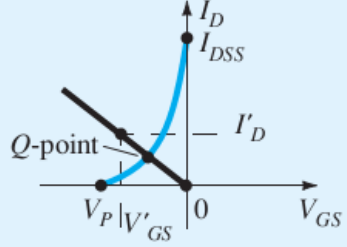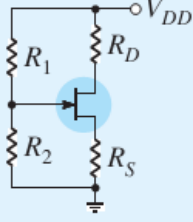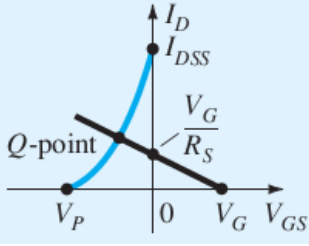JFET Fixed-bias		$V_{GS_Q} = -V_{GG}$ $V_{DS} = V_{DD} - I_D R_D$	
JFET Self-bias		$V_{GS} = -I_D R_S$ $V_{DS} = V_{DD} - I_D (R_D + R_S)$	
JFET Voltage-divider bias		$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$ $V_{GS} = V_G - I_D R_S$ $V_{DS} = V_{DD} - I_D (R_D + R_S)$	

MOSFET Bias

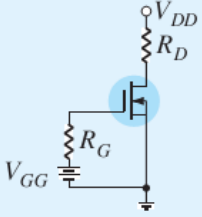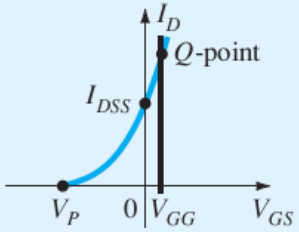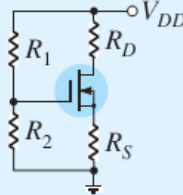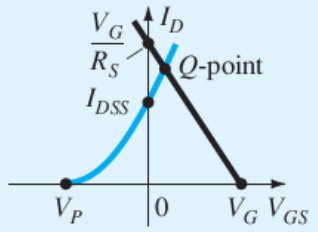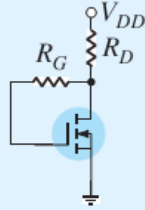
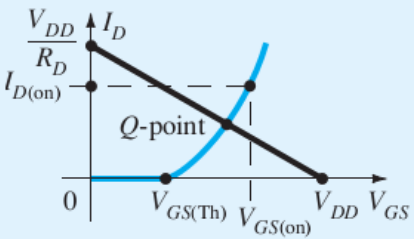
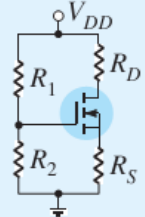
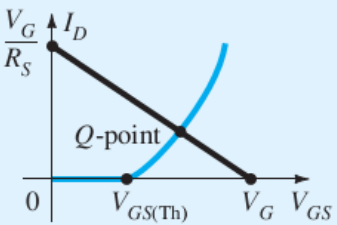
Depletion-type MOSFET Fixed-bias (and MESFETs)		$V_{GS_Q} = +V_{GG}$ $V_{DS} = V_{DD} - I_D R_D$	
Depletion-type MOSFET Voltage-divider bias (and MESFETs)		$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$ $V_{GS} = V_G - I_S R_S$ $V_{DS} = V_{DD} - I_D (R_D + R_S)$	
Enhancement type MOSFET Feedback configuration (and MESFETs)		$V_{GS} = V_{DS}$ $V_{GS} = V_{DD} - I_D R_D$	
Enhancement type MOSFET Voltage-divider bias (and MESFETs)		$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$ $V_{GS} = V_G - I_D R_S$	

MOSFET Operation Status





MOSFET type	$V_{GS} > 0$	$V_{GS} = 0$	$V_{GS} < 0$
N-Channel D-MOSFET	ON	ON	OFF
N-Channel E-MOSFET	ON	OFF	OFF
P-Channel D-MOSFET	OFF	ON	ON
P-Channel E-MOSFET	OFF	OFF	ON

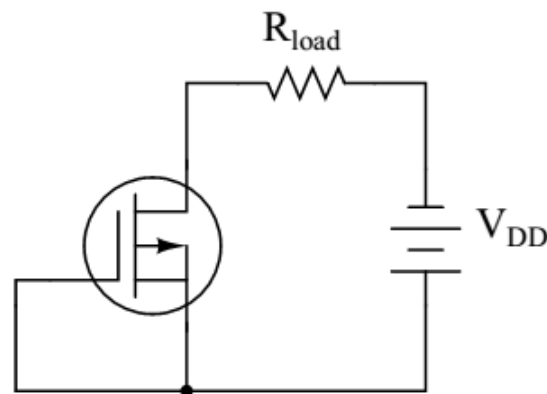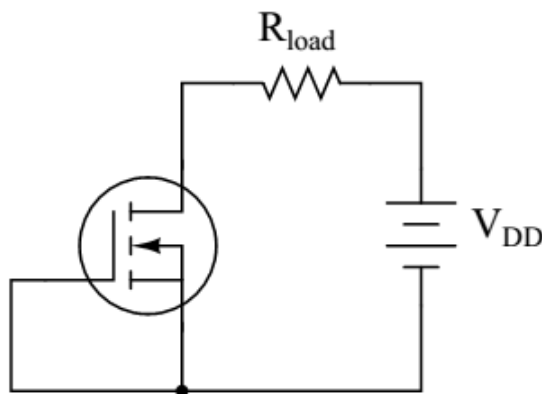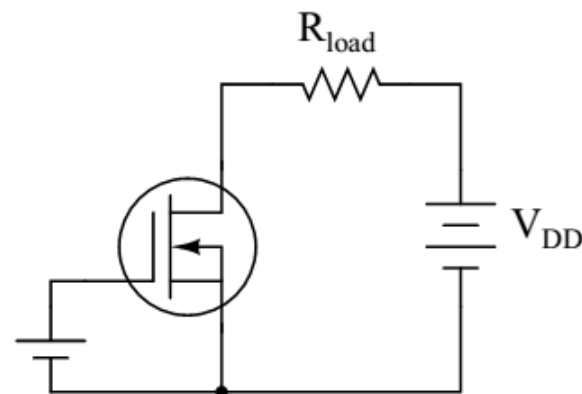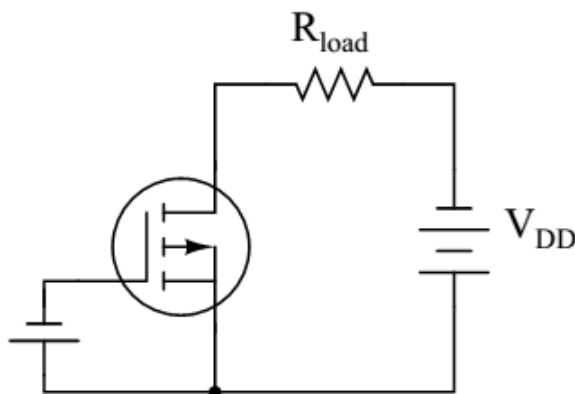Example

- Determine the correct type (p-channel or n-channel, D-type or E-type) of the following MOSFETs



Answer

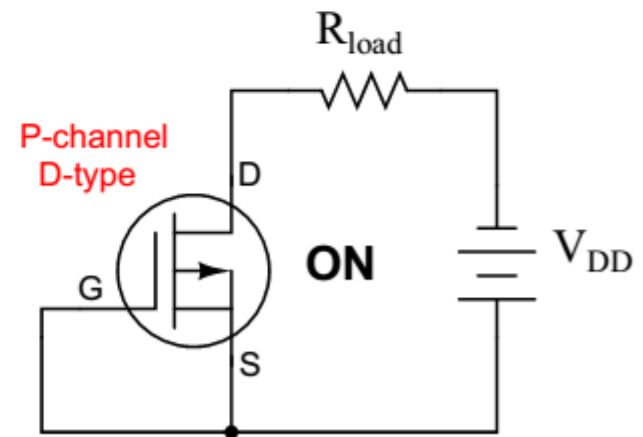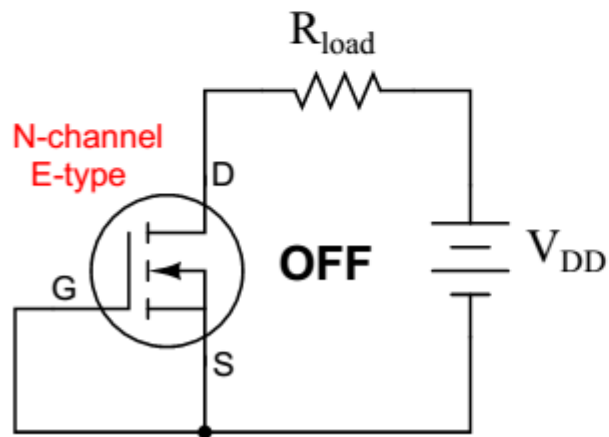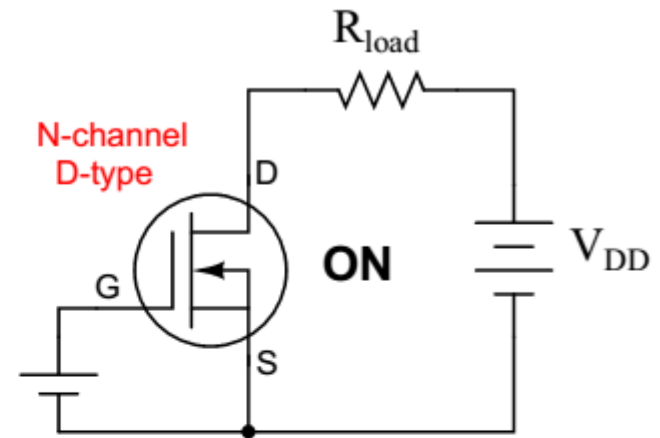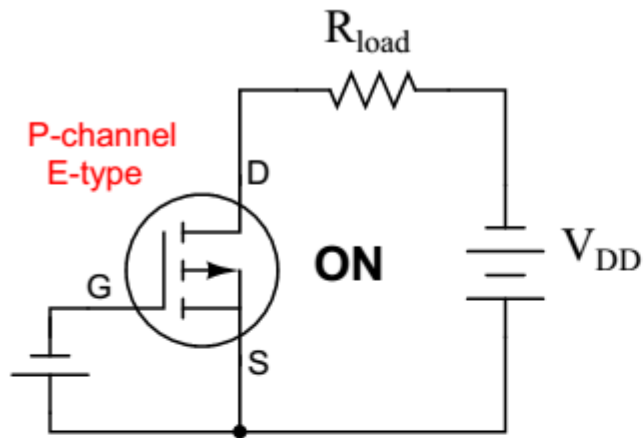

Reference

