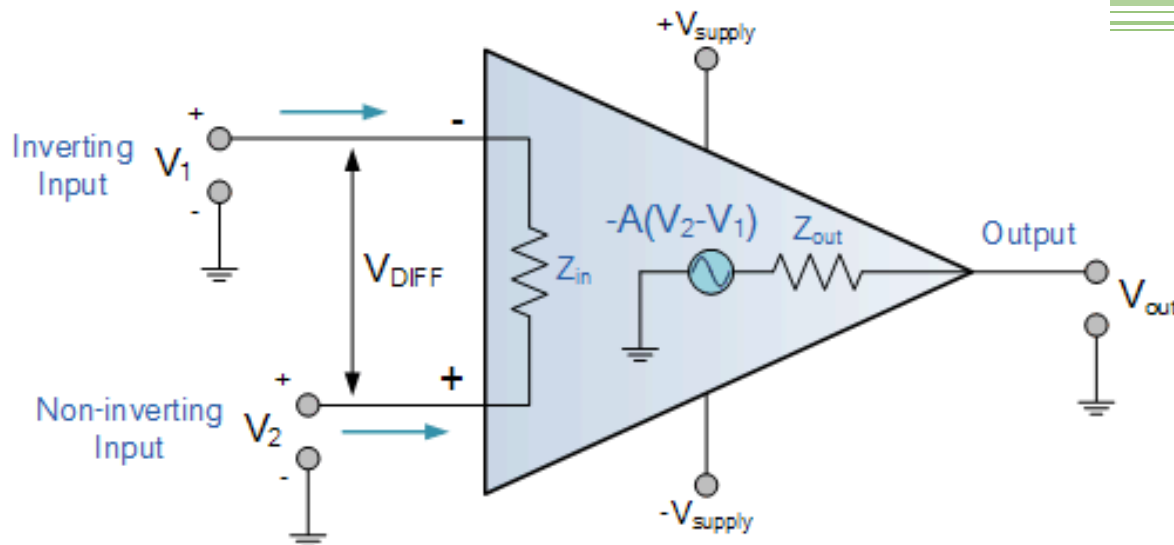




C02015

Operational Amplifier (Op-Amp)





Contents

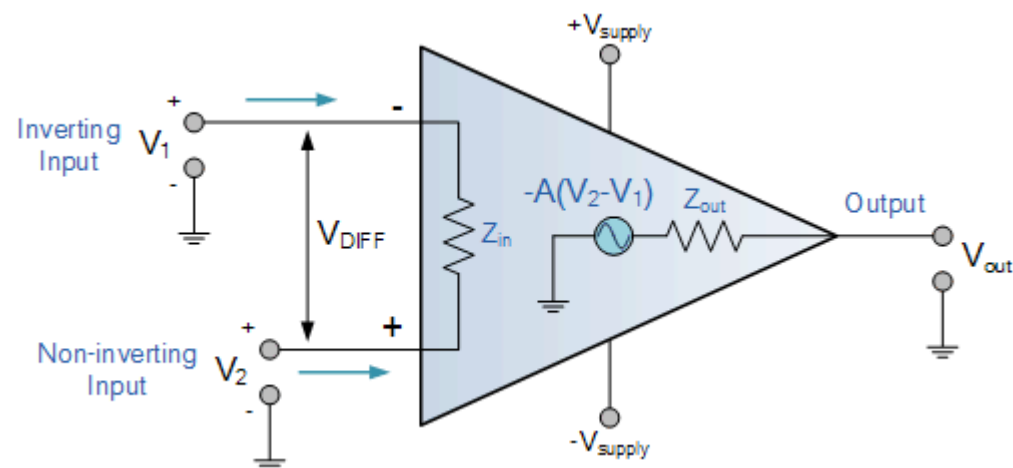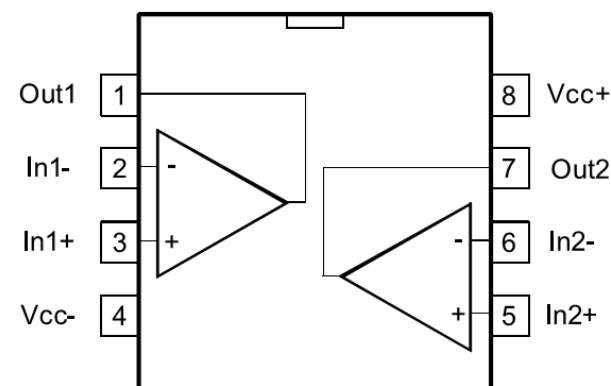- Operation
- Feedback Circuit
- Characteristics
- Practical Applications




Basic Op-Amp

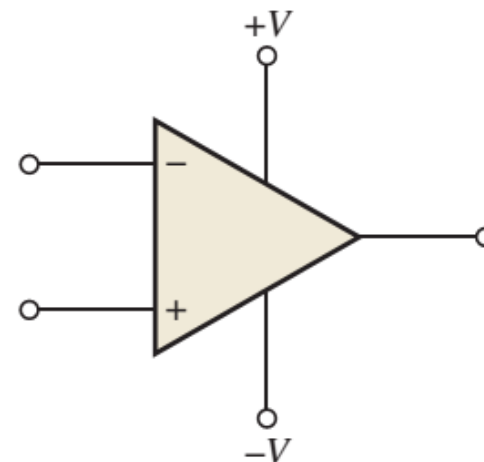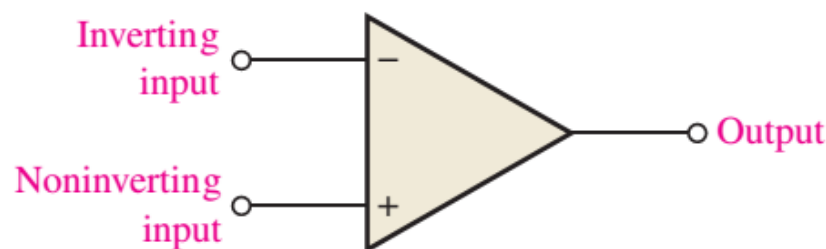

- Op-Amp = **O**perational **A**mplifier
- An Op-Amp consist
 - Inverting input
 - Noninverting input
 - Output
- Two power supply pins ($V+$ and $V-$)

Op-Amp Gain


- Op-Amps have a very high gain. They can be connected open-loop or close-loop.
 - **Open-loop** refers a configuration where there is no feedback from output back to the input. In the open-loop configuration, the gain can exceed 10^5 .
 - **Closed-loop** configuration reduces the gain. In order to control the gain of an op-amp it must have feedback. This feedback is a **negative feedback**. A **negative feedback** reduces the gain and improves many characteristics of the op-amp.

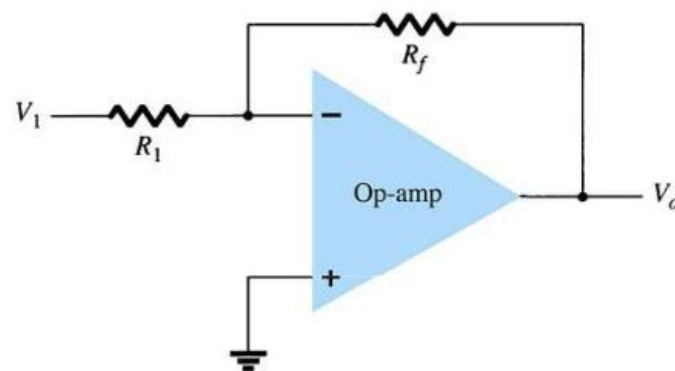

Op-Amp Models


■ Practical Model

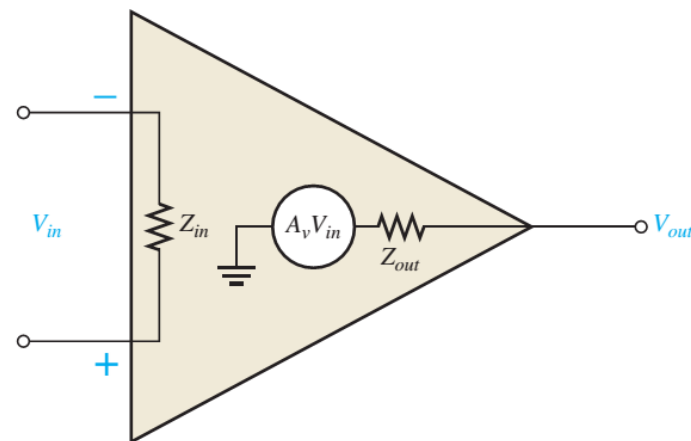- Z_{in} is very large
- Z_{out} is small
- The gain $A_v = \frac{V_{out}}{V_{in}}$ in open-loop configuration is very high.





■ Ideal Model (used for analysis)

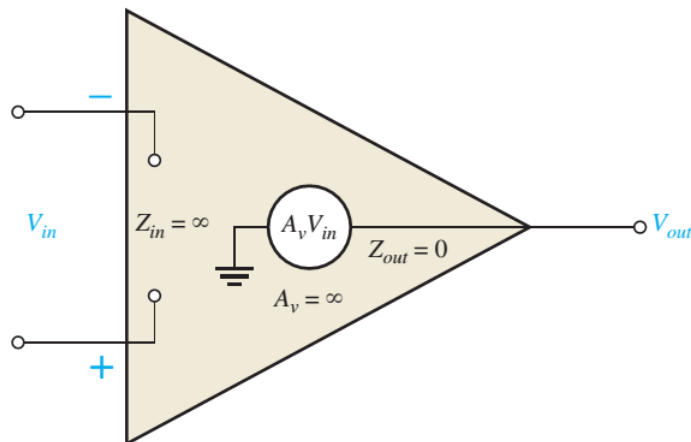- $Z_{in} = \infty \rightarrow I_{in+} = I_{in-} = 0$; $V_{in+} = V_{in-}$
- $Z_{out} = 0$
- The open-loop gain: $A_v = \frac{V_{out}}{V_{in}} = \infty$





Operation of Op-Amp

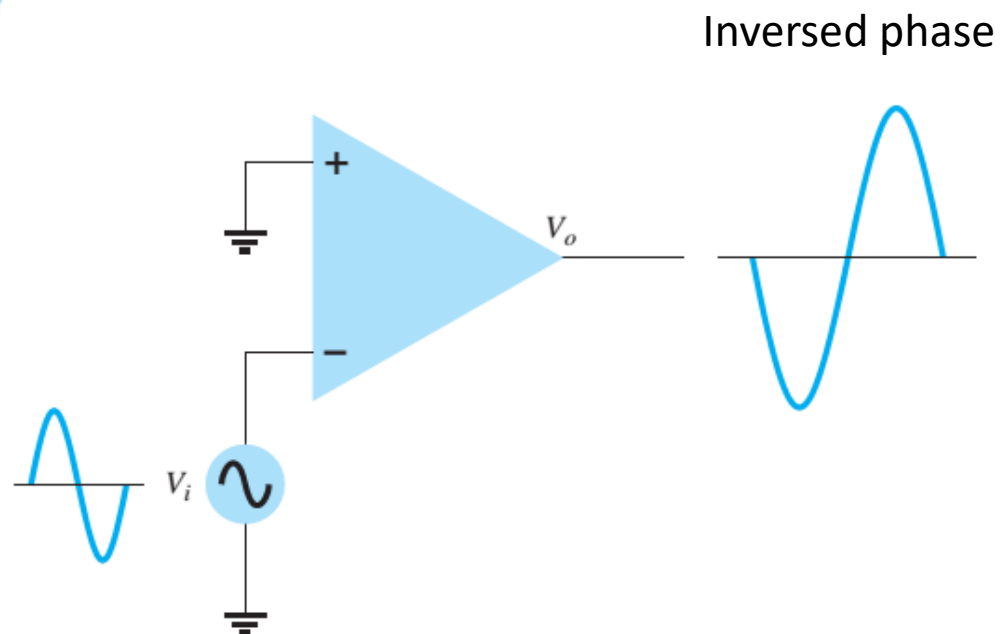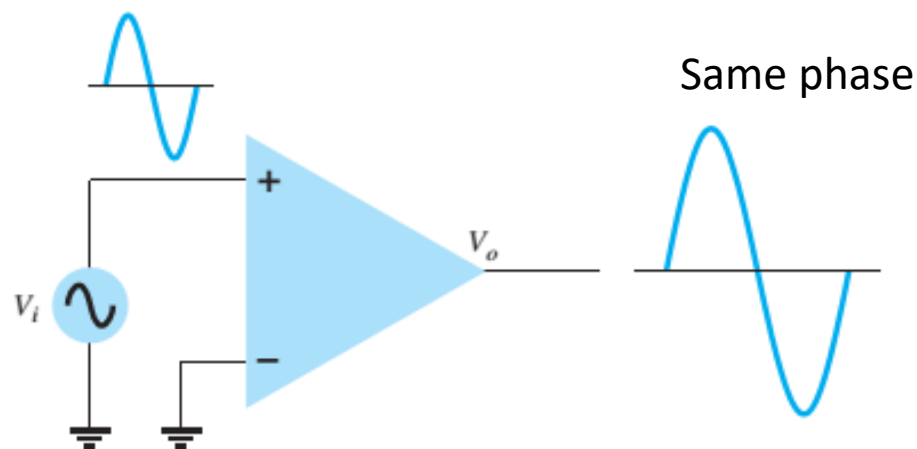- The amplitude of V_{out} is higher than amplitude of V_{in} .




Operation of Op-Amp (cont)

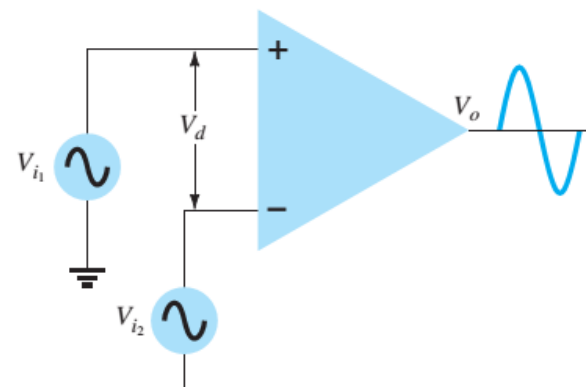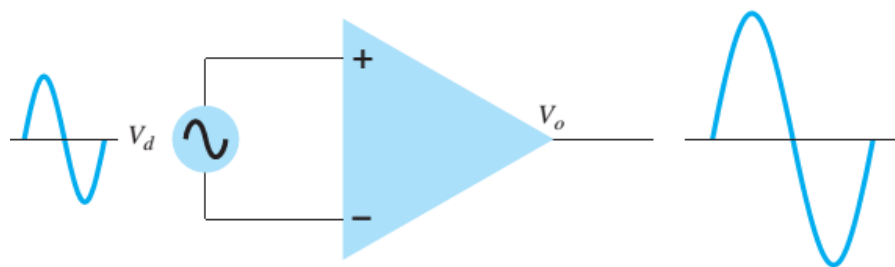- The differential signal of 2 inputs is amplified.






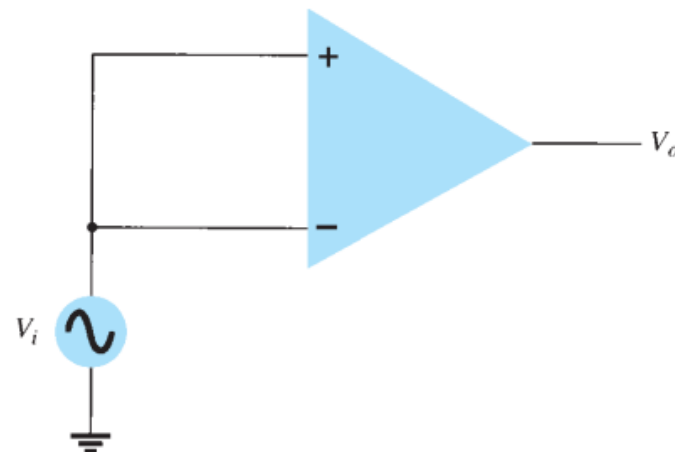- When 2 inputs use common signal, the output is zero.




Non Feedback Circuits (Open Loop)

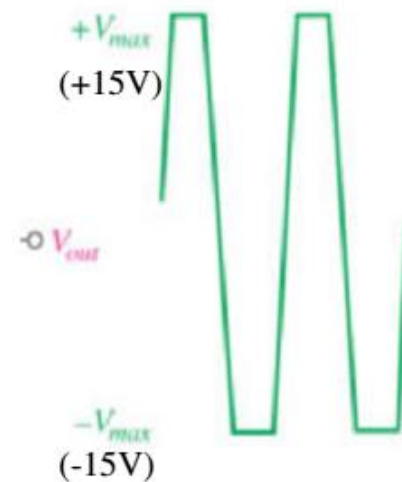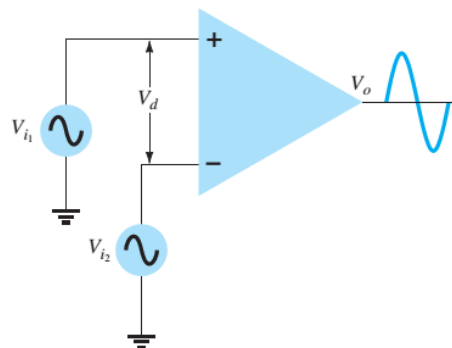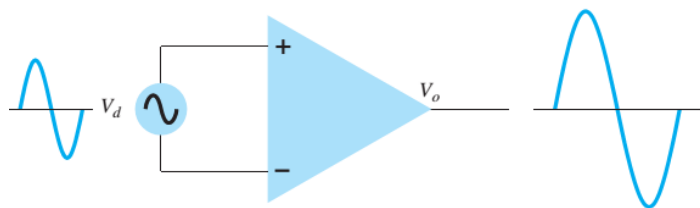- For the circuits without feedback (i.e. no connection between output and input), the open-loop gain is very large ($>10^5$).
- The output voltage will easily reach the saturation and the amplitude will be trimmed.




Negative Feedback Circuits (Close Loop)

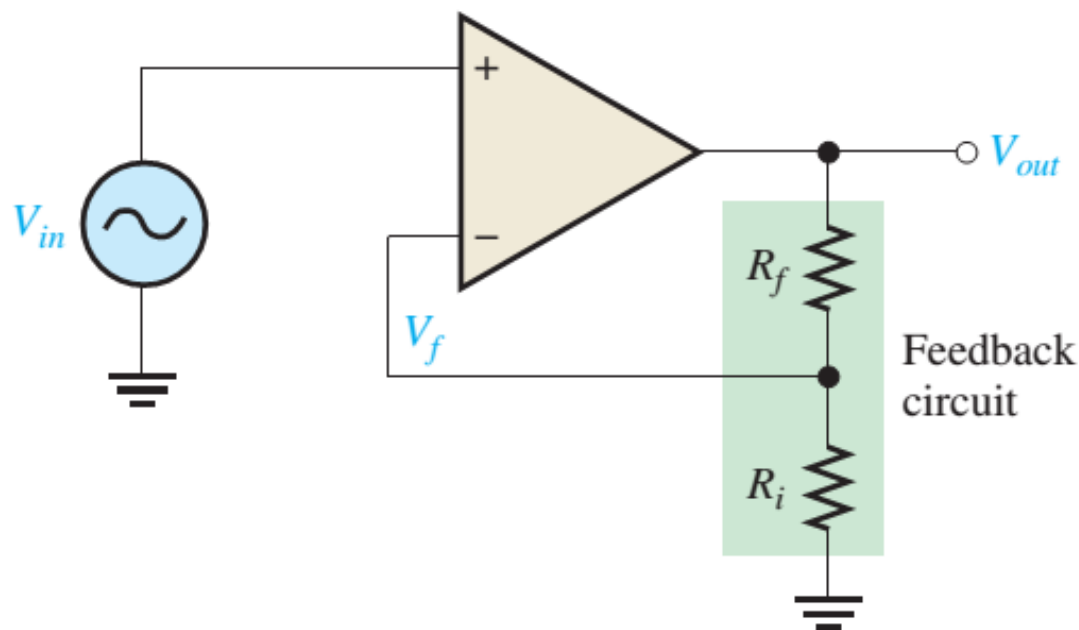- In order to control the gain of an op-amp it must have feedback. This feedback is a **negative feedback**. A **negative feedback** reduces the gain and improves many characteristics of the op-amp.



Negative Feedback

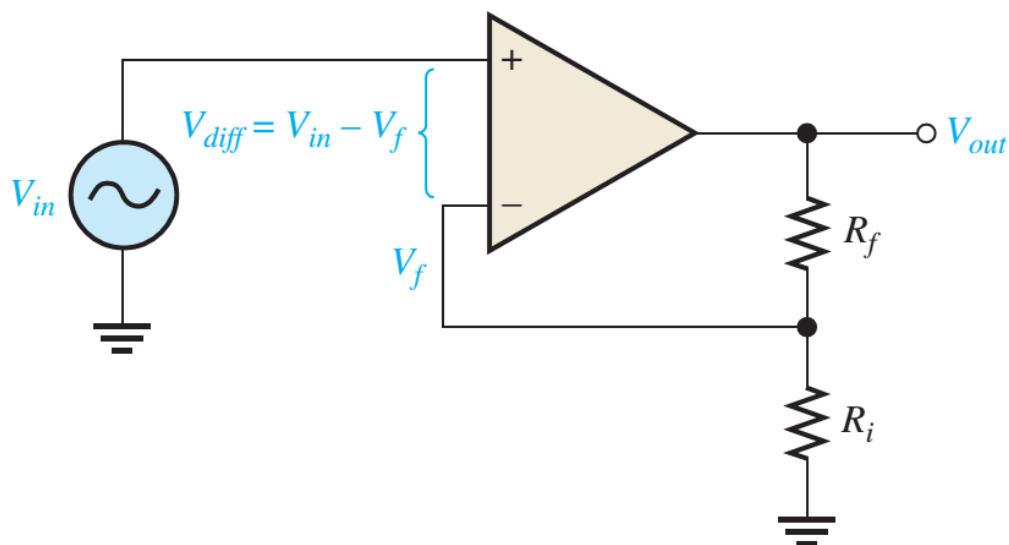

$$V_f = \left(\frac{R_i}{R_i + R_f} \right) V_{out} \quad B = \frac{R_i}{R_i + R_f}$$

$$V_{out} = A_{ol}(V_{in} - V_f)$$

$$V_{out} = A_{ol}(V_{in} - BV_{out})$$

$$V_{out} + A_{ol}BV_{out} = A_{ol}V_{in}$$


$$A_{cl(NI)} = 1 + \frac{R_f}{R_i}$$

$$\frac{V_{out}}{V_{in}} = \frac{A_{ol}}{1 + A_{ol}B}$$

$$A_{cl(NI)} = \frac{V_{out}}{V_{in}} \cong \frac{1}{B} = \frac{R_i + R_f}{R_i}$$

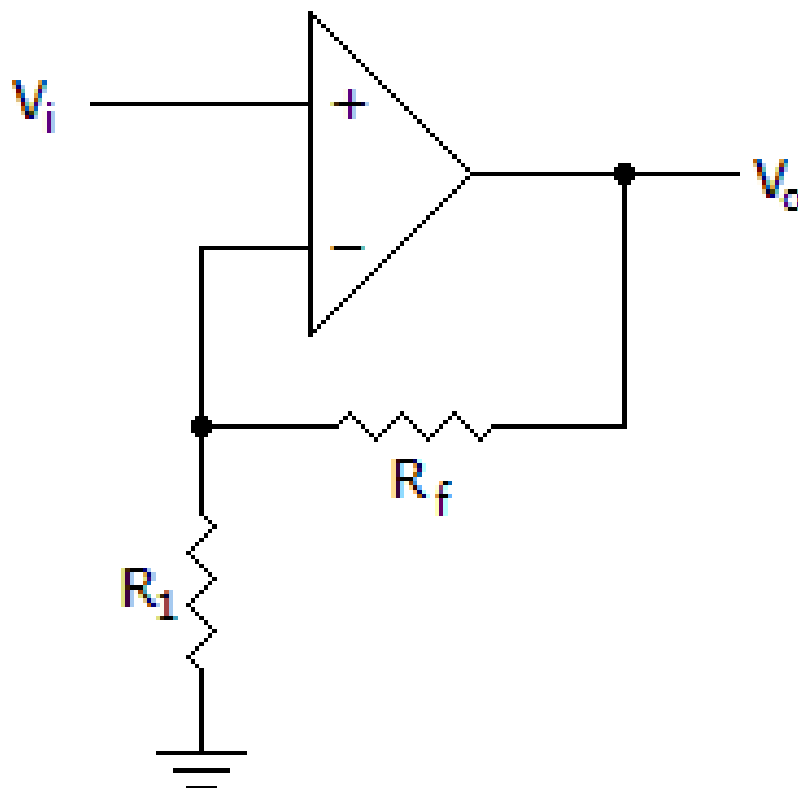Exercise


- Calculate the output gain of the circuit if $R_1 = 100(\text{Ohm})$ and $R_f = 1(\text{KOhm})$



Answer





- 11

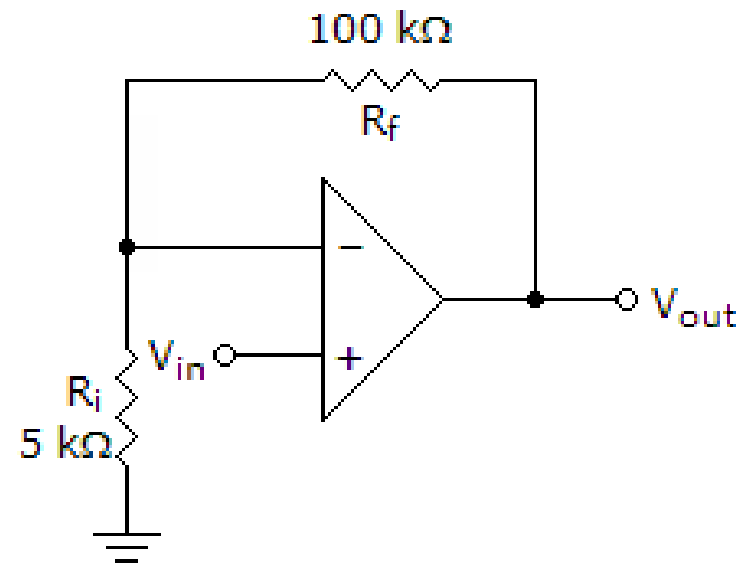- Refer to the given figure. A dc input signal of -50 mV is applied. You would measure _____ from the inverting input to ground.
 - 50mV
 - 1.05V
 - -1.05V
 - -50mV



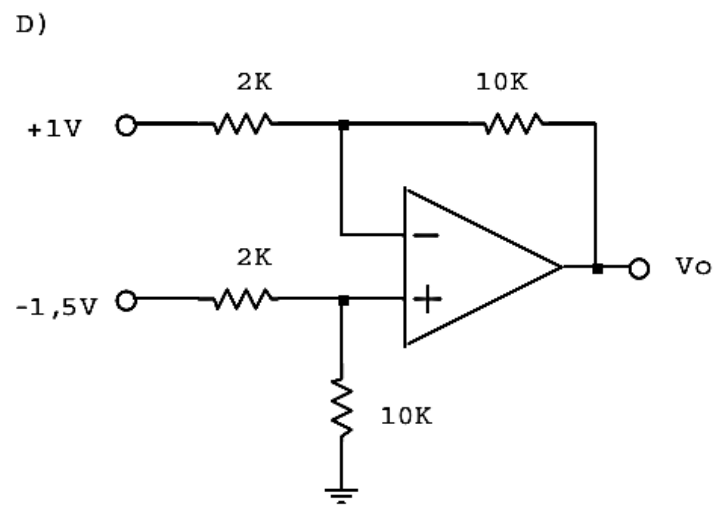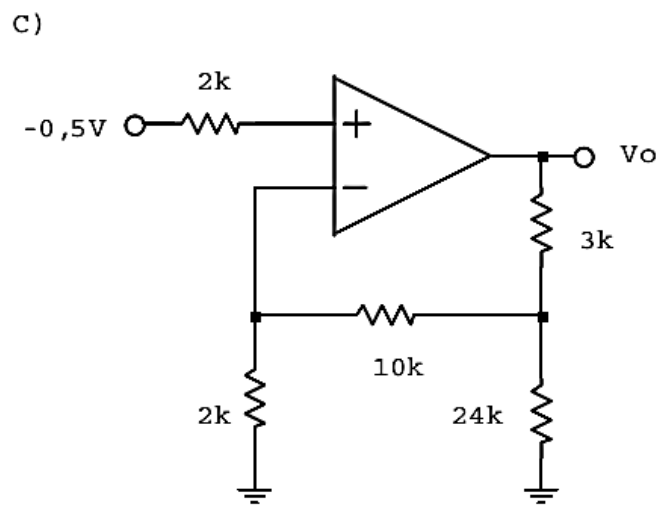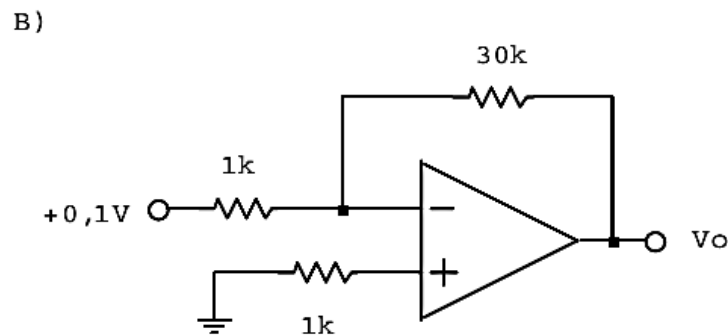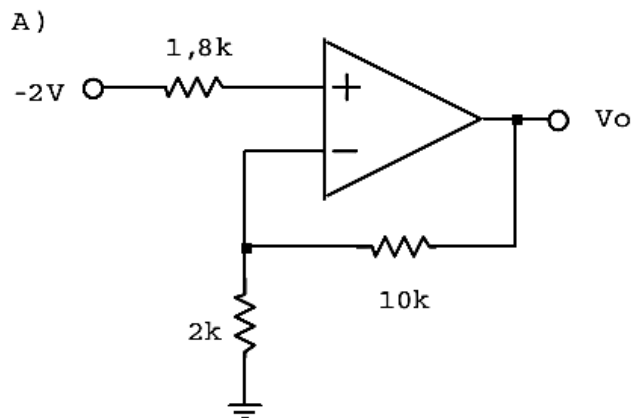
Exercise

- Compute the output voltage in the following circuits using **ideal op-amp**




Solution


No.1A)

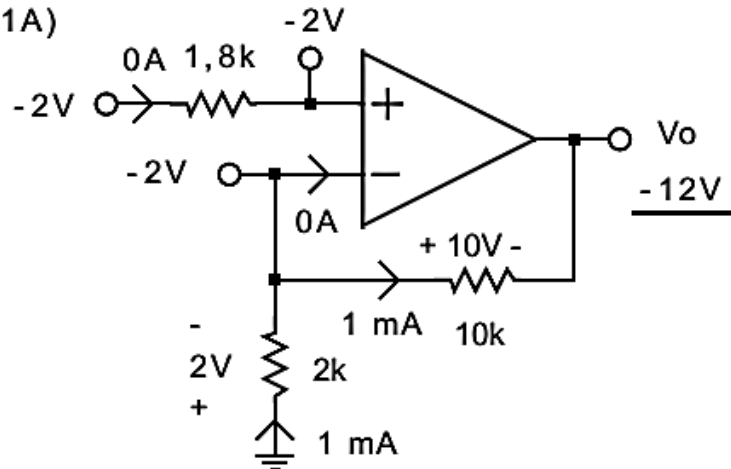


B)

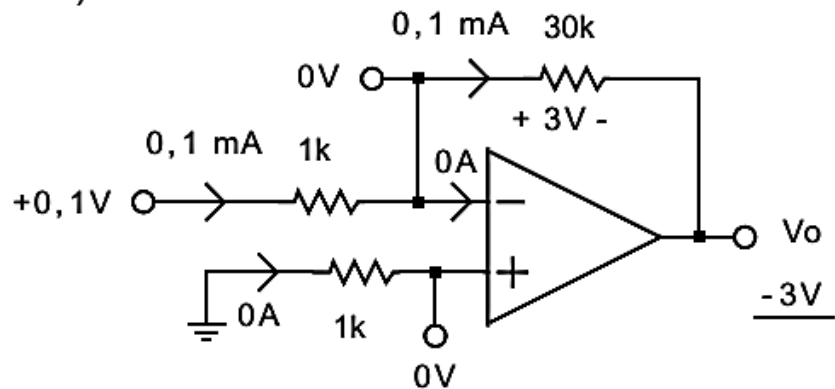

C)

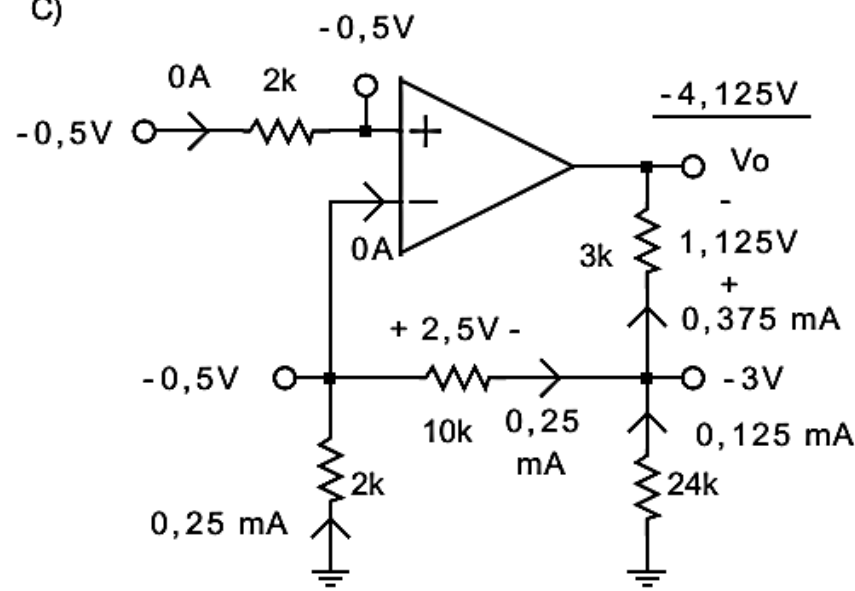

D)

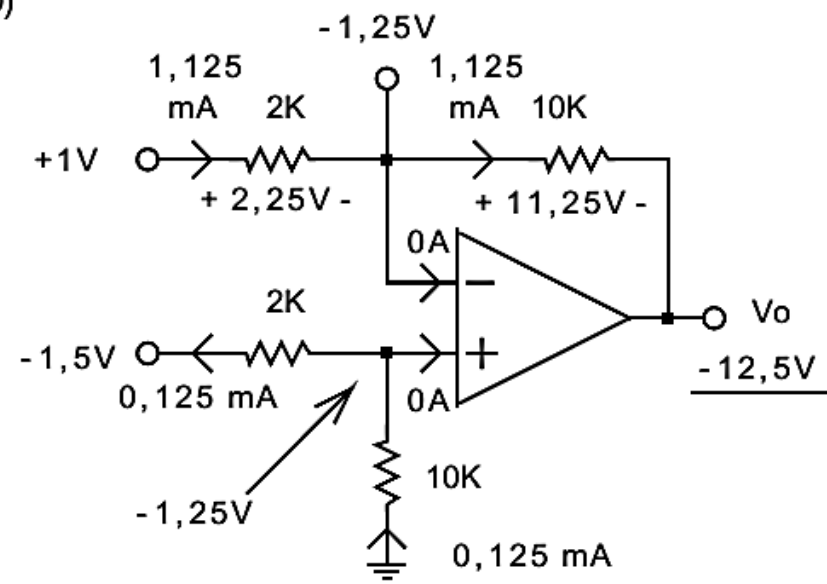


Exercise


- Characteristics of an Op-Amp is given in the following table. The power supply is $\pm 15\text{V}$.

Parameter	Minimum	Typical	Maximum
Output Voltage	$\pm 12\text{V}$	$\pm 13.5\text{V}$	
Input Voltage	$\pm 11\text{V}$	$\pm 12.5\text{V}$	
Output current of shorted-circuit	$\pm 12\text{mA}$	$\pm 20\text{mA}$	

- Determine V_x

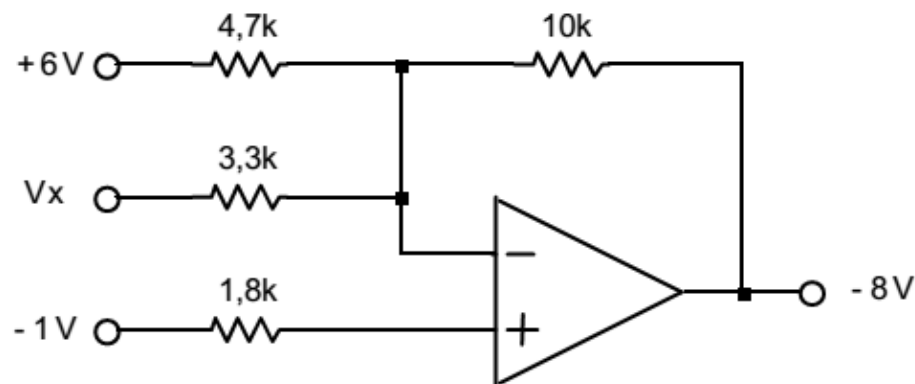


Solution

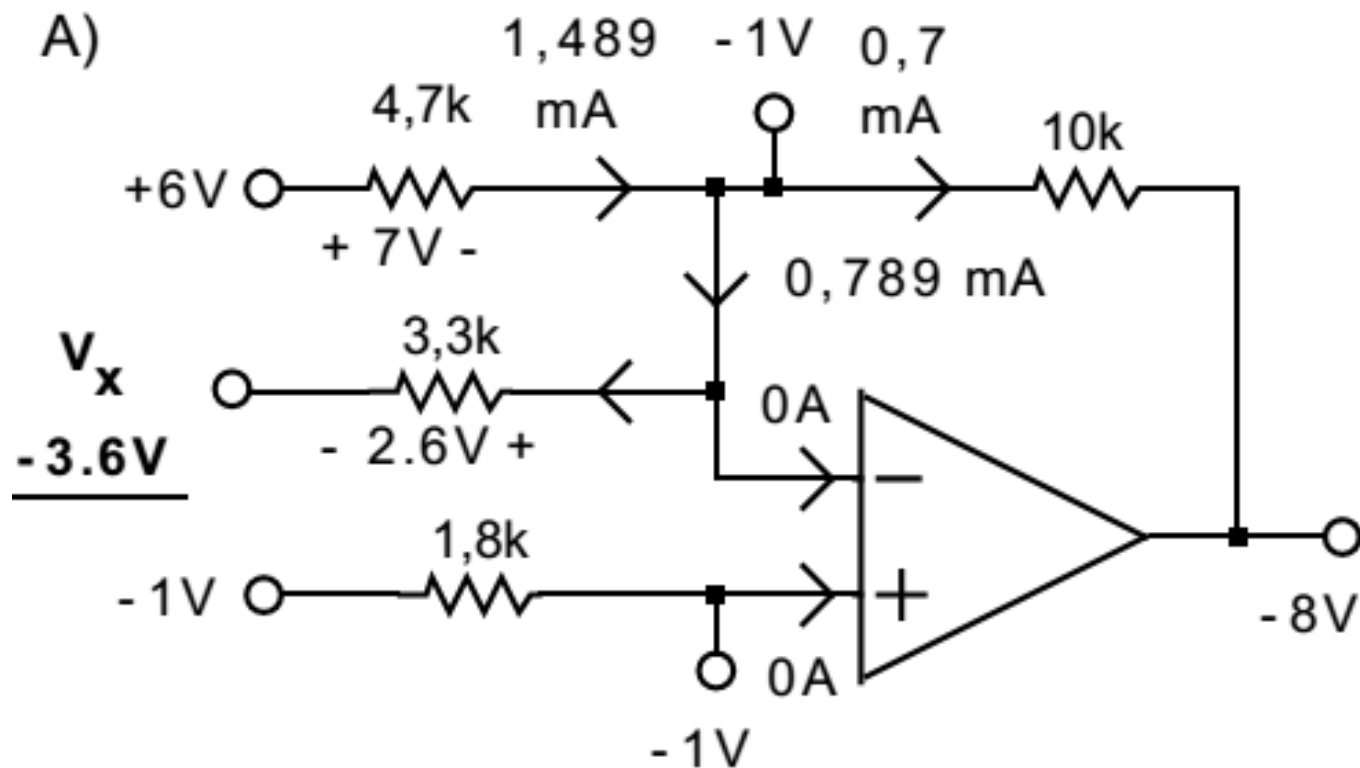

Op-Amp Datasheet

■ IC LM358

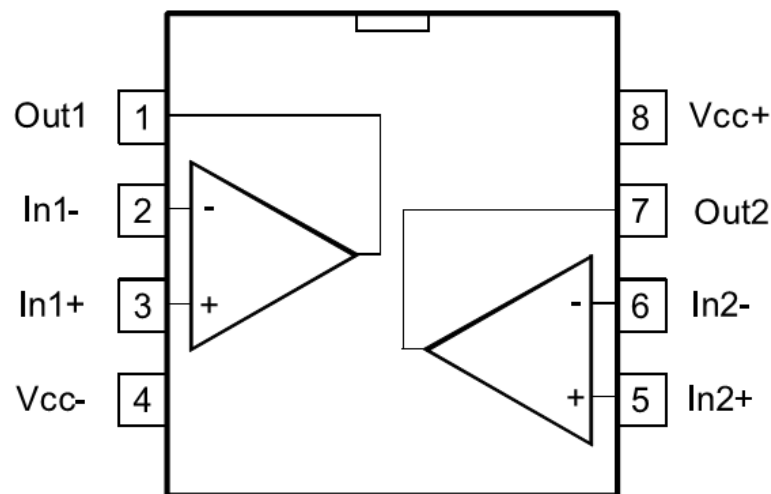


DFN8 2x2



MiniSO8



TSSOP8

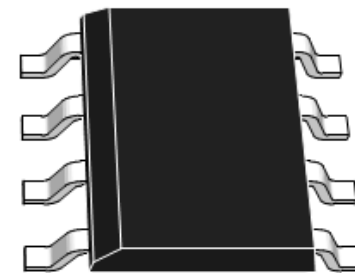

SO8

Op-Amp Datasheet (IC LM358)


- Maximum power supply: $\pm 22\text{V}$
- Maximum input voltage: $\pm 15\text{V}$
- Maximum differential input voltage: $\pm 30\text{V}$

Absolute maximum ratings over operating free-air temperature range (unless otherwise noted)

	uA741	UNIT
Supply voltage V_{CC+}	22	V
Supply voltage V_{CC-}	-22	V
Differential input voltage	± 30	V
Input voltage any input	± 15	V
Voltage between either offset null terminal (N1/N2) and V_{CC-}	± 0.5	V
Duration of output short-circuit	unlimited	
Continuous total power dissipation at (or below) 25°C free-air temperature	500	mW
Operating free-air temperature range	-40 to 85	°C
Storage temperature range	-65 to 150	°C
Lead temperature 1,6 mm (1/16 in.) from case for 60 seconds	300	°C
Lead temperature 1,6 mm (1/16 in.) from case for 10 seconds	260	°C

Op-Amp Datasheet

■ IC 741

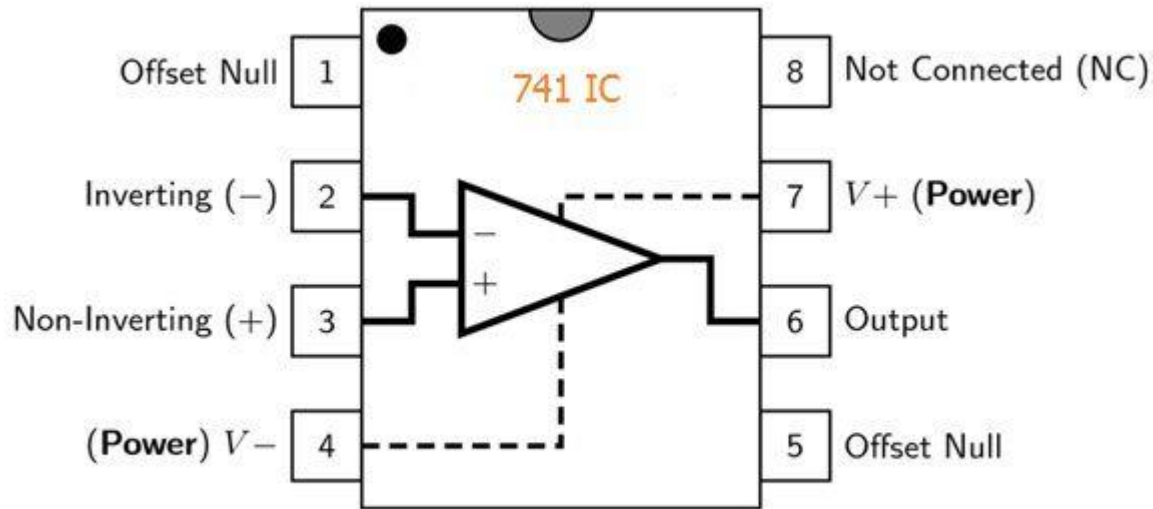

741 Op-Amp IC




Op-Amp Datasheet ($\mu A741$)

$\mu A741$ Electrical Characteristics: $V_{CC} = \pm 15\text{ V}$, $T_A = 25^\circ\text{C}$

Characteristic	Minimum	Typical	Maximum	Unit
V_{IO} Input offset voltage		1	6	mV
I_{IO} Input offset current		20	200	nA
I_{IB} Input bias current		80	500	nA
V_{ICR} Common-mode input voltage range	± 12	± 13		V
V_{OM} Maximum peak output voltage swing	± 12	± 14		V
A_{VD} Large-signal differential voltage amplification	20	200		V/mV
r_i Input resistance	0.3	2		M Ω
r_o Output resistance		75		Ω
C_i Input capacitance		1.4		pF
CMRR Common-mode rejection ratio	70	90		dB
I_{CC} Supply current		1.7	2.8	mA
P_D Total power dissipation		50	85	mW

- A_{VD} – Large-signal differential voltage amplification
– $200\text{V/mV} = 200.000$
- r_i – input resistance: $2\text{M}\Omega$
- r_o – output resistance: 75Ω

Output Voltage Threshold

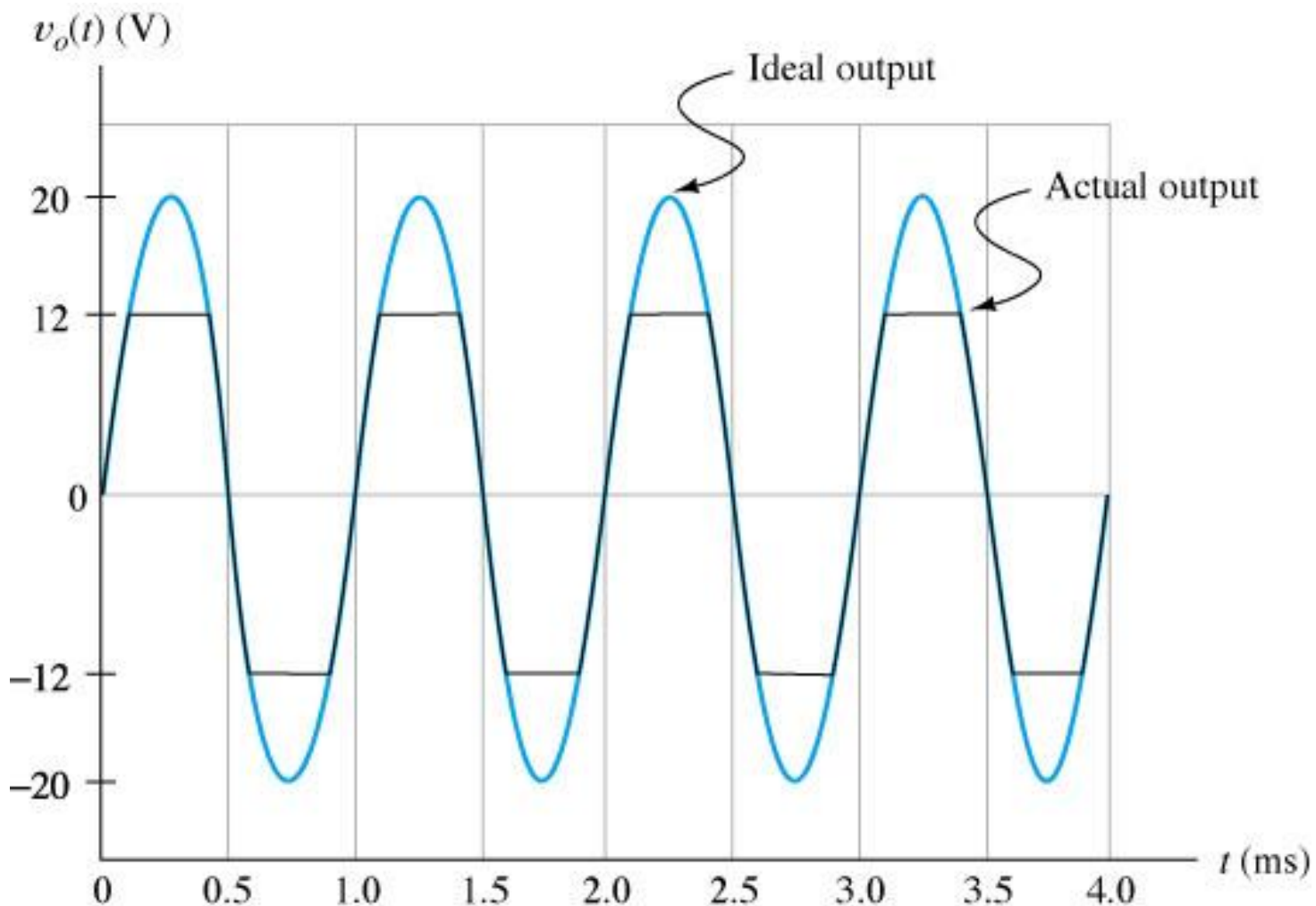


Practical Op-Amp Circuits

- Unity Follower
- Summing Amplifier
- Integrator
- Differentiator
- Comparator

Summing Amplifier

Because the op-amp has a high input impedance, the multiple inputs are treated as separate inputs.

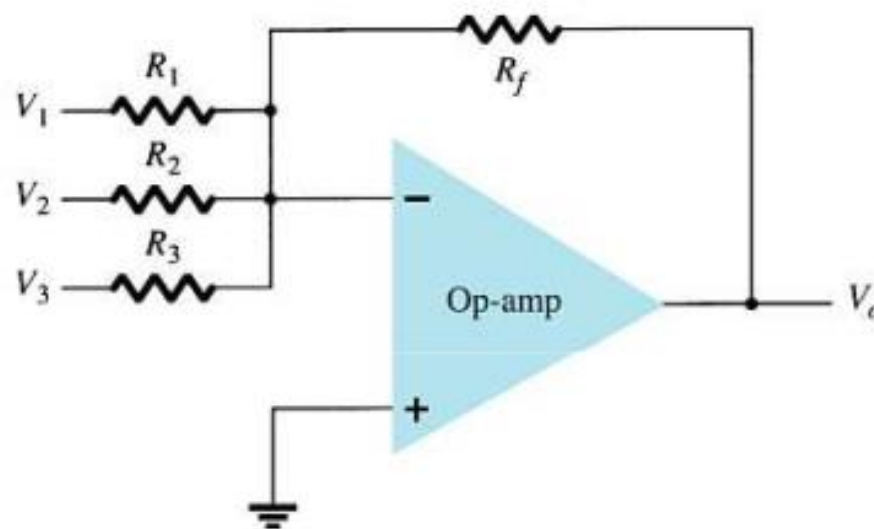
$$V_o = -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3\right)$$



Integrator

The output is the integral of the input. Integration is the operation of summing the area under a waveform or curve over a period of time. This circuit is useful in low-pass filter circuits and sensor conditioning circuits.

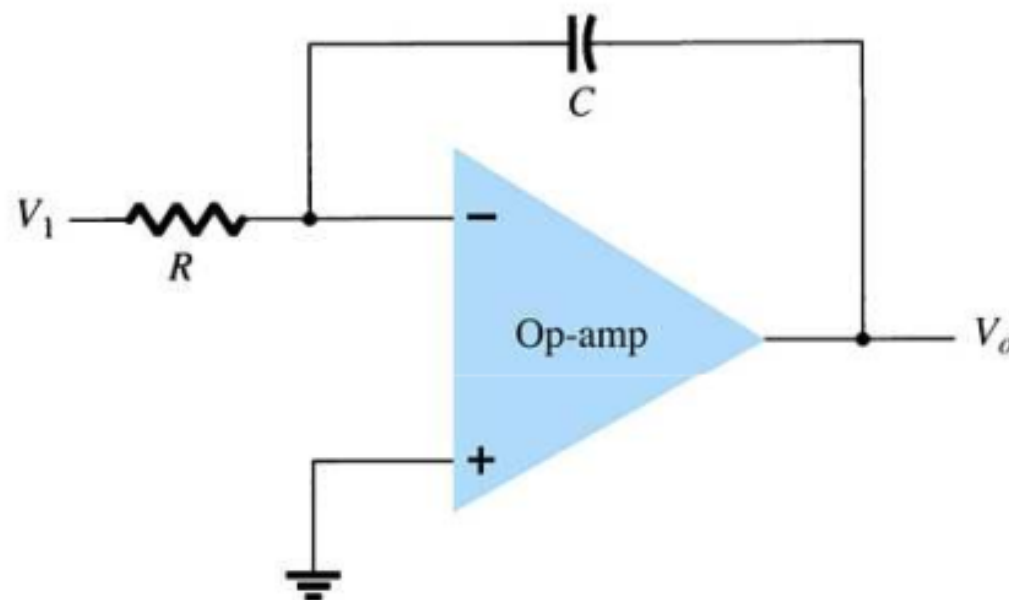
$$v_o(t) = -\frac{1}{RC} \int v_1(t) dt$$



Differentiator





The differentiator takes the derivative of the input. This circuit is useful in high-pass filter circuits.

$$v_o(t) = -RC \frac{dv_1(t)}{dt}$$

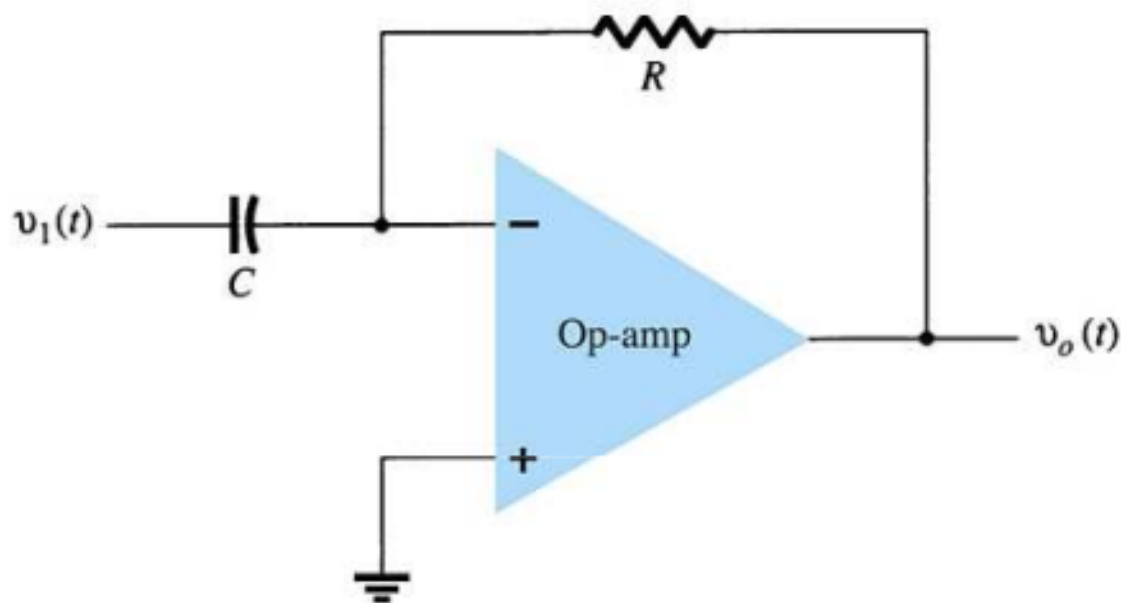



Comparator

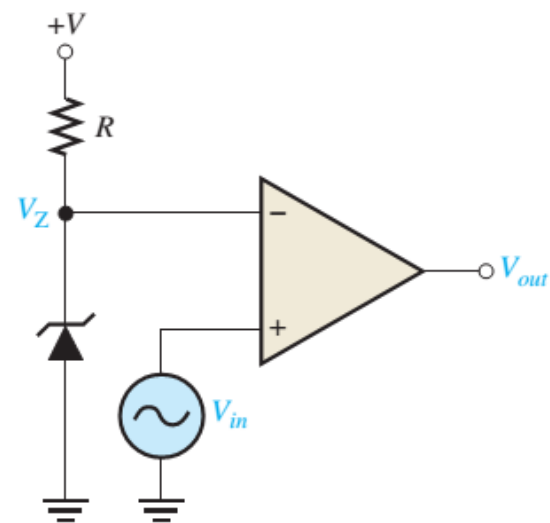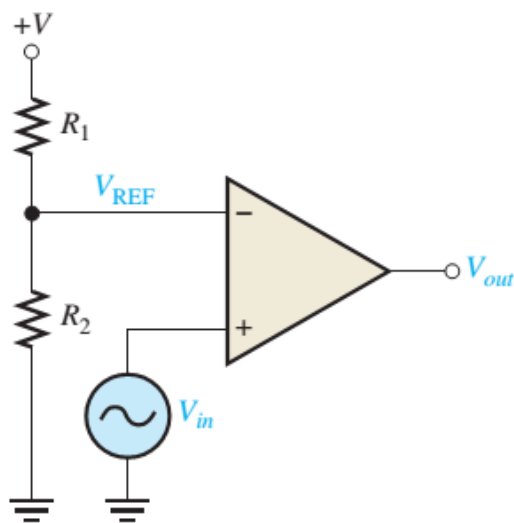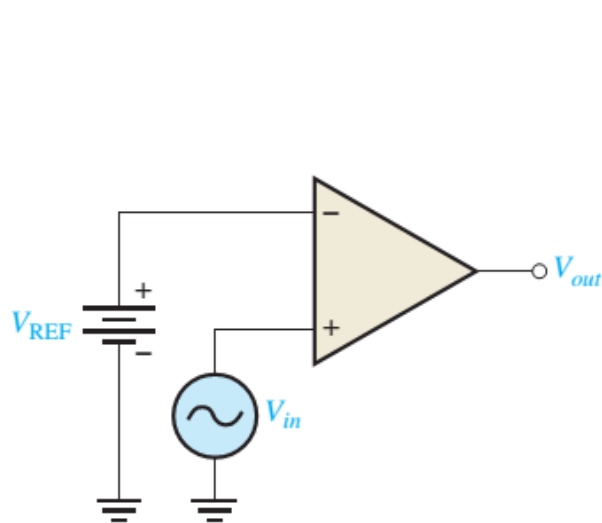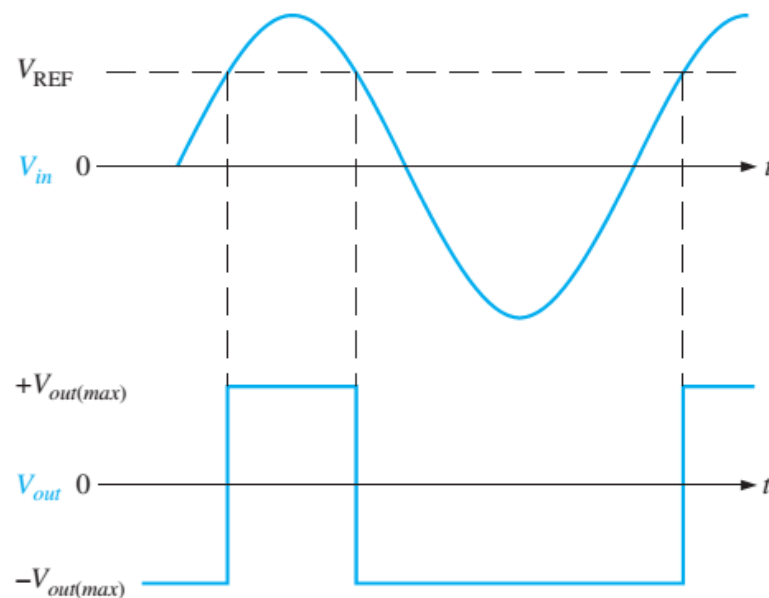- $V_{out} = +V_{out(max)}$ when $V_+ > V_-$
 - $V_{in} > V_{REF}$
- $V_{out} = -V_{out(max)}$ when $V_+ < V_-$
 - $V_{in} < V_{REF}$




Noisy Comparator

- Unexpected pulses

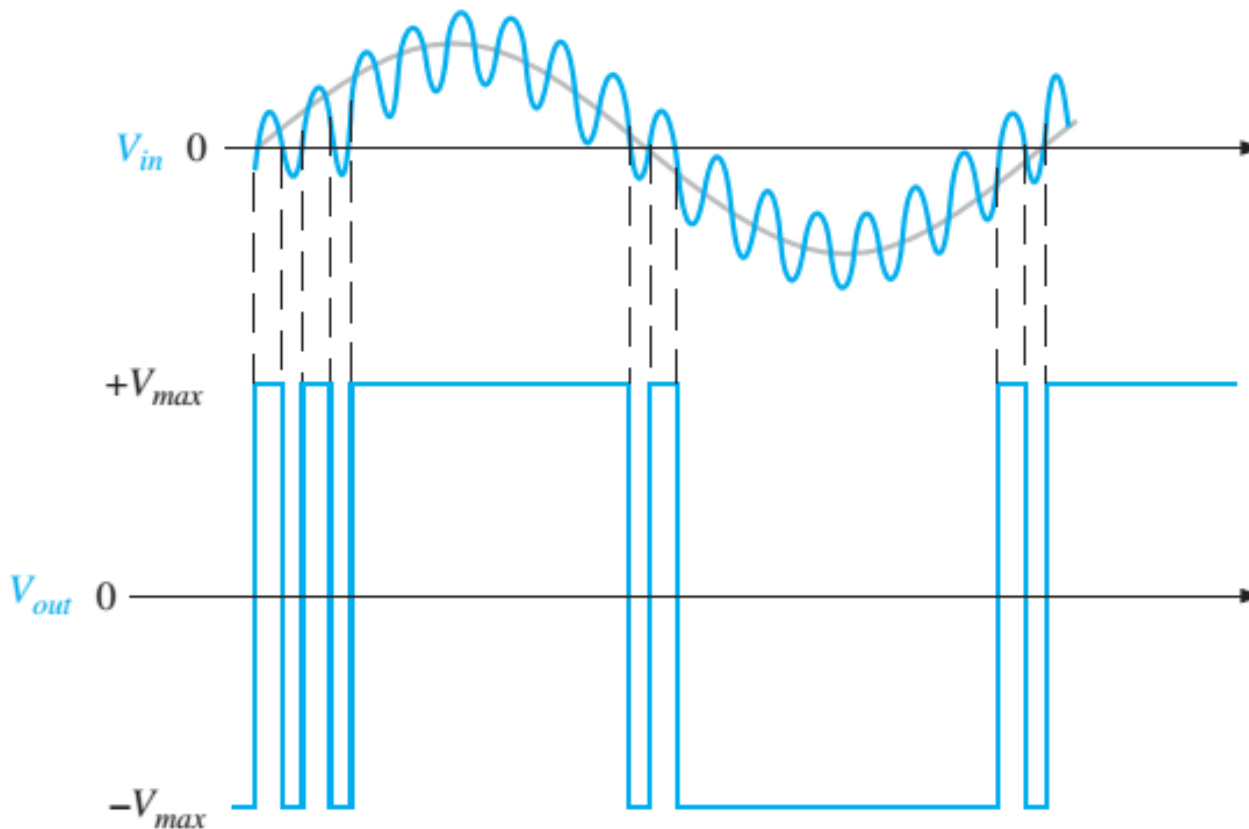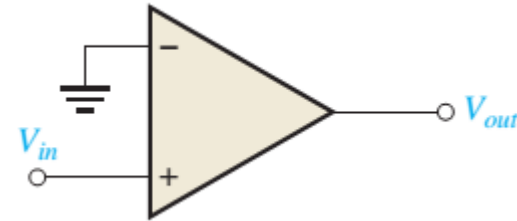


Noiseless Comparator

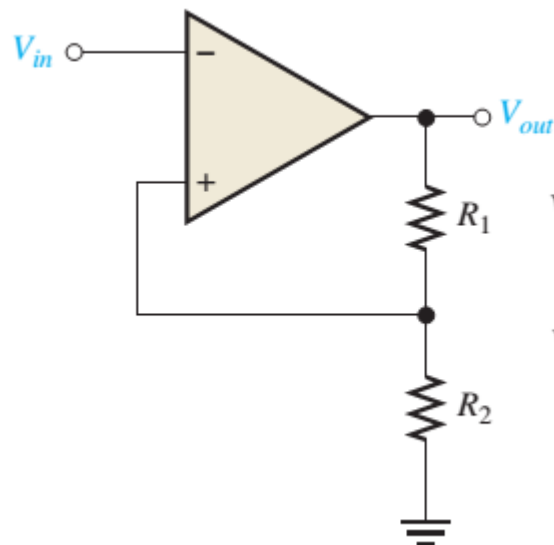

$$V_{UTP} = \frac{R_2}{R_1 + R_2} (+V_{out(max)})$$

$$V_{LTP} = \frac{R_2}{R_1 + R_2} (-V_{out(max)})$$

$$V_{HYS} = V_{UTP} - V_{LTP}$$

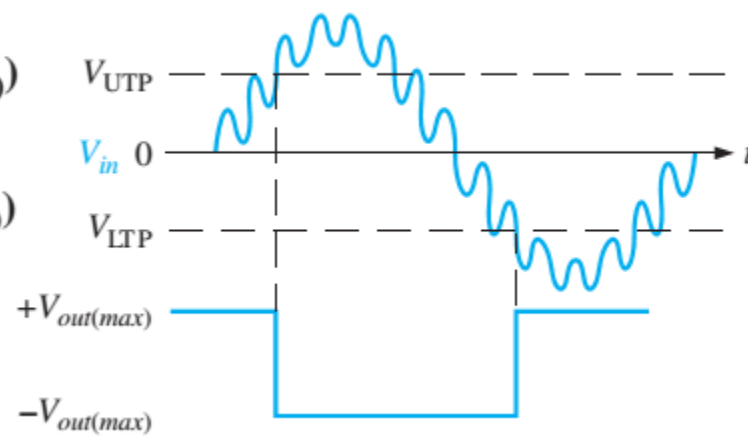


■ Hysteresis

- $+V_{out(max)} \rightarrow -V_{out(max)}$ if V_{in} is greater than V_{UTP} **threshold**
- $-V_{out(max)} \rightarrow +V_{out(max)}$ if V_{in} is smaller than V_{LTP} **threshold**


Application (1)

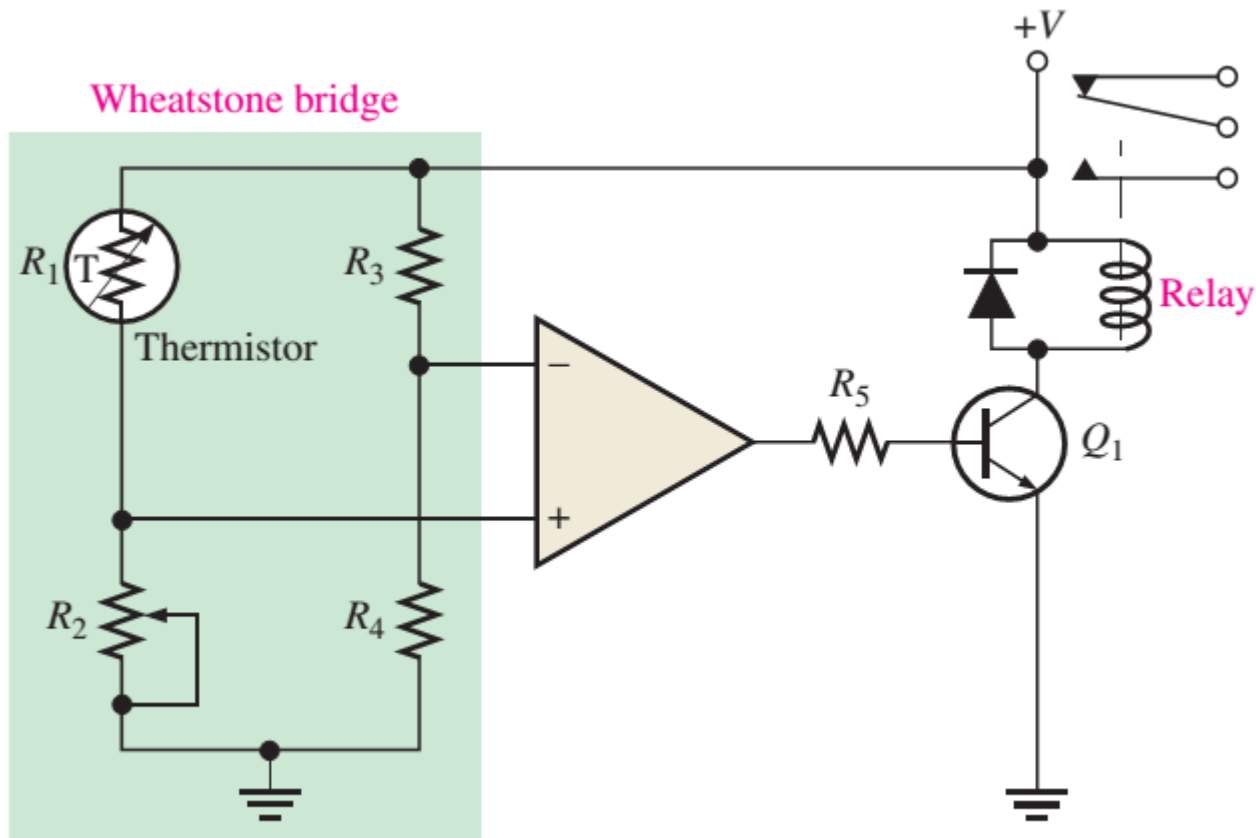- Protection Circuit using Op-Amp Comparator




Application (2)

- Analog to Digital Conversion

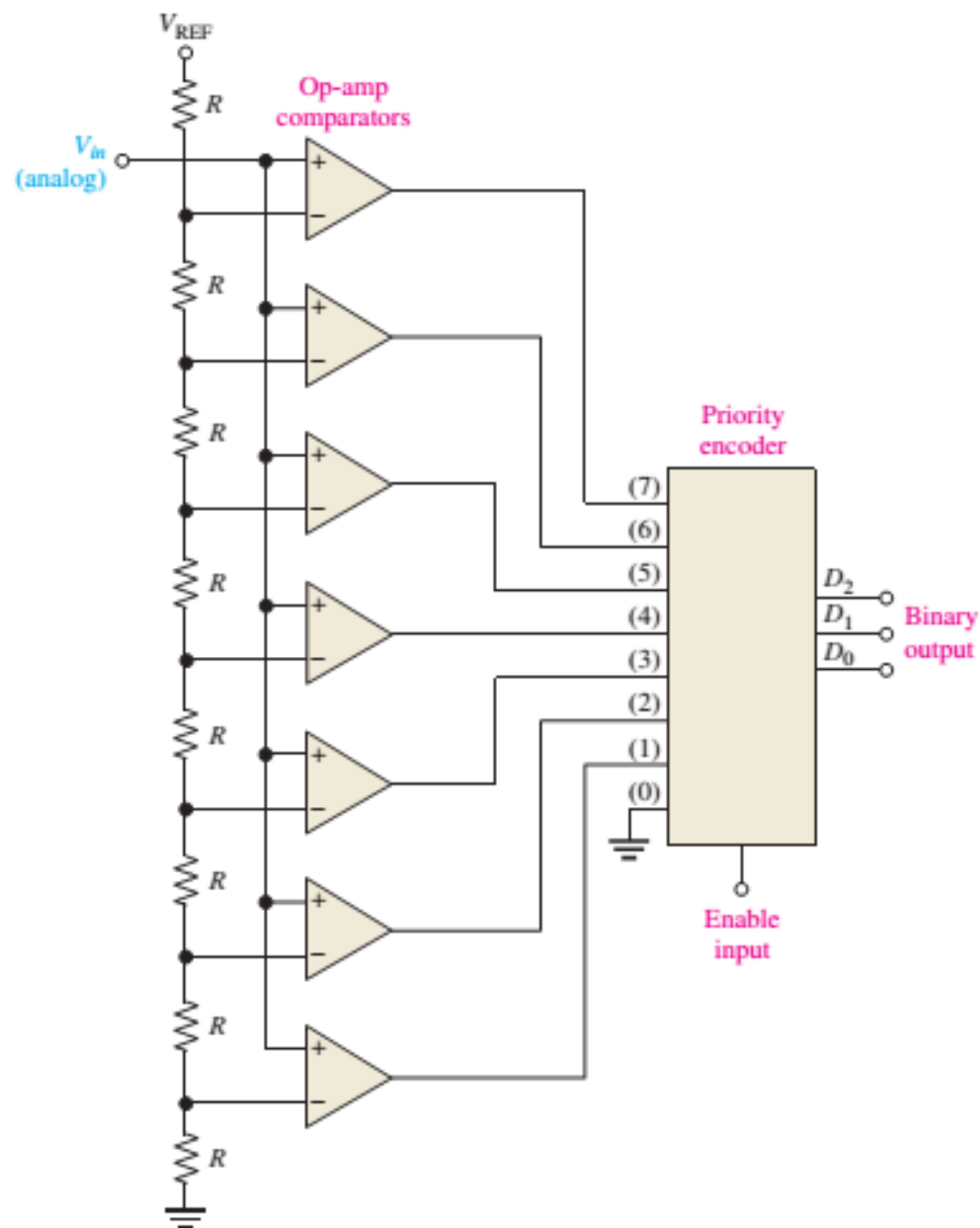

IC 555

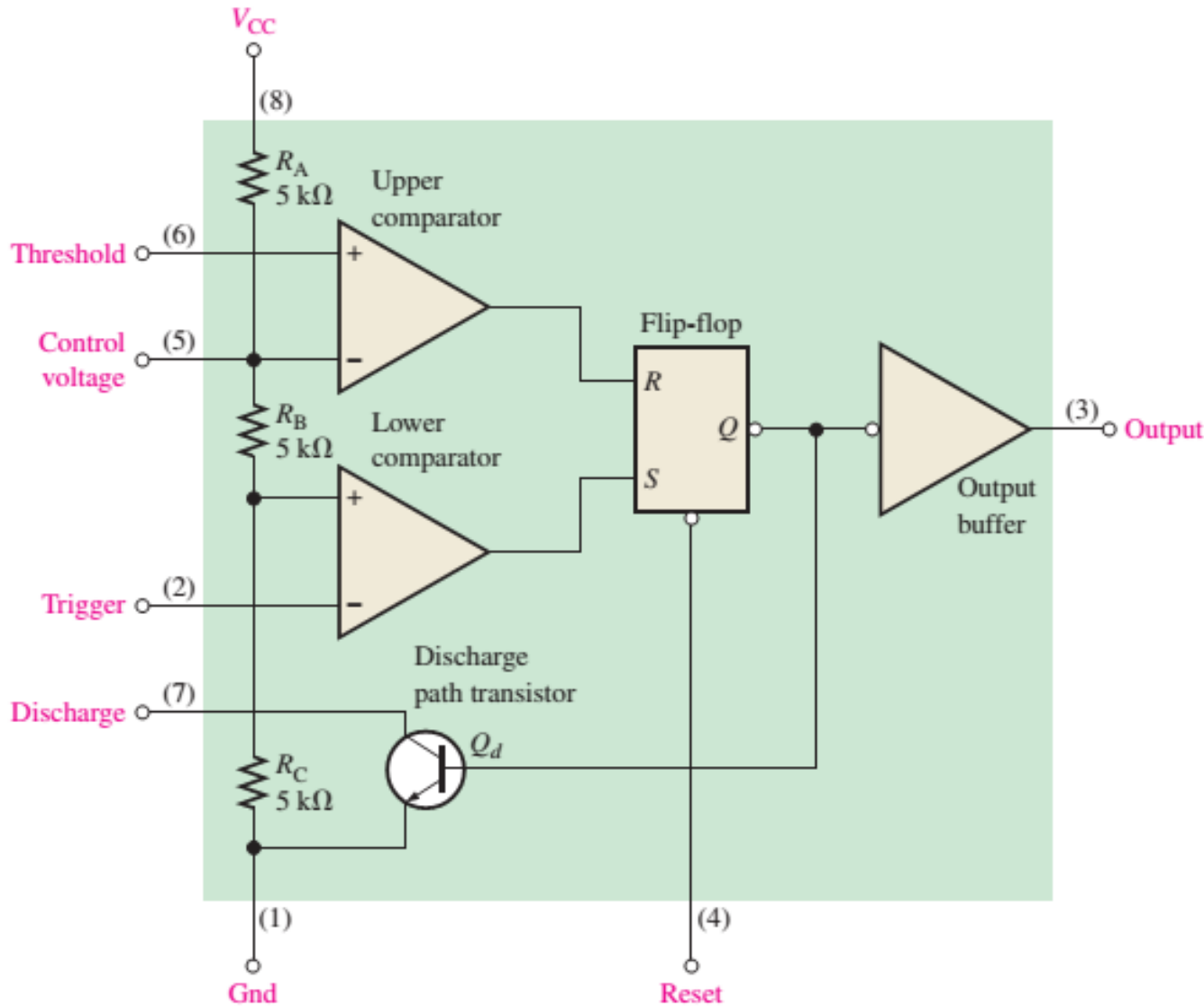


IC555 – Clock Pulse Generator

$$\text{Duty cycle} = \left(\frac{t_H}{T} \right) 100\% = \left(\frac{t_H}{t_H + t_L} \right) 100\%$$


$$\text{Duty cycle} = \left(\frac{R_1 + R_2}{R_1 + 2R_2} \right) 100\%$$

$$f_r = \frac{1.44}{(R_1 + 2R_2)C_{ext}}$$

$$t_H = 0.694(R_1 + R_2)C_{ext}$$

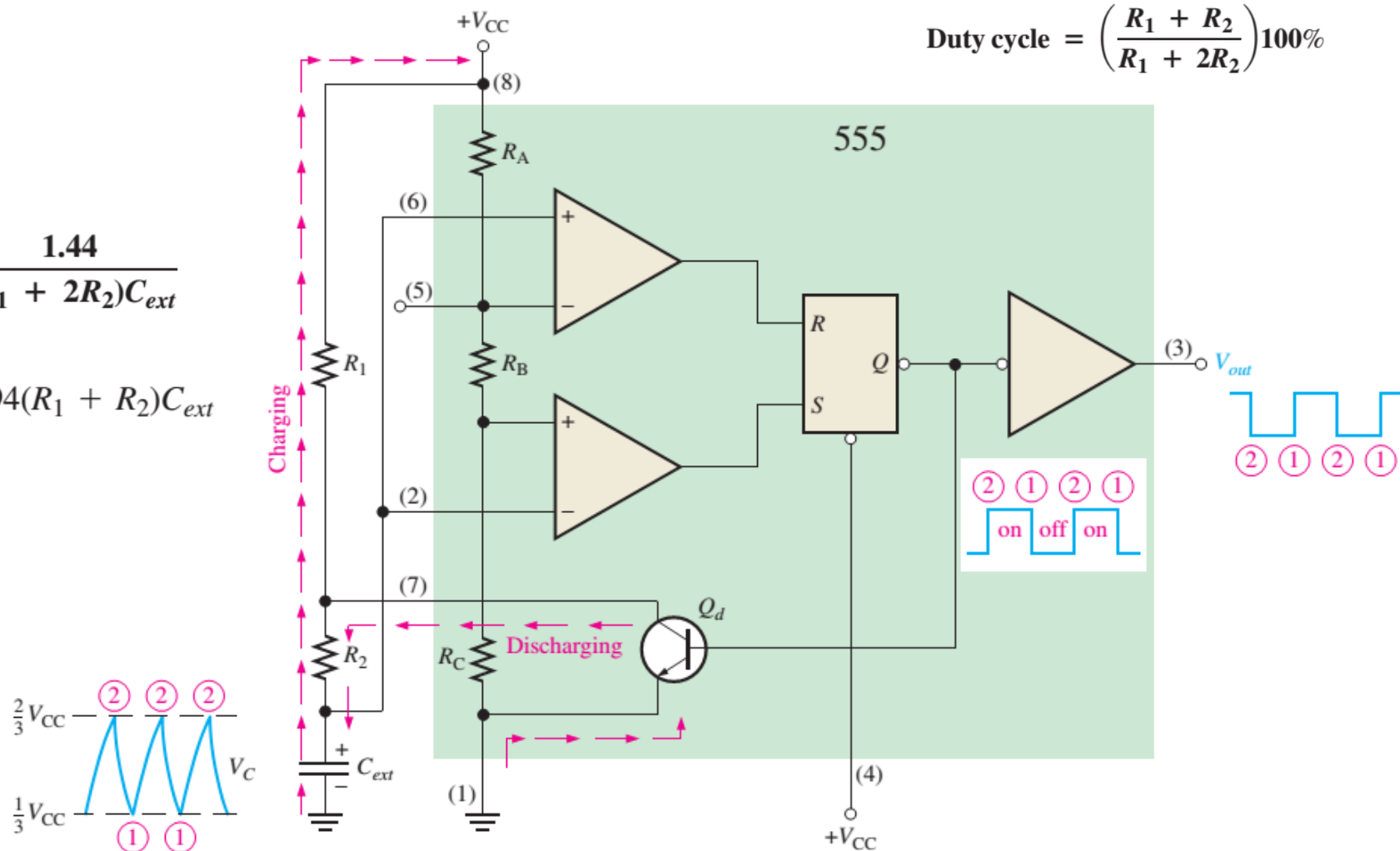

IC555 – Delay Circuit

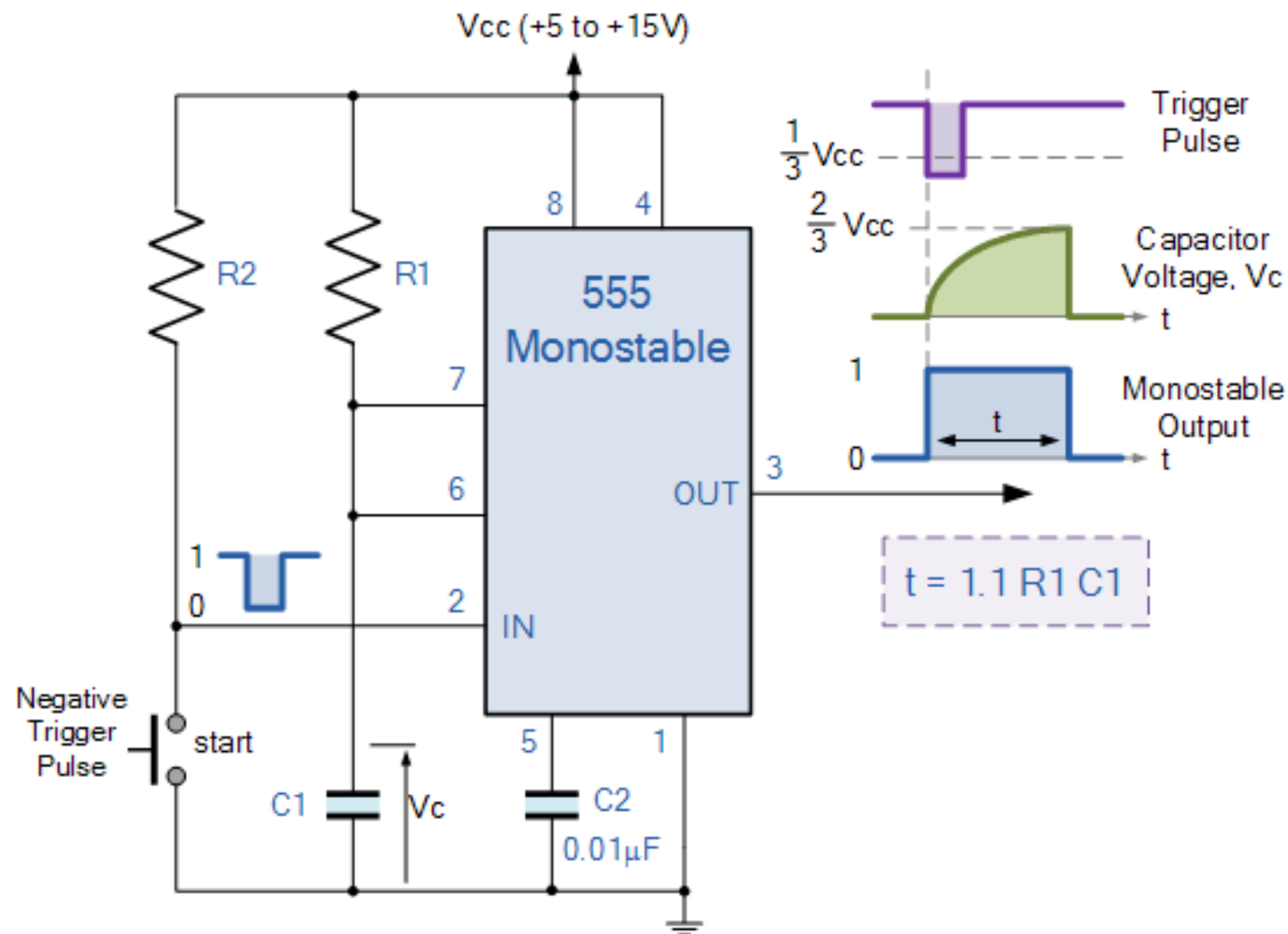

- Calculate the input voltage if the final output is 10.08 V
 - 0.168V

